
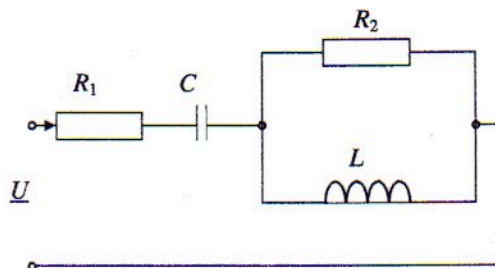


4.a domača naloga iz Osnov elektrotehnike II

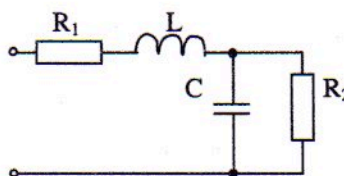
1. V vezju na sliki določite R_2 tako, da bo vezje v resonanci pri krožni frekvenci $\omega_0 = 1000 \text{ s}^{-1}$ ($L = 60 \text{ mH}$, $R_1 = 40 \Omega$, $C = 30 \mu\text{F}$).



2. V vezju na sliki določite R_2 tako, da bo vezje pri $\omega_0 = 1000 \text{ Hz}$ v resonanci. $L = 10 \text{ mH}$, $R_1 = 25 \Omega$ in $C = 50 \mu\text{F}$.



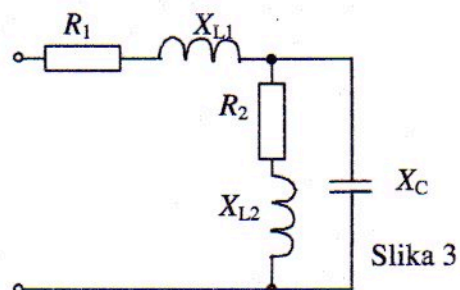3. V vezju na sliki določite X_C tako, da bo vezje v resonanci. $X_{L1} = 10 \Omega$, $R_1 = 8 \Omega$, $R_2 = 10 \Omega$ in $X_{L2} = 12 \Omega$.



Rešitve:

1. $R_2 = 67,08 \Omega$

2. $R_2 = 20 \Omega$

3. $X_{C1} = 14,57 \Omega$
 $X_{C2} = 7,61 \Omega$

(14,18)
(7,82)

4.1a DN


1. malogra

$\omega_0 = 1000 \text{ rad/s}$

$L = 60 \text{ mH}$

$R_1 = 40 \Omega$

$C = 30 \mu\text{F}$

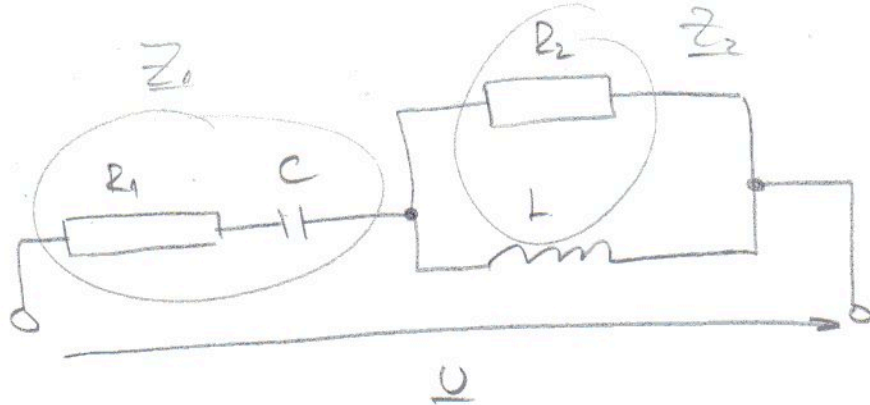

R_2 ? da 60 vezi
u osnovi

$Z = R + j(X_L - X_C)$

$X_L = \omega_0 L = 60 \cdot 10^{-3} \cdot 1 \cdot 10^3 = 60 \Omega$

$X_C = \frac{1}{\omega_0 C} = \frac{1}{1 \cdot 10^3 \cdot 30 \cdot 10^{-6}} = 33,33 \Omega$

$Z = Z_1 + Z_2$

$Z = 40 - j\frac{100}{3} \Omega + \frac{j60R_2}{j60 + R_2}$

$Z_2 = \frac{R_2 \cdot jX_C}{R_2 + jX_C}$

$Z_2 = \frac{j60R_2}{j60 + R_2}$

$Z = 40 - j\frac{100}{3} + \frac{(j60R_2) \cdot (R_2 - j60)}{+3600 + R_2^2}$

$Z = 40 - j\frac{100}{3} + \frac{j60R_2^2 + 3600R_2}{+3600 + R_2^2}$

$\frac{60R_2^2}{+3600 + R_2^2} = \frac{100}{3}$


$180R_2^2 = +360000 + 100R_2^2$

$R_2 = \sqrt{4500} = 67,08 \Omega$



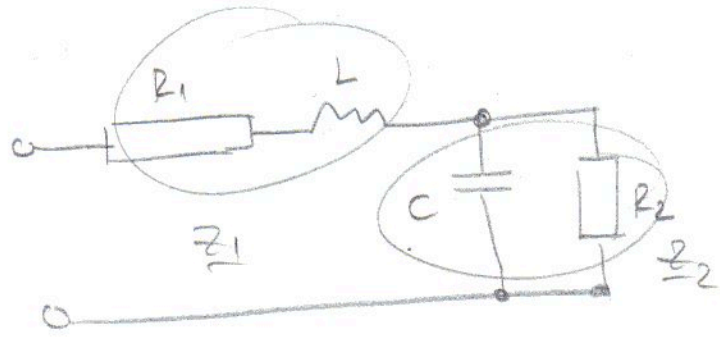Zadatak

$\omega_0 = 1000 \text{ Hz}$
 $L = 10 \text{ mH}$
 $R_1 = 25 \Omega$
 $C = 50 \mu\text{F}$



$R_2 = ?$, da bi
režnja u resonanciji!

$$\text{Im}(Z) = 0$$

$$X_L = \omega_0 L = 1 \cdot 10^3 \cdot 10 \cdot 10^{-3} = \underline{10 \Omega}$$

$$Z = Z_1 + Z_2$$

$$X_C = \frac{1}{\omega_0 C} = \frac{1}{1 \cdot 10^3 \cdot 50 \cdot 10^{-6}} = \underline{20 \Omega}$$

$$Z = 25 + j10 \Omega + \frac{j20R_2}{R_2 - j20}$$

$$Z_2 = \frac{-jX_C R_2}{R_2 - jX_C} = \frac{-j20R_2}{R_2 - j20}$$

$$Z = 25 + j10 + \frac{-j20R_2^2 - 400R_2}{R_2^2 + 400}$$

$$\text{Im}(Z) = 0$$

$$j10 - \frac{j20R_2^2}{R_2^2 + 400} = 0$$

$$\frac{10}{1} = \frac{10R_2^2}{R_2^2 + 400}$$

$$20R_2^2 - 10R_2^2 - 4000 = 0$$

$$R_2^2 (20 - 10) = 4000$$

$$R_2 = \sqrt{\frac{4000}{10}} = \underline{20 \Omega}$$



3.

$$X_{L1} = 10 \Omega$$


$$X_{L2} = 12 \Omega$$

$$R_1 = 8 \Omega$$

$$R_2 = 10 \Omega$$

$$X_C = ? \text{, oba}$$
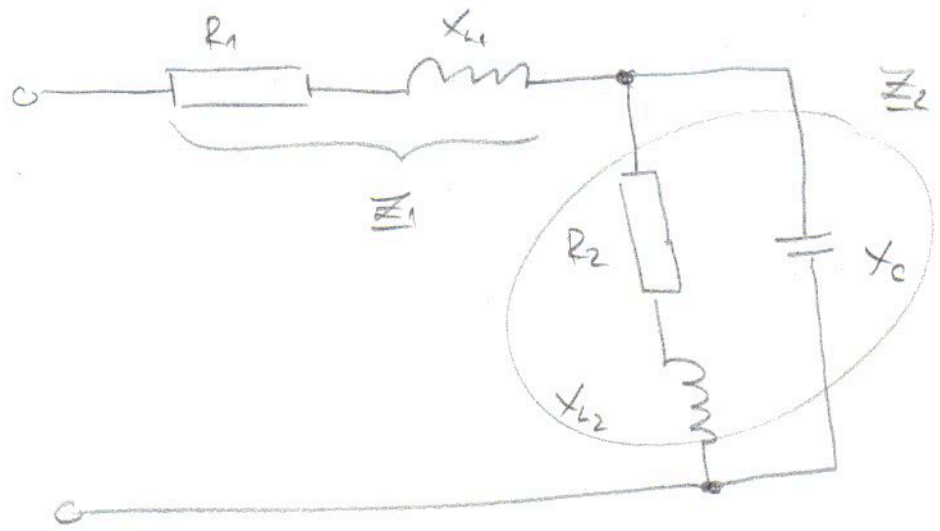
$$\text{bo } \text{Im}(\underline{Z}) = 0$$



$$\underline{Z} = \underline{Z}_1 + \underline{Z}_2$$

$$\underline{Z}_1 = 8 + j10 \Omega$$

$$\underline{Z} = 8 + j10 - \frac{j244X_C + j12X_C^2 + 10X_C^2}{(10 + j(12 - X_C))^2}$$

$$\underline{Z}_2 = \frac{(10 + j12) \cdot (-jX_C)}{10 + j(12 - X_C)} = \frac{12X_C - j10X_C}{10 + j(12 - X_C)}$$

$$\text{Im}(\underline{Z}) = 0$$

$$\underline{Z}_2 = \frac{(12X_C - j10X_C) \cdot (10 - j12 + jX_C)}{(10 + j(12 - X_C))^2}$$

$$\frac{-244X_C + 12X_C^2}{100 + 144 - 24X_C + X_C^2} = -\frac{10}{1}$$

$$\underline{Z}_2 = \frac{120X_C - j144X_C + j12X_C^2 - j100X_C - 120X_C + 10X_C^2}{(10 + j(12 - X_C))^2}$$

$$-2440 + 240X_C - 10X_C^2 = -244X_C + 12X_C^2$$

$$\underline{Z}_2 = \frac{-j244X_C + j12X_C^2 + 10X_C^2}{(10 + j(12 - X_C))^2}$$

$$-2440 + 240X_C - 10X_C^2 + 244X_C - 12X_C^2 = 0$$

$$-22X_C^2 + 484X_C - 2440 = 0$$

$$22X_C^2 - 484X_C + 2440 = 0$$

$$X_{C1,2} = \frac{484 \pm \sqrt{484^2 - 4 \cdot 22 \cdot 2440}}{2 \cdot 22}$$

$$X_{C1} = \underline{14,18 \Omega}$$

$$X_{C2} = \underline{7,82 \Omega}$$

