
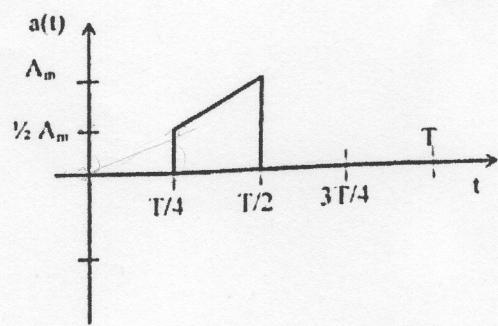


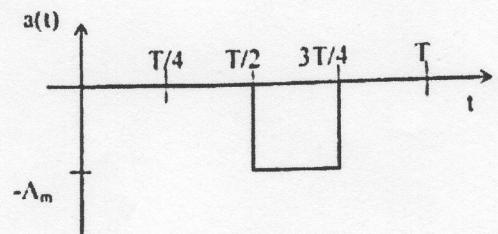- ✓ 1. Izračunajte srednjo efektivno vrednost signala na sliki.




- ✓ 2. Razvijte signal na sliki v Fourierjevo vrsto.




- ✓ 3. V vezju na sliki poznate tok

$$i_2(t) = 5\sqrt{2} \cdot \cos(\omega t + 30^\circ).$$

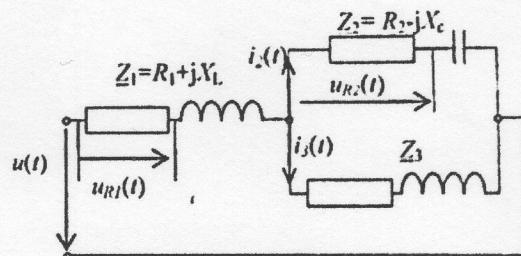Elementi vezja so: $Z_1 = 30 + j20 \Omega$, $Z_2 = 10 - j20 \Omega$ in $Z_3 = 20 + j20 \Omega$. Izračunajte trenutno vrednost napetosti $u_{R1}(t)$.




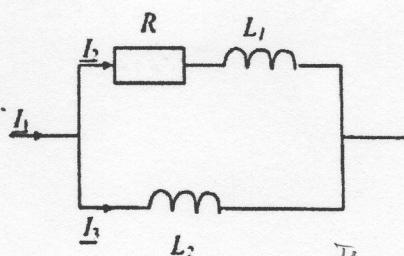4. V vezju na sliki smo izmerili toke $I_1 = 6 \text{ A}$, $I_2 = 4 \text{ A}$ in $I_3 = 3 \text{ A}$. Izračunajte elemente vezja (R , L in C), če poznamo $X_{L2} = 10 \Omega$ (vezje deluje pri $\omega = 500 \text{ s}^{-1}$)



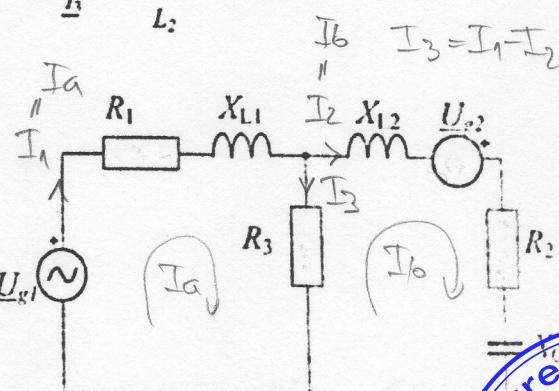5. Izračunajte toke v vezju na sliki.

$$U_{s1} = 100 + j100 \text{ V}, U_{s2} = 60 \text{ V}, R_1 = 5 \Omega, R_2 = 5 \Omega, R_3 = 10 \Omega, X_{L1} = 15 \Omega, X_{L2} = 20 \Omega, X_C = 5 \Omega.$$



a	b	c
$I_a(R_1 + X_{L1} + R_2) - I_b(R_3)$	U_{g1}	
$I_a(R_3)$	$I_b(R_3 + X_{L2} + R_2 + X_C)$	U_{g2}

$$I_a = 7.31 + j1.49 \text{ A}$$

$$I_b = 3.12 + j1.26 \text{ A}$$

COMPLEX MATRIX

$$\begin{pmatrix} 15, 15 \\ 0, -10 \end{pmatrix} \begin{pmatrix} 0, -10 \\ 20, 15 \end{pmatrix}$$

CURRENTS

$$\begin{pmatrix} 100 & 100 \\ 60 & 0 \end{pmatrix}$$


Gregor N

nikolic.gregor@gmail.com
051/636-239



$$I_3 = 10.81 + j2.75 \text{ A}$$

①

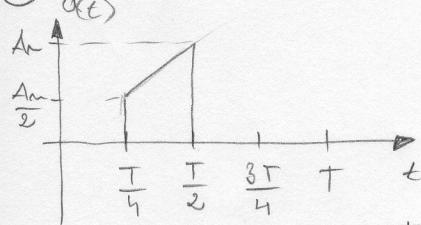


$$\alpha(t) = \begin{cases} \frac{2Am \cdot t}{T}; & \frac{T}{4} \leq t \leq \frac{T}{2} \\ 0; & \text{otherwise} \end{cases}$$

$$A_{\text{av}} = \frac{1}{T} \int_{\frac{T}{4}}^{\frac{T}{2}} \frac{2Am}{T} \cdot t \, dt = \frac{1}{T} \cdot \frac{2Am}{T} \cdot \frac{t^2}{2} \Big|_{\frac{T}{4}}^{\frac{T}{2}} = \frac{2Am}{2T^2} \cdot \left(\frac{4T^2}{16} - \frac{T^2}{16} \right) = \frac{Am}{T^2} \cdot \frac{3T^2}{16} = \frac{3Am}{16}$$

$$A^2 = \frac{1}{T} \int_{\frac{T}{4}}^{\frac{T}{2}} \left(\frac{2Am}{T} \cdot t \right)^2 \, dt = \frac{1}{T} \cdot \frac{4Am^2}{T^2} \cdot \frac{t^3}{3} \Big|_{\frac{T}{4}}^{\frac{T}{2}} - \frac{4Am^2}{3T^3} \cdot \left(\frac{T^3}{8} - \frac{T^3}{64} \right) = \frac{4Am^2}{3T^3} \cdot \frac{7T^3}{64} = \frac{7Am^2}{192}$$

$$\Rightarrow A = \sqrt{\frac{7Am^2}{192}} = \sqrt{\frac{Am}{192}} \cdot \sqrt{\frac{7}{16}}$$

②

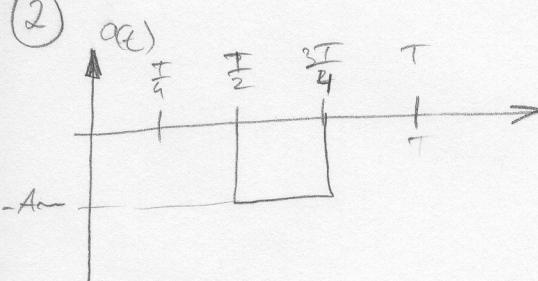

$$A_0 = \frac{2}{T} \int_0^{\frac{T}{2}} \alpha(t) \, dt$$

$$A_0 = \frac{2}{T} \cdot \int_{\frac{T}{2}}^T -Am \, dt = \frac{2Am}{T} \cdot \frac{T}{2} = -\frac{Am}{2}$$

$$A_m = \frac{2}{T} \int_{\frac{T}{2}}^{\frac{3T}{4}} -Am \sin(m\omega t) \, dt = \frac{2}{T} \left(+\frac{Am}{m\pi} \cos(m\omega t) \Big|_{\frac{T}{2}}^{\frac{3T}{4}} \right) = \frac{2Am}{T m \pi \cos(\pi)} \cdot \left(\cos\left(m \frac{3\pi}{2}\right) - \cos(\pi m) \right)$$

$$A_m = \frac{Am}{m\pi} \cdot \left(\cos\left(m \frac{3\pi}{2}\right) - (-1)^n \right)$$

$$B_m = \frac{2}{T} \int_{\frac{T}{2}}^{\frac{3T}{4}} -Am \cos(m\omega t) \, dt = \frac{2Am}{T m \cos(\pi)} \sin(m\omega t) \Big|_{\frac{T}{2}}^{\frac{3T}{4}} = \frac{Am}{m\pi} \cdot \left(\sin\left(m \frac{3\pi}{2}\right) - \sin(\pi m) \right)$$

$$B_m = -\frac{Am}{m\pi} \sin\left(m \frac{3\pi}{2}\right)$$

$$A_1 = \frac{Am}{\pi}, \quad A_2 = \frac{Am}{3\pi}, \quad A_3 = \frac{Am}{5\pi}, \quad B_1 = \frac{Am}{\pi}, \quad B_2 = \emptyset, \quad B_3 = \frac{-Am}{3\pi}, \quad B_4 = \frac{Am}{5\pi}$$

$$\alpha(t) = \frac{Am}{4} + \frac{Am}{\pi} \left(\sin(\omega t) + \frac{1}{2} \sin(2\omega t) + \frac{1}{3} \sin(3\omega t) + \frac{1}{5} \sin(5\omega t) + \dots \right) + \frac{Am}{\pi} \left(\cos(4\omega t) + \frac{1}{5} \cos(6\omega t) + \dots \right)$$



③


$$i_2(t) = 5\sqrt{2} \cos(\omega t + 30^\circ)$$

$$\underline{Z}_1 = 30 + j20 \Omega$$

$$\underline{Z}_2 = 10 - j20 \Omega$$

$$\underline{Z}_3 = 20 + j20 \Omega$$

$$U_{ref}(t) = ?$$

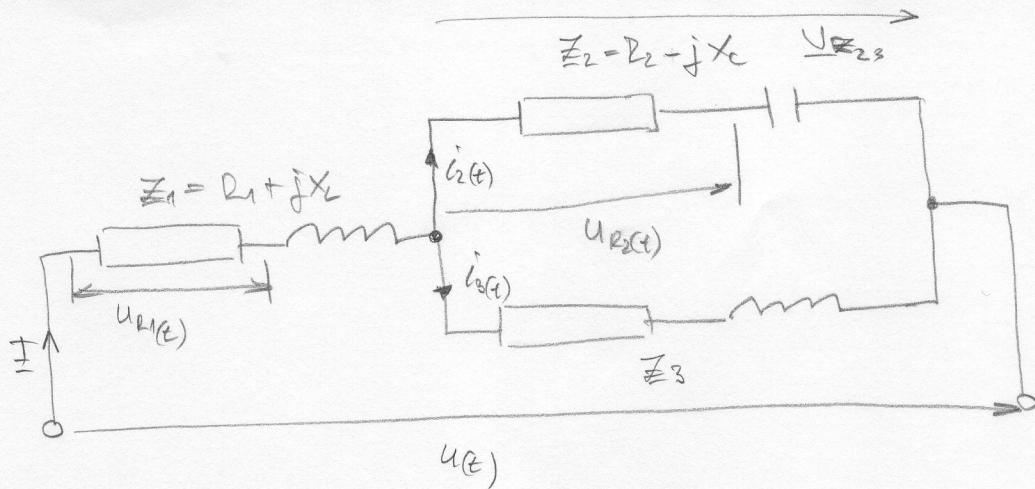

$$\underline{I}_2 = \frac{5\sqrt{2}}{\sqrt{2}} e^{j30^\circ} = \boxed{\frac{5\sqrt{3}}{2} + j\frac{5}{2} \text{ A}}$$

$$\underline{U}_{Z_{23}} = \underline{I}_2 \quad \underline{Z}_2 = \left(\frac{5\sqrt{3}}{2} + j\frac{5}{2} \right) (10 - j20) = \boxed{93,3 \ j61,6 \text{ V}}$$

$$\underline{I}_3 = \frac{\underline{U}_{Z_{23}}}{\underline{Z}_3} = \frac{93,3 - j61,6}{20 + j20} = \boxed{0,179 \ j3,87 \text{ A}}$$

$$\underline{I} = \underline{I}_2 + \underline{I}_3 = \boxed{5,12 \ j137 \text{ A}}$$

$$U_{R_1} = \underline{I} \cdot R_1 = \boxed{153,68 - j41,18 \text{ V}}$$

$$= 153,68 \cdot e^{-j18^\circ}$$

$$\boxed{U_{R_1(t)} = 153,68 \sqrt{2} \cos(\omega t - 18^\circ)}$$