

Preenosna oz. preovojalna funkcija vezja

$$U_2(j\omega) = \frac{U_1(j\omega) \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \Rightarrow \frac{U_2(j\omega)}{U_1(j\omega)} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

$$H(j\omega) = \frac{U_2(j\omega)}{U_1(j\omega)} = \frac{\frac{1}{j\omega C}}{Rj\omega C + 1} = \frac{1}{1 + j\omega RC}$$

$\omega_1 = \frac{1}{RC}$  (najmanj frekvenca)  
 $T_1 = RC$

Amplitudni odziv  $|H(j\omega)|$

$$|H(j\omega)| = \frac{|U_2(j\omega)|}{|U_1(j\omega)|} = \sqrt{\text{Re}^2\{H(j\omega)\} + \text{Im}^2\{H(j\omega)\}}$$

Re:  $\frac{\omega_1^2}{\omega_1^2 + \omega^2}$   
Im:  $\frac{-j\omega\omega_1}{\omega_1^2 + \omega^2}$

$$= \sqrt{\left(\frac{\omega_1^2}{\omega_1^2 + \omega^2}\right)^2 + \left(\frac{-j\omega\omega_1}{\omega_1^2 + \omega^2}\right)^2} = \sqrt{\frac{\omega_1^2(\omega_1^2 + \omega^2)}{(\omega_1^2 + \omega^2)^2}} = \sqrt{\frac{\omega_1^2}{\omega_1^2 + \omega^2}}$$

$\omega_1 = \frac{1}{RC}$

$$= \sqrt{\frac{\frac{1}{(RC)^2}}{1 + (\omega RC)^2}} = \sqrt{\frac{1}{1 + (\omega RC)^2}}$$

$$\Rightarrow |H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

# Fazni odziv

$$\varphi = \arctg \frac{\text{Im} \{H(j\omega)\}}{\text{Re} \{H(j\omega)\}}$$


$$= \arctg \frac{\frac{-\omega R C}{\omega_1^2 + \omega^2}}{\frac{\omega_1^2}{\omega_1^2 + \omega^2}} \Rightarrow \frac{-\omega R C}{\omega_1^2} \Rightarrow -\frac{\omega}{\omega_1} \Rightarrow -\omega R C$$

$\omega_1 = \frac{1}{RC}$

$$\Rightarrow -\arctg(\omega R C)$$

$$H(j\omega) = 20 \cdot \text{Log} |H(j\omega)|$$

$\omega R C$	$ H(j\omega) $	$H(j\omega)$ [dB]	$\varphi$ [°]
0,01	0,99995	-0,000434	-0,573
0,1	0,995	-0,0432	-5,710
0,5	0,894	-0,969	-26,565
1	0,707	-3,010	-45,000
2	0,447	-6,989	-63,435
10	0,110	-20,043	-84,289
100	0,010	-40,000	-89,427

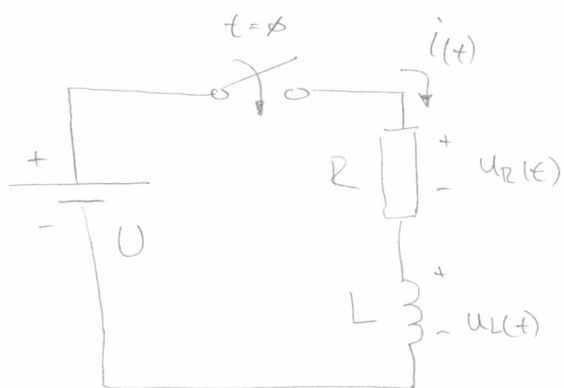

or  $t = 0^-$ :

$$u_R(t) = \phi$$

$$u_L(t) = \phi$$

or  $t = 0^+$ :

$$U = u_R(t) + u_L(t)$$

$$U = i(t)R + L \frac{di(t)}{dt}$$

$i_L = i(t)$

$$U = i(t)R + L \frac{di(t)}{dt}$$

Diferencialna enačba 1. reda  
(1. order)

1. Poiščemo splošno rešitev  
oz. homogeno rešitev.

$$i(t) \cdot R + L \frac{di(t)}{dt} = 0$$

$$L \frac{di(t)}{dt} = -i(t) \cdot R$$

$$\frac{di(t)}{dt} = -\frac{R}{L} \cdot i(t)$$

$$\frac{di(t)}{i(t)} = -\frac{R}{L} \cdot dt \quad \int$$

$$\int \frac{1}{i(t)} di(t) = -\frac{R}{L} \int dt$$

$$\ln(i(t)) = -\frac{R}{L} \cdot t + k_1 / e^x$$

$$e^{\ln(i(t))} = e^{-\frac{R}{L} \cdot t + k_1}$$

$$i(t) = e^{-\frac{R}{L} \cdot t} \cdot e^{k_1} \Rightarrow$$

$$i(t) = k_2 \cdot e^{-\frac{R}{L} \cdot t}$$

# METODA VARIACIJE KONSTANT (Partikularna rešitev)

$$i(t) = k_2 \cdot e^{-\frac{R}{L} \cdot t} \quad k_2 = e^{k_1}$$

+ možno da je tudi spremenljivka zasto odrgamo po parametri:

$$\frac{di(t)}{dt} = \frac{dk_2}{dt} \cdot e^{-\frac{R}{L} \cdot t} + k_2 \cdot e^{-\frac{R}{L} \cdot t} \cdot \left(-\frac{R}{L}\right) \quad (f(x) \cdot g(x))' = f(x)' \cdot g(x) + f(x) \cdot g(x)'$$

$$= \frac{dk_2}{dt} \cdot e^{-\frac{R}{L} \cdot t} - k_2 \cdot e^{-\frac{R}{L} \cdot t} \cdot \frac{R}{L}$$

$$U = i(t)R + L \frac{di(t)}{dt}$$

$$U = R \cdot k_2 \cdot e^{-\frac{R}{L} \cdot t} + L \cdot \left( \frac{dk_2}{dt} \cdot e^{-\frac{R}{L} \cdot t} - k_2 \cdot e^{-\frac{R}{L} \cdot t} \cdot \frac{R}{L} \right)$$

$$U = \cancel{k_2 \cdot e^{-\frac{R}{L} \cdot t} \cdot R} + L \frac{dk_2}{dt} \cdot e^{-\frac{R}{L} \cdot t} - \cancel{k_2 \cdot e^{-\frac{R}{L} \cdot t} \cdot R}$$

$$U = L \frac{dk_2}{dt} \cdot e^{-\frac{R}{L} \cdot t}$$

$$U \cdot \left(e^{-\frac{R}{L} \cdot t}\right)^{-1} = L \frac{dk_2}{dt} \Rightarrow \frac{U}{L} \cdot e^{\frac{R}{L} \cdot t} = \frac{dk_2}{dt}$$

$$dk_2 = \frac{U}{L} \cdot e^{\frac{R}{L} \cdot t} dt \quad \int$$

$$\int dk_2 = \frac{U}{L} \cdot \int e^{\frac{R}{L} \cdot t} dt$$

$$k_2 = \frac{U}{L} \cdot \frac{L}{R} \cdot e^{\frac{R}{L} \cdot t} + k_3$$

$$\boxed{k_2 = \frac{U}{R} \cdot e^{\frac{R}{L} \cdot t} + k_3}$$

vstajino  $\approx i(t)$

$$\int e^{\frac{R}{L} \cdot t} dt = \int e^n dt = \int e^{\frac{n}{L} \cdot L} dn$$

$$\frac{Rt}{L} = n$$

$$\left(\frac{Rt}{L}\right)' dt = (n)' dn$$

$$\frac{R}{L} dt = dn$$

$$dt = \frac{L}{R} dn$$

$$= \frac{L}{R} \cdot e^n + k_3$$

$$i(t) = k_2 \cdot e^{-\frac{R}{L}t}$$

$$i(t) = \left( \frac{U}{R} \cdot e^{\frac{R}{L}t} + k_3 \right) \cdot e^{-\frac{R}{L}t}$$

$$\boxed{i(t) = \frac{U}{R} + k_3 e^{-\frac{R}{L}t}}$$

Za  $k_3$ :

$$i(0^+) = i(t) = \varnothing = i(0^+);$$

$$i(0^+) = \frac{U}{R} + k_3 \cdot \underbrace{e^{-\frac{R}{L} \cdot \varnothing}}_1 \Rightarrow \boxed{k_3 = -\frac{U}{R}}$$

$$R: \boxed{i(t) = \frac{U}{R} \left( 1 - e^{-\frac{R}{L}t} \right) A}$$

$$u_R(t) = i(t) \cdot R$$

$$= \boxed{U \cdot \left( 1 - e^{-\frac{R}{L}t} \right) V}$$

$$u_L(t) = L \frac{di}{dt} = L \frac{d\left(\frac{U}{R} \left( 1 - e^{-\frac{R}{L}t} \right)\right)}{dt} = L \frac{U}{R} \cdot \left( -e^{-\frac{R}{L}t} \right) \cdot \left( -\frac{R}{L} \right)$$

$$u_L(t) = \boxed{U e^{-\frac{R}{L}t} V}$$

$$P_e(t) = u_R(t) \cdot i(t)$$


$$= U e^{-\frac{R}{L}t} \cdot \left( \frac{U}{R} \left( 1 - e^{-\frac{R}{L}t} \right) \right)$$

$$= \frac{U^2}{R} \cdot e^{-\frac{R}{L}t} \left( 1 - e^{-\frac{R}{L}t} \right)$$


$$= \boxed{\frac{U^2}{R} \left( 1 - e^{-\frac{R}{L}t} \right)^2}$$

$$P_L(t) = u_L(t) \cdot i(t)$$
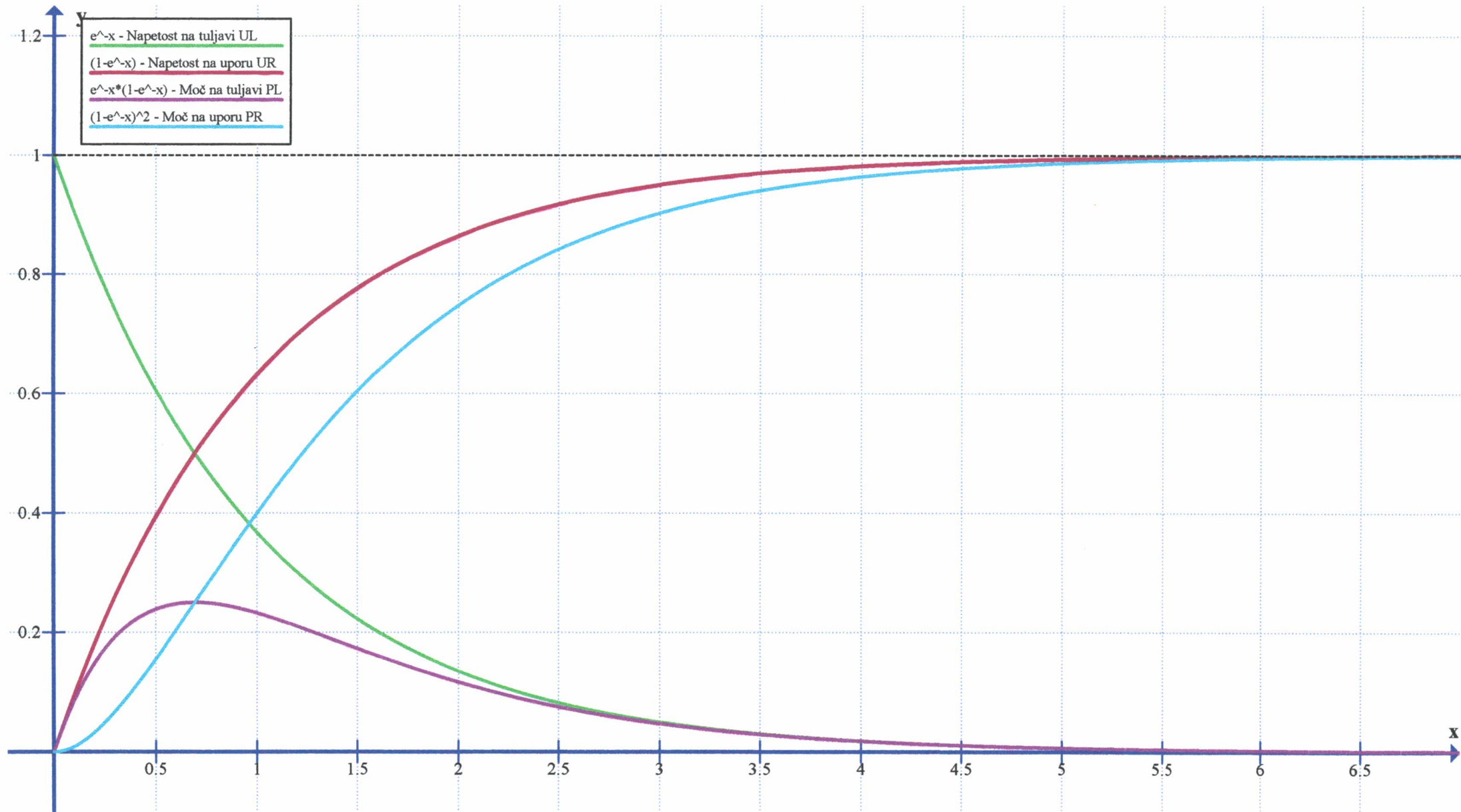
$$= \boxed{\frac{U^2}{R} \cdot e^{-\frac{R}{L}t} \left( 1 - e^{-\frac{R}{L}t} \right)}$$



# Emotina stopnica

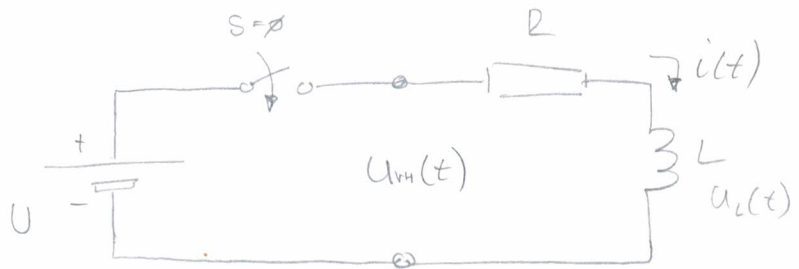


$$① \quad U_{RH}(p) = \frac{U}{p}$$

$$② \quad H(p) = \frac{U_{RH}(p)}{U_{RH}(p)}$$

$$H(p) = \frac{I(p) \cdot pL}{I(p) \cdot (R + pL)}$$

$$H(p) = \frac{pL}{R + pL}$$

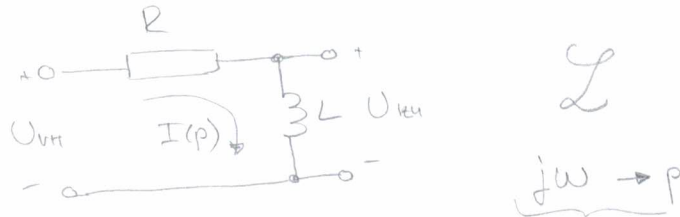

$$U_{RH} = I(j\omega) \cdot (R + j\omega L)$$

$$U_{RH} = I(j\omega) \cdot j\omega L$$

$$\begin{cases} U_{RH} = I(p) \cdot (R + pL) \\ U_{RH} = I(p) \cdot pL \end{cases}$$

$$③ \quad U_{RH}(p) = U_{RH}(p) \cdot H(p)$$


$$U_{RH}(p) = \frac{U}{p} \cdot \frac{pL}{R + pL} = \frac{UL}{R + pL}$$

$$\boxed{\frac{1}{p+a} \rightarrow e^{-at}} \quad \text{+ transform}$$

$$U_{RH}(p) = U \cdot \frac{1}{\frac{R}{L} + p}$$

$$④ \quad \text{Prieslibava } U_{RH}(p) \rightarrow U_{RH}(t) \rightarrow U_{RH}(t) = e^{-\frac{R}{L}t}$$

PREHODNI POKLAVI

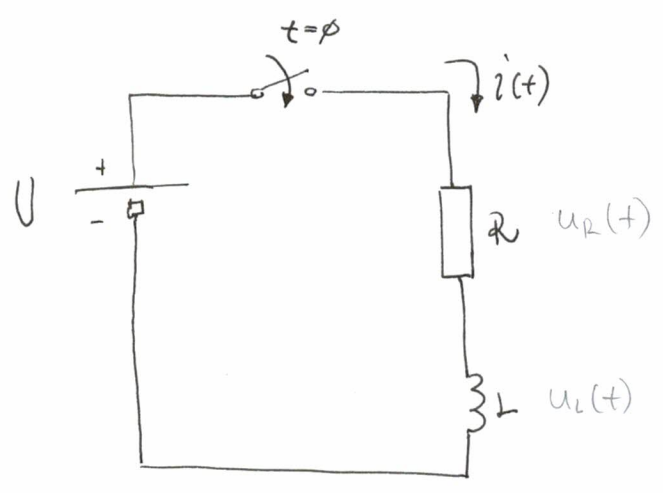

POMNI:

$$i_c = C \frac{du_c}{dt}$$

$$u_L = L \frac{di_L}{dt}$$

$t = \phi^-$

$$u_R(t) = \phi$$

$$u_L(t) = \phi$$

$t = \phi^+$

$$U = u_R(t) + u_L(t) \quad i_L = i(t)$$

$$= i(t) \cdot R + L \frac{di(t)}{dt} \quad \leadsto \text{diferencialna ena\u010dba 1. reda}$$

① Homogena re\u0161itev:

$$i(t) \cdot R + L \frac{di(t)}{dt} = \phi$$

$$L \frac{di(t)}{dt} = -i(t) \cdot R \quad /: iL$$

$$\frac{di(t)}{dt} = -i(t) \cdot \frac{R}{L} \quad /: i(t) \quad /: dt$$

$$\frac{di(t)}{i(t)} = -\frac{R}{L} dt \quad / \int$$

$$\ln(i(t)) = -\frac{R}{L} \int_0^t dt$$

$$\ln(i(t)) = -\frac{R}{L} \cdot t + k_1 \quad / e^x \quad \leftarrow \text{konstanta}$$

$$i(t) = e^{-\frac{R}{L}t} \cdot e^{k_1}$$

$$i(t) = e^{-\frac{R}{L}t} \cdot k_2$$

↓  
je lahko tudi  
Sprenelj\u0161evka



# metoda variacije konstant (parcijalna rezider)

- odvajamo homogenu rezider

$$\text{homogena: } \underline{i(t) = k_2 e^{-\frac{R}{L}t}} \quad (k_2' e^{-\frac{R}{L}t} + k_2 e^{-\frac{R}{L}t})$$

$$\underline{\frac{di(t)}{dt} = \frac{dk_2}{dt} \cdot e^{-\frac{R}{L}t} + k_2 \cdot e^{-\frac{R}{L}t} \cdot \left(-\frac{R}{L}\right)}$$

1. enačba (na zveščku):  $U = i(t) \cdot R + L \frac{di(t)}{dt}$

$$\Rightarrow U = k_2 \cdot e^{-\frac{R}{L}t} \cdot R + L \left( \frac{dk_2}{dt} \cdot e^{-\frac{R}{L}t} - k_2 \cdot e^{-\frac{R}{L}t} \cdot \frac{R}{L} \right)$$

$$U = \cancel{k_2 \cdot e^{-\frac{R}{L}t} \cdot R} + \frac{dk_2}{dt} \cdot e^{-\frac{R}{L}t} \cdot L - \cancel{k_2 \cdot e^{-\frac{R}{L}t} \cdot R}$$

$$U = \frac{dk_2}{dt} \cdot e^{-\frac{R}{L}t} \cdot L$$

$$\frac{dk_2}{dt} = \frac{U}{L e^{-\frac{R}{L}t}} \Rightarrow \frac{dk_2}{dt} = \frac{U}{L} \cdot e^{\frac{R}{L}t} \quad / \cdot dt$$

$$1 \cdot dk_2 = \frac{U}{L} \cdot e^{\frac{R}{L}t} dt \quad // \quad - \text{integriramo!}$$

$$k_2 = \frac{U}{L} \cdot e^{\frac{R}{L}t} \cdot \frac{L}{R} = \boxed{\frac{U}{R} \cdot e^{\frac{R}{L}t} + k_3}$$

↓  
vstavimo v  $i(t)$

$$\Rightarrow i(t) = \left( \frac{U}{R} \cdot e^{\frac{R}{L}t} + k_3 \right) \cdot e^{-\frac{R}{L}t} =$$

$$= \frac{U}{R} + k_3 e^{-\frac{R}{L}t}$$

$$\Rightarrow \text{Za } k_3: \quad t = 0^+ \quad i(t) = 0 = i(0^+);$$

$$i(0^+) = \frac{U}{R} + k_3 \cdot \underbrace{e^{-\frac{R}{L} \cdot 0}}_1$$

$$\text{Z: } i(t) = \frac{U}{R} - \frac{U}{R} \cdot e^{-\frac{R}{L}t}$$

$$\Rightarrow \boxed{i(t) = \frac{U}{R} \left( 1 - e^{-\frac{R}{L}t} \right)}$$

$$\Rightarrow \boxed{k_3 = -\frac{U}{R}}$$

$$u_R(t) = i(t) \cdot R = \frac{U}{R} (1 - e^{-\frac{R}{L} \cdot t}) \cdot R = \frac{L}{R} = \tau$$

$$= \boxed{U (1 - e^{-\frac{R}{L} \cdot t})}$$

$$u_L(t) = L \frac{di(t)}{dt} = \frac{-R U}{R} \cdot e^{-\frac{R}{L} \cdot t} \cdot \left(-\frac{R}{L}\right) = \boxed{+ U \cdot e^{-\frac{R}{L} \cdot t}}$$


$$P_L(t) = u_L(t) \cdot i(t) =$$

$$= U e^{-\frac{R}{L} \cdot t} \cdot \frac{U}{R} (1 - e^{-\frac{R}{L} \cdot t}) = \boxed{\frac{U^2}{R} e^{-\frac{R}{L} \cdot t} (1 - e^{-\frac{R}{L} \cdot t})}$$


$$P_R(t) = u_R(t) \cdot i(t) =$$

$$= U (1 - e^{-\frac{R}{L} \cdot t}) \cdot \frac{U}{R} (1 - e^{-\frac{R}{L} \cdot t}) = \boxed{\frac{U^2}{R} (1 - e^{-\frac{R}{L} \cdot t})^2}$$

$\tau$	$u_R(t) = U (1 - e^{-\frac{t}{\tau}})$	$u_L(t) = U \cdot e^{-\frac{t}{\tau}}$	$i(t) = \frac{U}{R} (1 - e^{-\frac{t}{\tau}})$	$P_L(t) = \frac{U^2}{R} (1 - e^{-\frac{t}{\tau}})$	$P_R(t) = \frac{U^2}{R} (1 - e^{-\frac{t}{\tau}})^2$
1	0,632	0,369	0,632	0,233	0,399
2	0,865	0,135	0,865	0,117	0,748
3	0,950	0,0499	0,950	0,0473	0,903
4	0,982	0,0183	0,982	0,0179	0,964
5	0,993	0,00674	0,993	0,00669	0,987

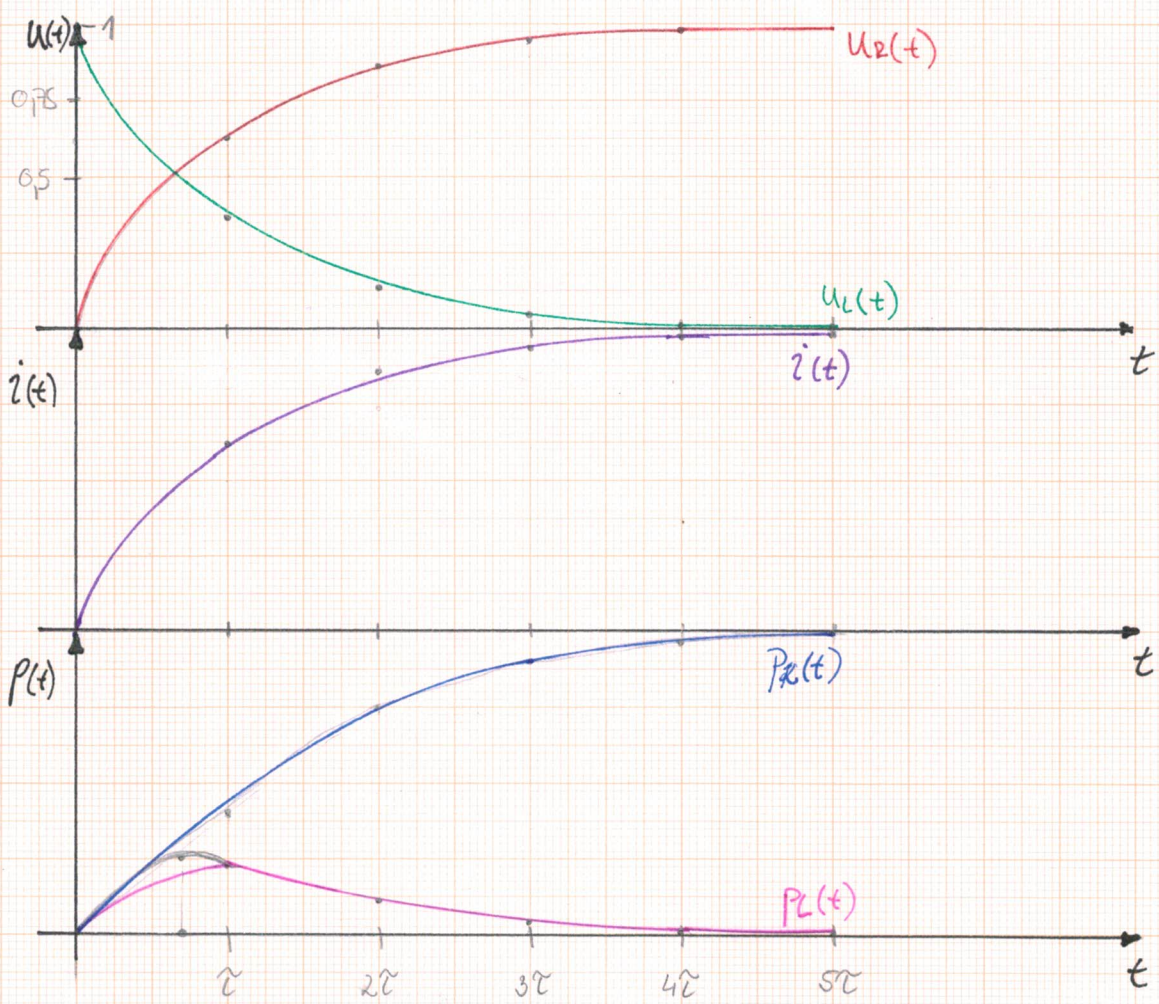


3. Zylal - pueholni pojivo

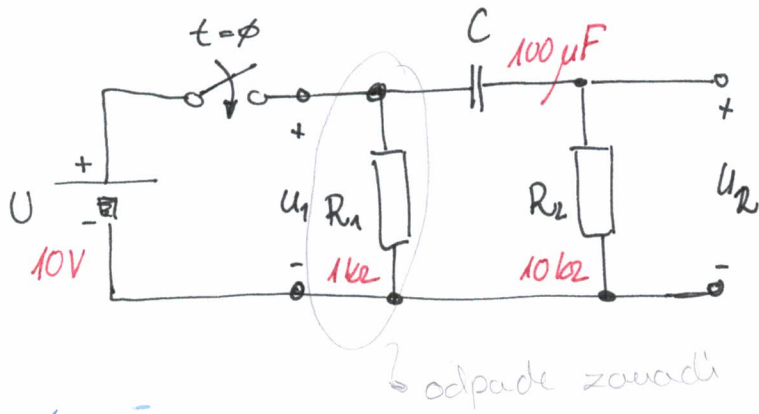

$U_2(t) = ?$


$t = 0^-$

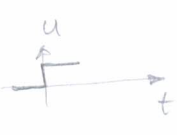1. Na vhodu rezjer je enotina stopnica  sledi: 

$F(t)$	$\mathcal{L}$
$u(t)$	$\frac{1}{s}$ (p)

$$U_1(p) = U \cdot \frac{1}{p} = \frac{U}{p}$$

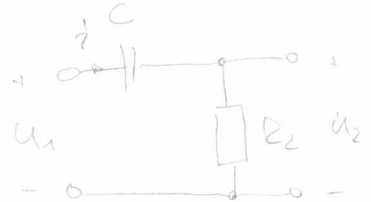2. Zapiseru puevajerno funkcijo rezjer:  $p = j\omega$



$$H(p) = \frac{U_2(p)}{U_1(p)}$$

$$H(p) = \frac{R_2}{R_2 + \frac{1}{pC}} = \frac{pR_2C}{pR_2C + 1}$$

3. Zapiseru enotno ka izhodno napetost  $U_2(t)$  v puevajerno funkcijo  $H(p)$ :

$$U_2(p) = H(p) \cdot U_1(p) \Rightarrow U_2(p) = \frac{pR_2C}{pR_2C + 1} \cdot \frac{U}{p} = U \cdot \frac{1}{p + \frac{1}{R_2C}}$$


$$U_2(t) = U \cdot e^{-\frac{t}{R_2C}} \quad \tau = R_2C$$

$$\boxed{U \cdot e^{-\frac{t}{\tau}} \text{ [V]}}$$


Transformirano v časovni puotam

$$F(p) \rightarrow F(t)$$

$F(p)$	$F(t) \text{ } 0 \leq t$
$\frac{1}{p+a}$	$e^{-at}$

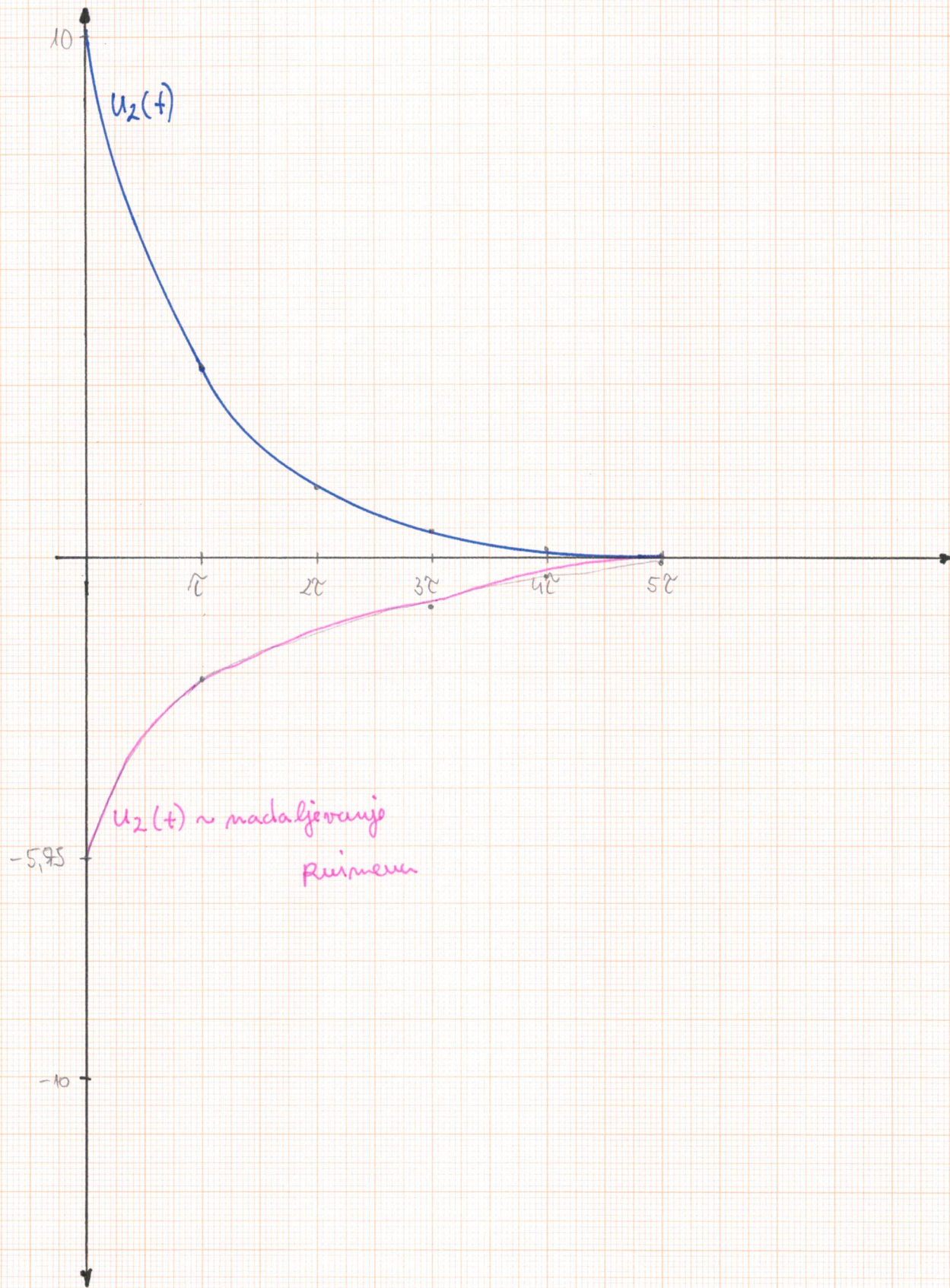

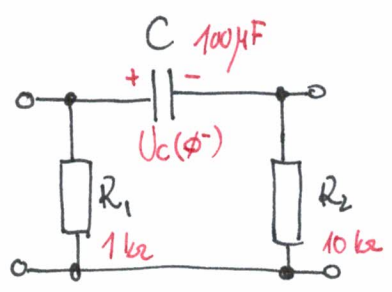naduljevanje pri meri: - izlopinno stikalo v času  $t$





$$U_C(\phi^-) = U - U_2(\phi^-) = 10V - 3,68V = \boxed{6,32V}$$

Nabit kondenzator nadomestimo z modelom:

$t = \phi^+$

$$R_{12} = R_1 + R_2$$

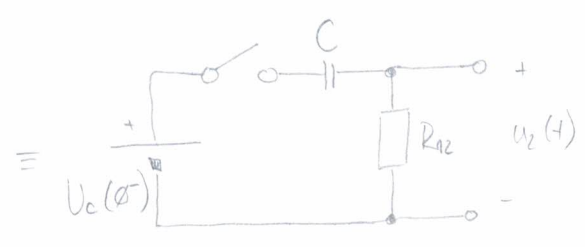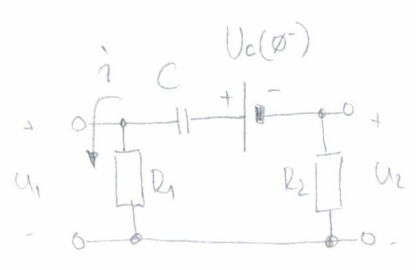

$$U_C(t) = U_C(\phi^-) \cdot (1 - e^{-\frac{t}{\tau}})$$

$$i_C = C \frac{dU_C(t)}{dt} = C \cdot U_C(\phi^-) \cdot (+e^{-\frac{t}{\tau}}) \cdot (+\frac{1}{\tau}) = C \cdot U_C(\phi^-) \cdot \frac{1}{R_{12}} \cdot e^{-\frac{t}{\tau}}$$

$$\tau = R_{12}C$$


$$= \frac{U_C(\phi^-) \cdot e^{-\frac{t}{\tau}}}{R_{12}}$$

konduktorov želi tož, v obratni smeri

$$U_2(t) = -i_C(t) \cdot R_2$$

$$= -\frac{R_2 U_C(\phi^-)}{R_{12}} \cdot e^{-\frac{t}{\tau}} = -\frac{10k\Omega \cdot 6,32V}{11k\Omega} \cdot e^{-\frac{t}{\tau}} = \boxed{-5,75 \cdot e^{-\frac{t}{\tau}} [V]}$$

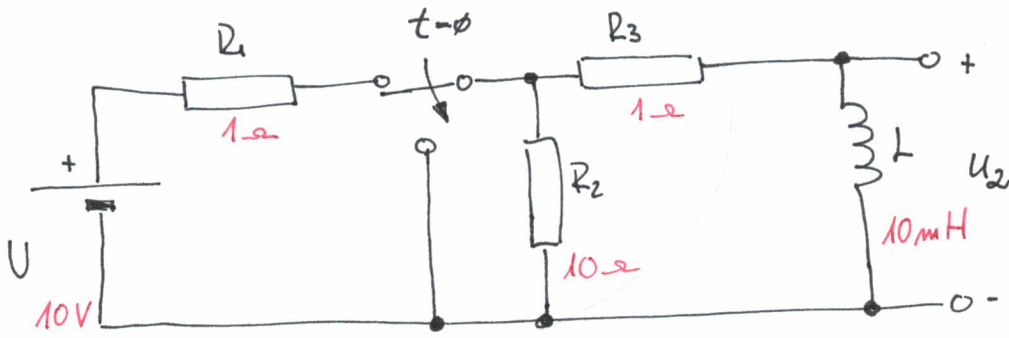
Prehodni pojav - zglej s tuljavo (potek napetosti po preoblopi stikala) ( $u_2(t)$ )







$$u_2(t) = ?$$

$t = 0^-$

Themin

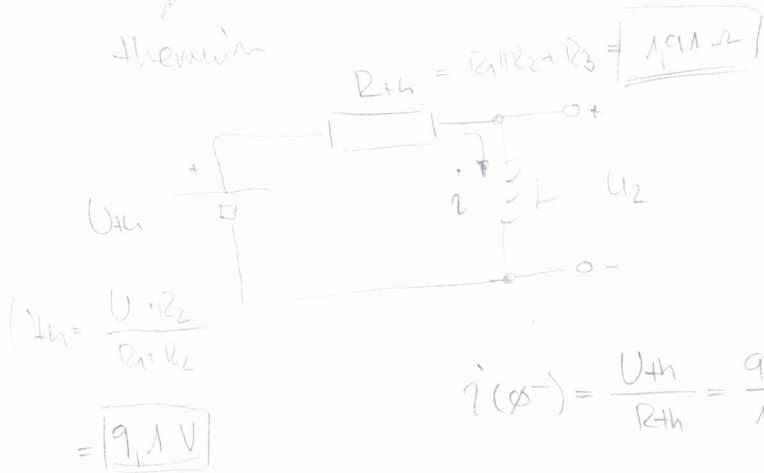

$t = 0^+$

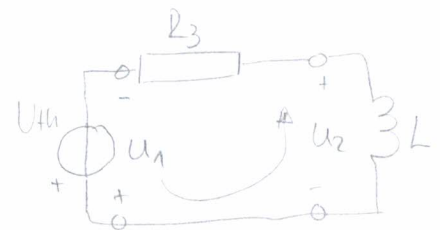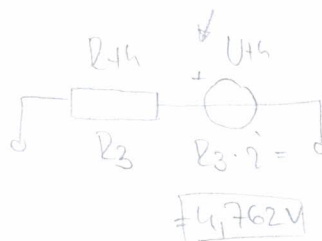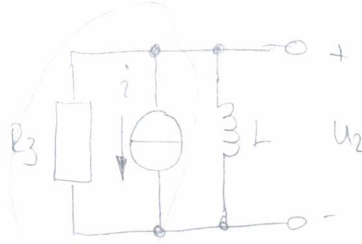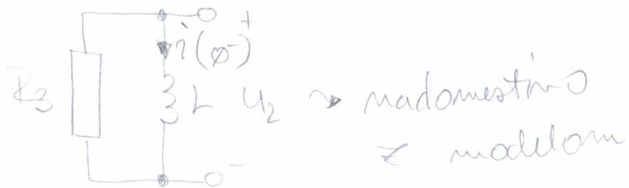

$$(1.) U_2(s) = \left[ U_{th} \cdot \frac{1}{P} \right] \quad (\text{stopnica})$$

"  $U_1(p)$

(2.) Pevnjalna funkcija:

$$H(p) = \frac{U_2(p)}{U_1(p)} = \frac{pL}{pL + R_3}$$

(3.)  $U_2(p)$

$$U_2(p) = U_1(p) \cdot H(p) = \frac{U_{th}}{P} \cdot \frac{pL}{pL + R_3} = \boxed{U_{th} \cdot \frac{1}{p + \frac{R_3}{L}}}$$

$F(s)$	$f(t)$
$\frac{1}{p+a}$	$e^{-at}$


(4.)  $\tau$  časovni konstanta

$$\tau = \frac{L}{R_3}$$


$$U_2(t) = U_{th} \cdot e^{-\frac{R_3}{L} t}$$
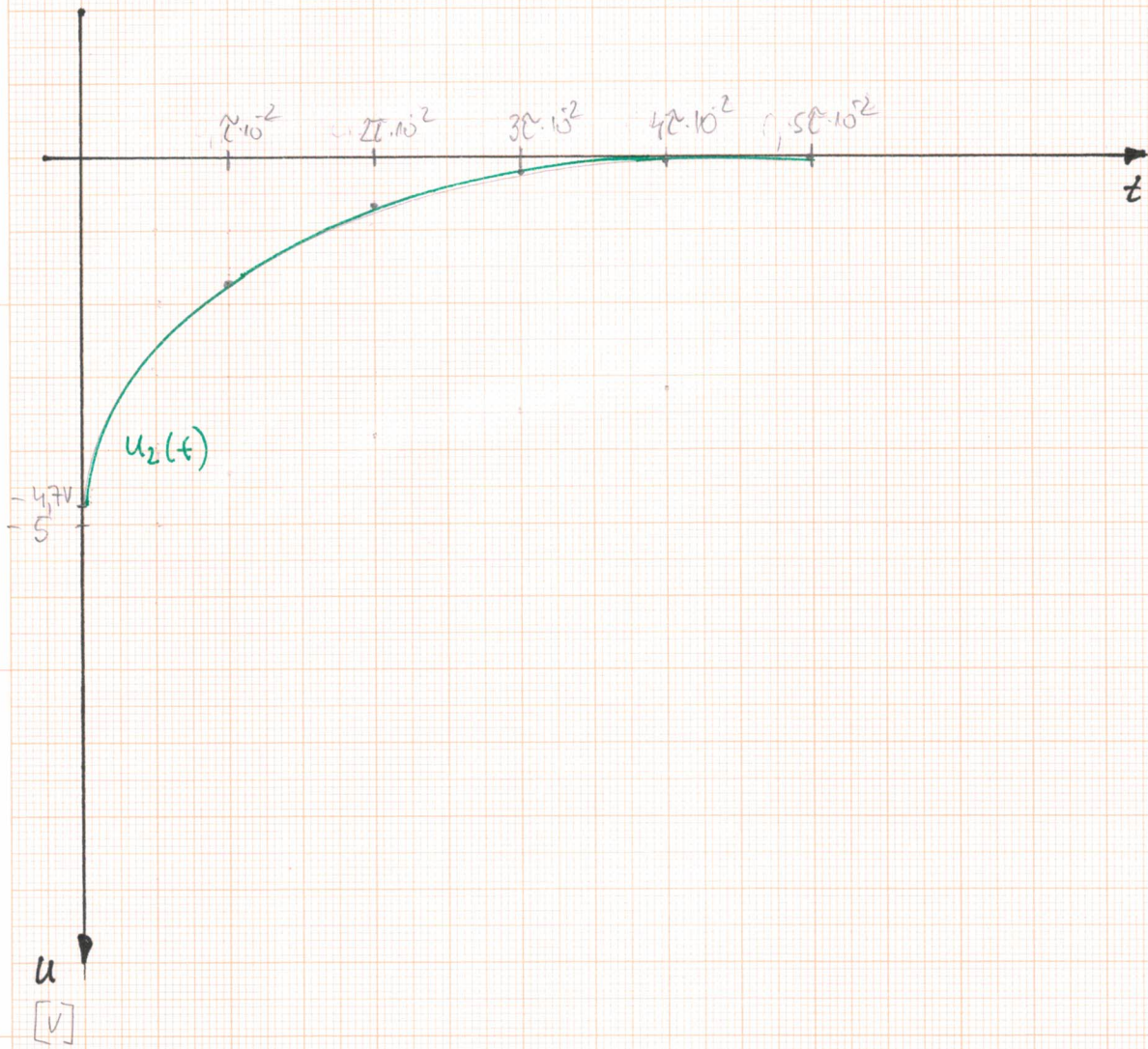
$$= \boxed{U_{th} \cdot e^{-\frac{t}{\tau}}}$$






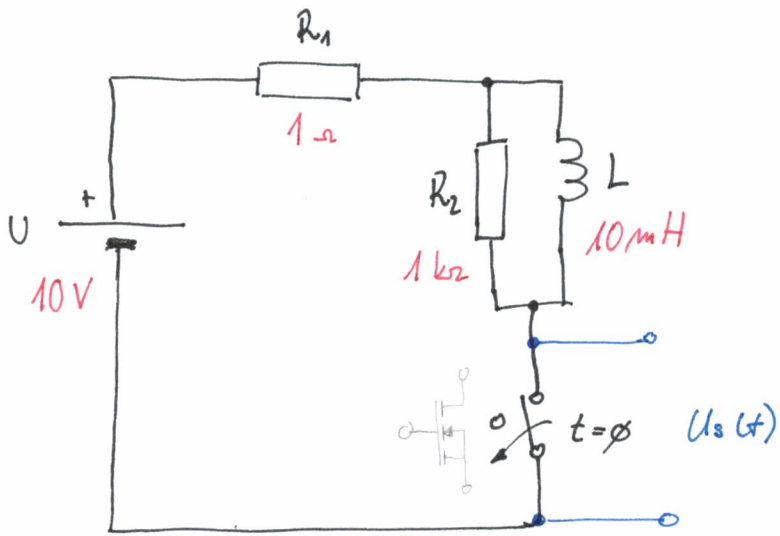Predalnik pojmovi - napetost na tiskalu ob izklopu



$t = 0^-$


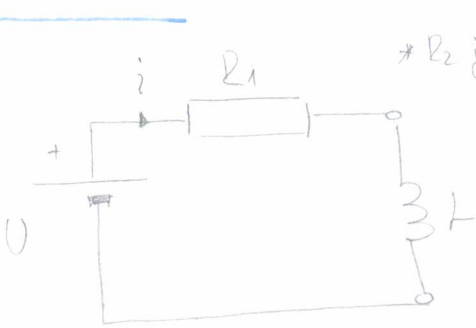


\*  $R_2$  je odpadel saj je  $L$  v stacionarni reazni kvantiteta stika.


$$I(0^-) = \frac{U}{R_1} = \frac{10V}{1\Omega} = \boxed{10A}$$

$t = 0^+$

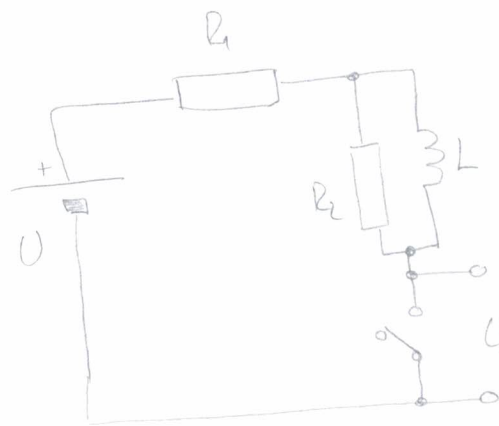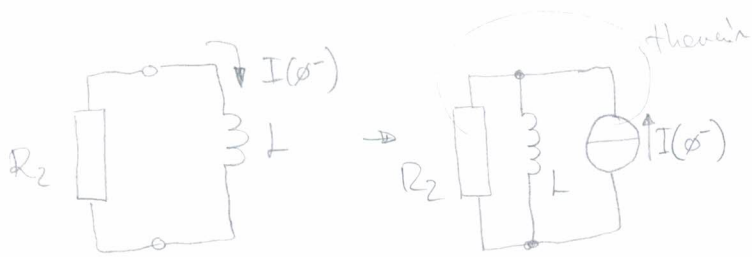\* V naslednji je že računani tok  $I(0^-)$ ;



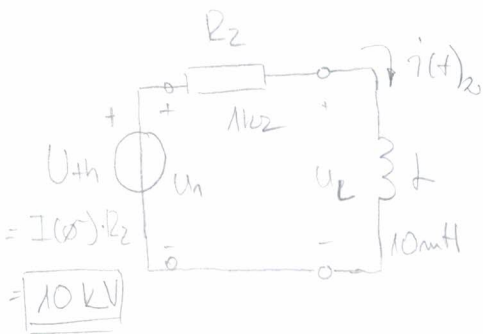(napetost na  $R_1$  mi, ker tok ne teče skozi)



$$H(p) = \frac{U_L(p)}{U_{th}(p)} = \frac{pL}{pL + R_2} = \frac{p}{p + \frac{R_2}{L}}$$

\*  $\frac{1}{p} \cdot U_{th}$

$$U_L(p) = H(p) \cdot U_{th}(p)$$

$$= \frac{U_{th}}{p} \cdot \frac{p}{p + \frac{R_2}{L}} = U_{th} \cdot \frac{1}{p + \frac{R_2}{L}} = U_{th} \cdot \frac{1}{p + a}$$

$F(p)$	$f(t)$
$\frac{1}{p+a}$	$e^{-at}$

$$U_{R_2}(t) = U_{th} - U_L = U_{th} - U_{th} \cdot e^{-\frac{R_2}{L}t} = U_{th} \left(1 - e^{-\frac{t}{\tau}}\right) [V]$$

$$\tau = \frac{L}{R_2}$$

$$i(t)_{R_2} = \frac{U_{R_2}(t)}{R_2} = \frac{U_{th}}{R_2} \cdot \left(1 - e^{-\frac{t}{\tau}}\right) [A]$$

$$i(t) = I(\infty) + i(t)_{R_2} = I(\infty) + \frac{U_{th}}{R_2} \cdot \left(1 - e^{-\frac{t}{\tau}}\right)$$


$$\begin{aligned} i_L(t) &= I(\infty) - i(t) = \cancel{I(\infty)} - \cancel{I(\infty)} - \frac{U_{th}}{R_2} \left(1 - e^{-\frac{t}{\tau}}\right) = \\ &= -\frac{U_{th}}{R_2} \left(1 - e^{-\frac{t}{\tau}}\right) \end{aligned}$$

$$\begin{aligned} U_L(t) &= L \frac{di_L(t)}{dt} = +L \cdot \frac{U_{th}}{R_2} \cdot e^{-\frac{t}{\tau}} \cdot \left(-\frac{1}{\tau}\right) = \\ &= -U_{th} \cdot e^{-\frac{t}{\tau}} \end{aligned}$$


$$U_{\Delta}(t) = U + U_L = \boxed{U - U_{th} \cdot e^{-\frac{t}{\tau}} [V]}$$

$$\begin{aligned} P_2(t) &= i_L(t) \cdot U_L(t) = -\frac{U_{th}}{R_2} \left(1 - e^{-\frac{t}{\tau}}\right) \cdot \left(-U_{th} \cdot e^{-\frac{t}{\tau}}\right) = \\ &= \frac{U_{th}^2}{R_2} \cdot e^{-\frac{t}{\tau}} \left(1 - e^{-\frac{t}{\tau}}\right) \end{aligned}$$

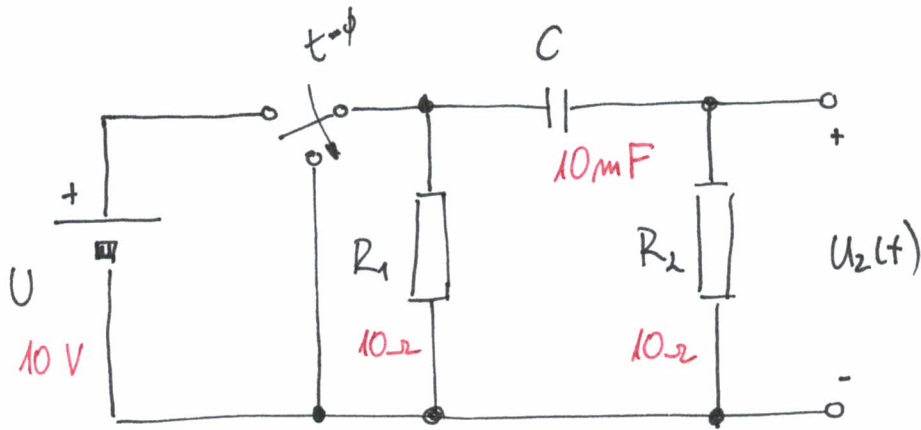Pneralni pojavi - dobovite napetost  $U_2(t)$  po sklenitvi stizala prouti masi




$t = \phi^-$

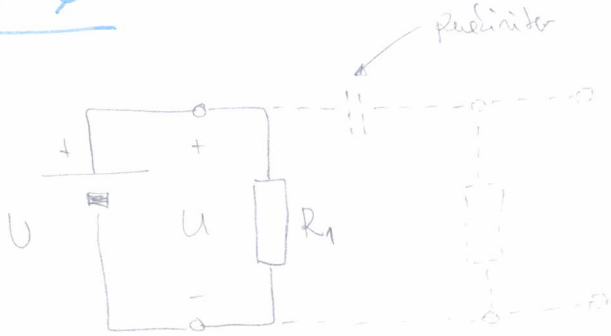


$$U_C(\phi^-) = U \xrightarrow{\mathcal{L}} U_C(p) = U \cdot \frac{1}{p}$$

$t = \phi^+$

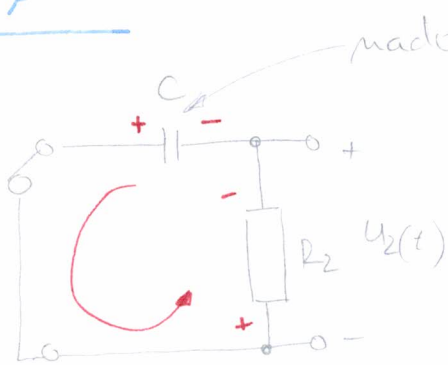

nadomestimo z modelom

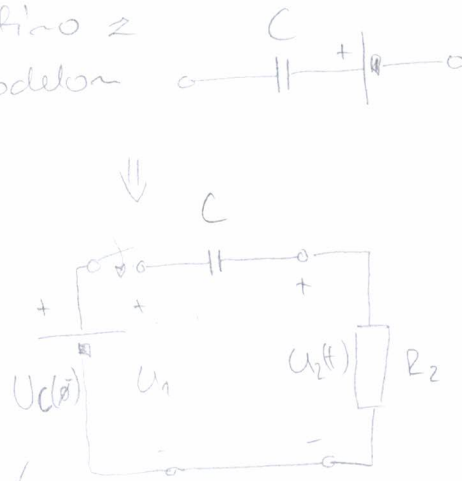

$$H(p) = \frac{U_2(p)}{U_1(p)} =$$

$$= \frac{R_2}{\frac{1}{pC} + R_2} = \frac{pR_2C}{pR_2C + 1}$$

$$U_C(p) = \frac{U_C}{p}$$

$$U_2(p) = H(p) \cdot U_1(p) = \frac{U_C}{p} \cdot \frac{pR_2C}{pR_2C + 1} = U_C \cdot \frac{1}{p + \frac{1}{R_2C}}$$

$$= U_C \cdot \frac{1}{p + a} \Big|_{F(p)} \Big|_{F(t)} \frac{1}{p+a} \Big| e^{-at}$$

$$U_2(t) = U_C \cdot e^{-\frac{t}{R_2C}} \quad \tau = R_2C$$

$$= \boxed{U_C e^{-\frac{t}{\tau}}}$$

$$U_c(t) = U_c(\infty) - U_2(t) = U_c(\infty) - U_c(\infty) \cdot e^{-\frac{t}{\tau}} =$$

$$= \boxed{U_c(\infty) \left(1 - e^{-\frac{t}{\tau}}\right)}$$

$$U_{\text{sup.}}(t) = U_c(\infty) \cdot e^{-\frac{t}{\tau}}$$