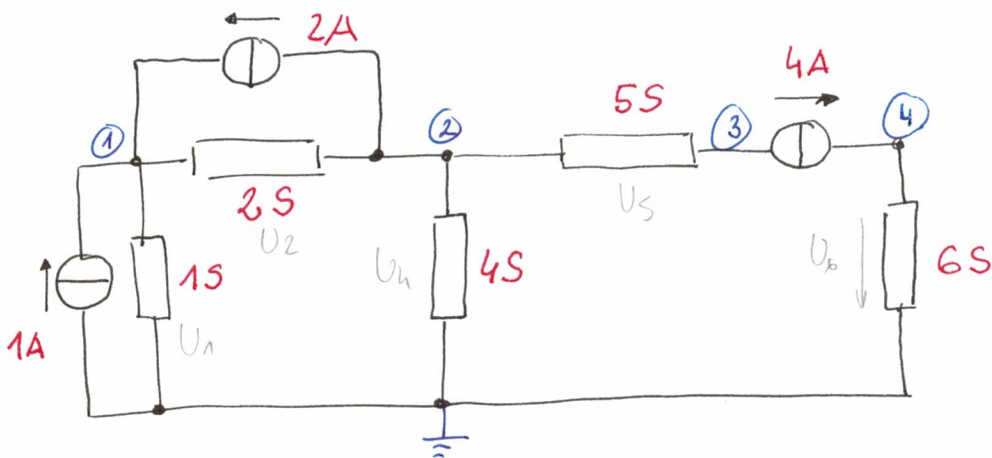


VOZLIŠČNA METODA



$$[I] = [Y] \cdot [U]$$

$$[Y] = \begin{bmatrix} 1+2 & -2 & \emptyset & \emptyset \\ -2 & 2+4+5 & -5 & \emptyset \\ \emptyset & -5 & 5 & \emptyset \\ \emptyset & \emptyset & \emptyset & 6 \end{bmatrix}$$

$$[I] = \begin{bmatrix} 1+2 \\ -2 \\ -4 \\ 4 \end{bmatrix}$$

Tok, ki teče v vozlišče ima predznak +

$$U_1 = 0,429V$$

$$U_2 = \frac{1}{2} \cdot 2A = 1V$$





$$U_4 = -0,857V$$

$$U_5 =$$

$$U_6 = 0,666V$$

$$I = Yx \Rightarrow x = Y^{-1}I$$
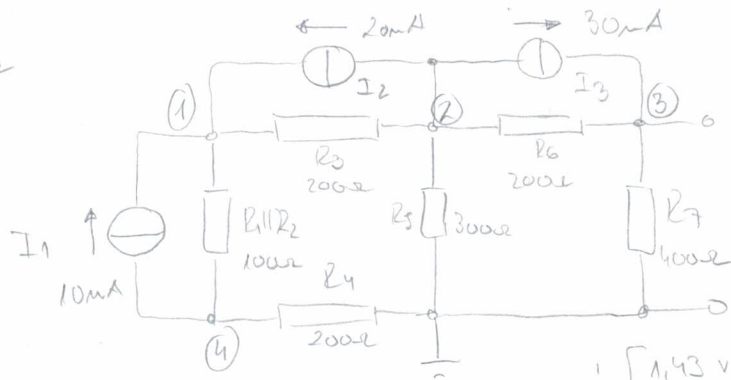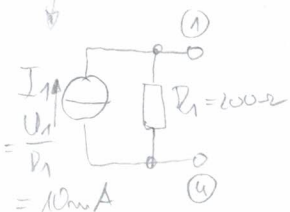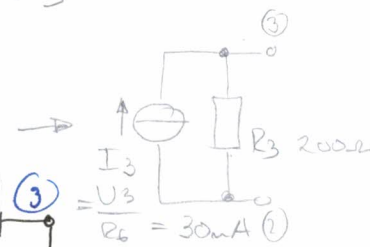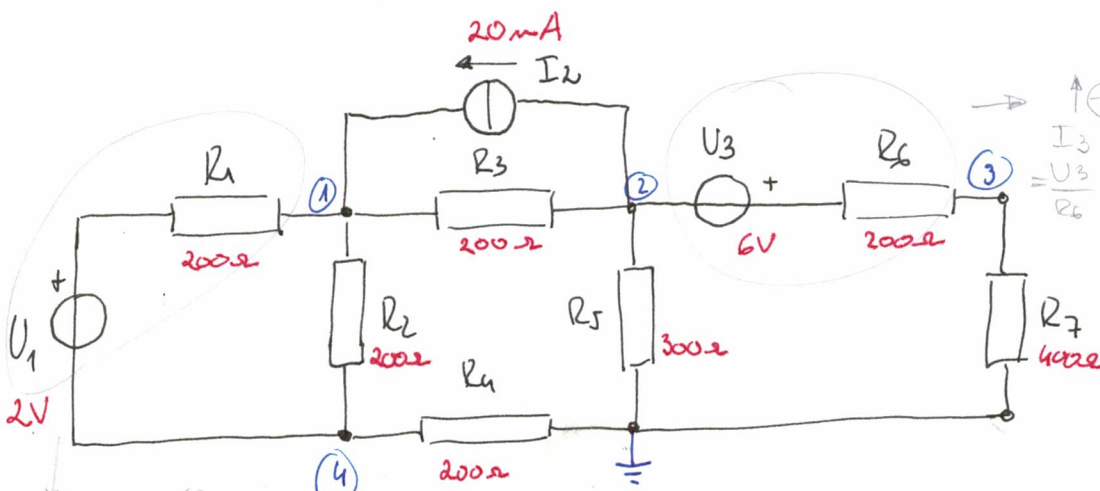
$$x = \begin{bmatrix} 0,429 \\ -0,857 \\ -1,657 \\ 0,666 \end{bmatrix} [V]$$




$U_{R7} = ?$

$$[Y] = \begin{bmatrix} 0,015 & -0,015 & \emptyset & -0,01 \\ -0,015 & 0,015+0,003 & -0,015 & \emptyset \\ \emptyset & -0,015 & 0,015 & \emptyset \\ -0,01 & \emptyset & \emptyset & 0,015 \end{bmatrix}$$

$$[I] = \begin{bmatrix} 30mA \\ -50mA \\ 30mA \\ -10mA \end{bmatrix}$$

$$U_{R7} = 2,48V$$
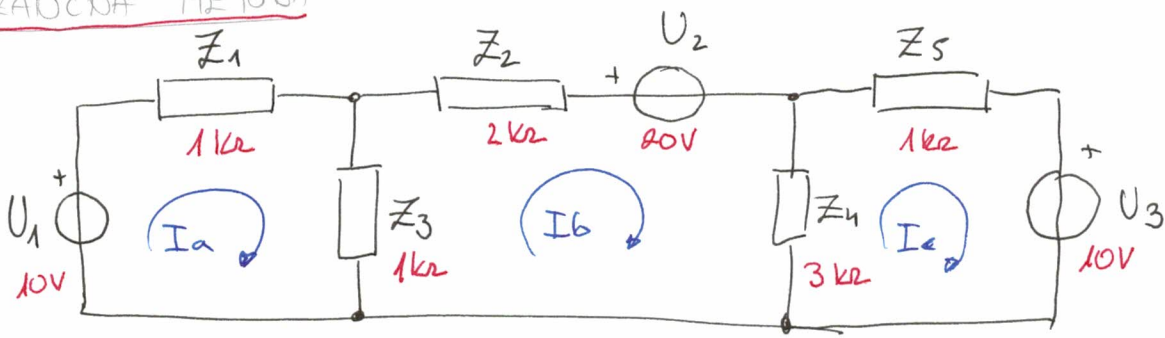
$$[U] = \begin{bmatrix} 1,43V \\ -2,29V \\ 2,48V \\ 0,25V \end{bmatrix}$$



$$I_a(Z_1 + Z_3) - I_b Z_3 + \emptyset = U_1$$

$$-I_a Z_3 + I_b(Z_3 + Z_2 + Z_4) - I_c Z_4 = -U_2$$

$$\emptyset - I_b Z_4 + I_c(Z_5 + Z_4) = -U_3$$

$\begin{bmatrix} 2k & -1k & \emptyset \\ Z_1+Z_3 & -Z_3 & \emptyset \\ -Z_3 & Z_2+Z_3+Z_4 & -Z_4 \\ -1k & 6k & -3k \\ \emptyset & -Z_4 & Z_4+Z_5 \\ & -3k & 4k \end{bmatrix}$	x	$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} U_1 \\ -U_2 \\ -U_3 \end{bmatrix}$
A		B

$$U_1 = I_a \cdot Z_1 = \boxed{1,53V}$$


$$U_2 = (I_a - I_b) \cdot Z_3 = \boxed{8,46V}$$

$$U_2 = I_b \cdot Z_2 = \boxed{-13,85V}$$

$$U_4 = (I_b - I_c) \cdot Z_4 = \boxed{2,31V}$$

$$U_5 = I_c \cdot Z_5 = \boxed{-7,69V}$$
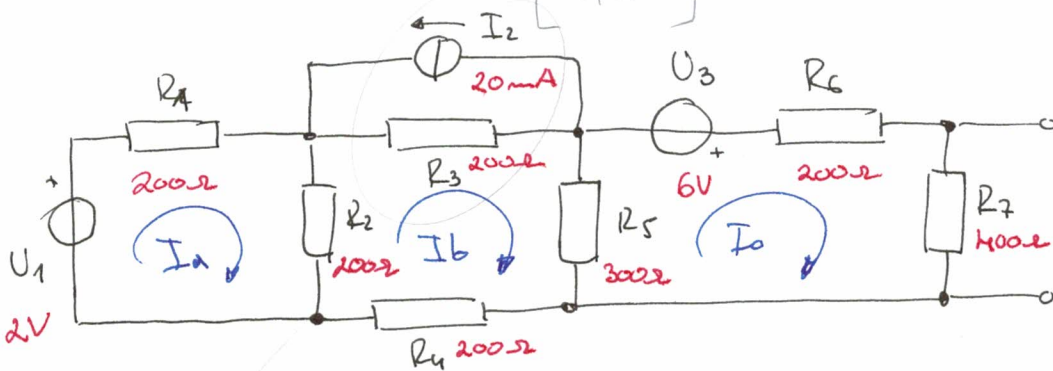
$$X = A^{-1}B = \begin{bmatrix} 1,53 \cdot 10^{-3} \\ -6,92 \cdot 10^{-3} \\ -7,69 \cdot 10^{-3} \end{bmatrix}$$



$$I_a(R_2 + R_4) - I_b R_2 + \emptyset = U_1$$

$$-I_a R_2 + I_b(R_2 + R_3 + R_4 + R_5) - I_c R_5 = -U_2$$

$$\emptyset - I_b R_5 + I_c(R_5 + R_6 + R_7) = U_3$$







$\begin{bmatrix} 400 & -200 & \emptyset \\ R_1+R_2 & -R_2 & \emptyset \\ -200 & R_2+R_3+R_4+R_5 & -R_5 \\ \emptyset & -R_5 & R_5+R_6+R_7 \end{bmatrix}$	x	$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} U_1 \\ -U_2 \\ U_3 \end{bmatrix}$
A		B

$$I_a = 4,051 \text{ mA}$$

$$I_b = -1,899 \text{ mA}$$

$$I_c = 4,937 \text{ mA}$$
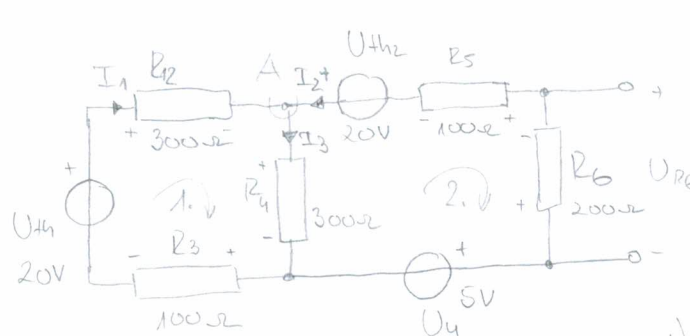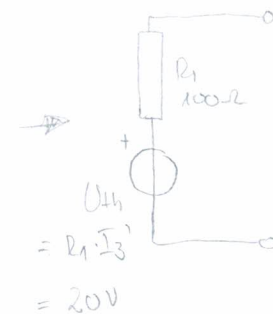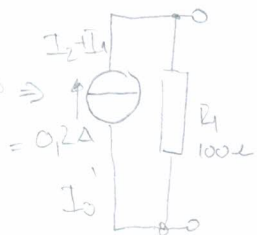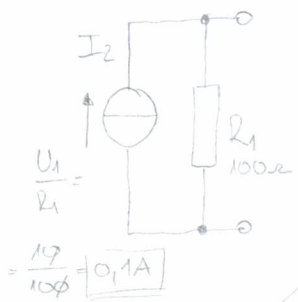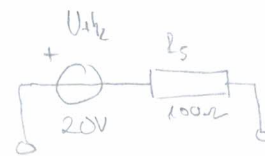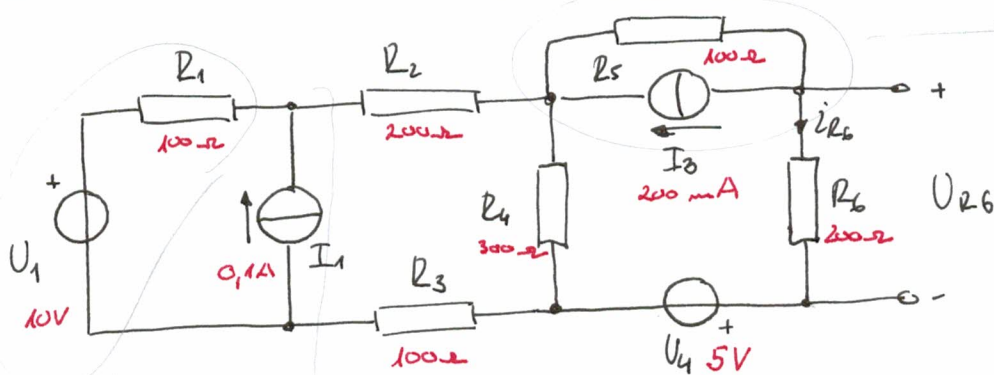
$$U_{R7} = I_c \cdot R_7 = \boxed{1,975V}$$



$$1.) -U_{th} + I_1(R_{12} + R_3) + I_3 R_4 = 0$$

$$2.) U_{th2} - I_2(R_5 + R_6) - I_3 R_4 + U_4 = 0$$

$$A.) I_3 - I_1 - I_2 = 0$$

$$1.) \Rightarrow I_1 = \frac{20 - I_2 \cdot 300}{R_{12} + R_3} = 18,18 \text{ mA}$$

$$2.) \Rightarrow I_2 = \frac{U_{th2} + U_4 - I_3 R_4}{R_5 + R_6} = 34,85 \text{ mA} = I_{R_6}$$

$$U_{R_6} = I_2 \cdot R_6 = 34,85 \text{ mA} \cdot 200 \Omega = 6,97 \text{ V}$$

$$= -6,97 \text{ V}$$


Ja jeste u drugo smer

$$I_3 = \left(\frac{U_{th} - I_2 R_4}{R_{12} + R_3} \right) - \left(\frac{U_{th2} + U_4 - I_3 R_4}{R_5 + R_6} \right) = 0$$



$$I_3 \left(1 + \frac{R_4}{R_{12} + R_3} + \frac{R_4}{R_5 + R_6} \right) = \frac{U_{th}}{R_{12} + R_3} + \frac{U_{th} + U_4}{R_5 + R_6}$$

$$I_3 = 48,49 \text{ mA}$$

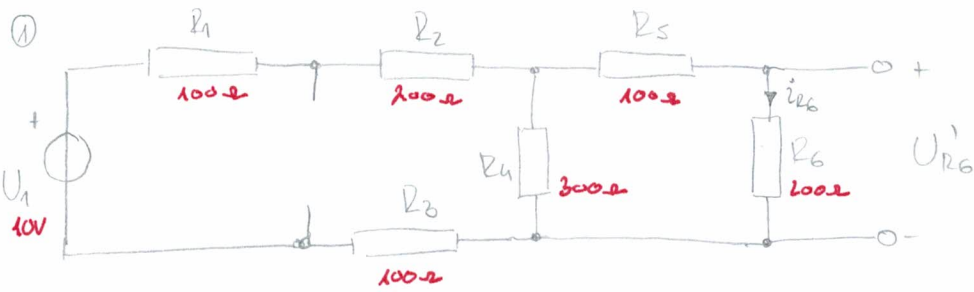
$$P_{RC} = I_{R_6} \cdot U_{R_6} = 0,253 \text{ W}$$


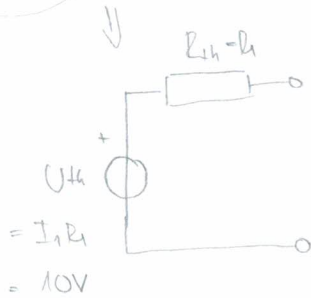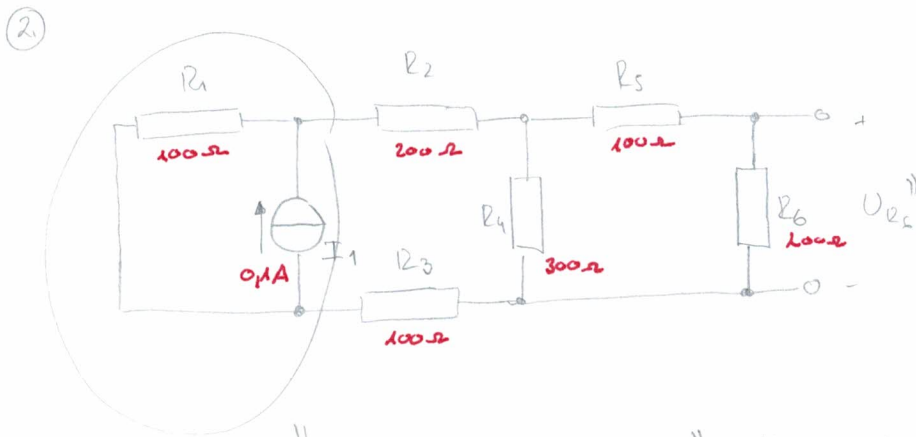
$$U'_{R6} = \frac{U_1 \cdot R_4 \parallel (R_5 + R_6) \cdot R_6}{(R_1 + R_2 + R_3 + R_4 \parallel (R_5 + R_6)) \cdot (R_5 + R_6)} = \frac{10V \cdot 150\Omega \cdot 200\Omega}{550\Omega \cdot 300\Omega} = \boxed{1,82 V}$$



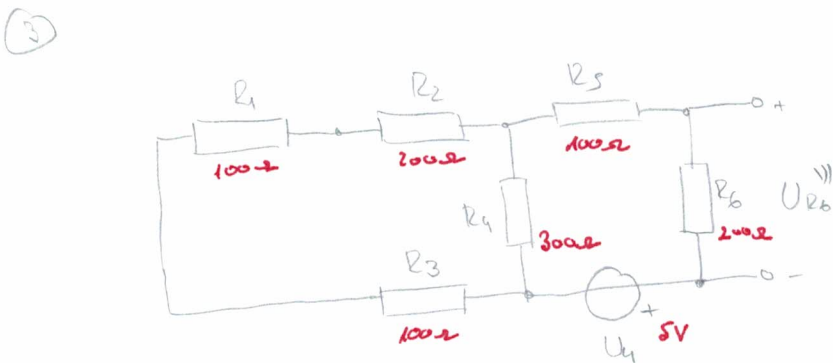
$$U''_{R6} = \frac{U_{th} \cdot R_4 \parallel (R_5 + R_6) \cdot R_6}{R_1 + R_2 + R_3 + R_4 \parallel (R_5 + R_6)} = \boxed{1,82 V}$$



$$U'''_{R6} = \frac{-U_4 \cdot R_6}{(R_1 + R_2 + R_3) \parallel R_4 + R_5 + R_6} = \boxed{-2,12 V}$$

6

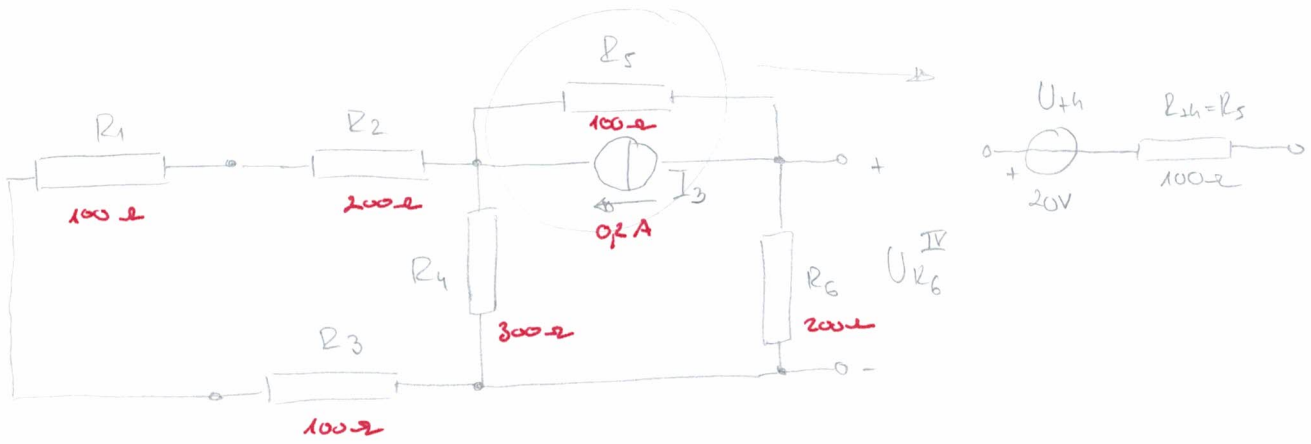

$$U_{R_6}^{IV} = \frac{-U_{th} \cdot R_6}{(R_1 + R_2 + R_3) \parallel R_4 + R_5 + R_6} = \boxed{-8,49 \text{ V}}$$

$$U_{R_6} = U_{R_6}^I + U_{R_6}^{II} + U_{R_6}^{III} + U_{R_6}^{IV}$$








$$= 1,82 \text{ V} + 1,82 \text{ V} - 2,12 \text{ V} - 8,49 \text{ V}$$

$$= \boxed{-6,97 \text{ V}}$$

$$I_{R_6} = \frac{U_{R_6}}{R_6} = \boxed{34,85 \text{ mA}}$$

$$P_{R_6} = I_{R_6} \cdot U_{R_6} = \boxed{0,243 \text{ W}}$$

po Theveninovem teoremu

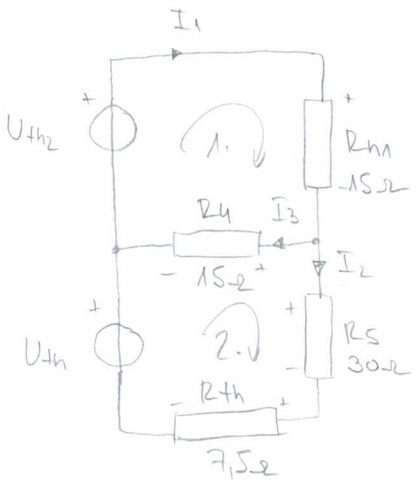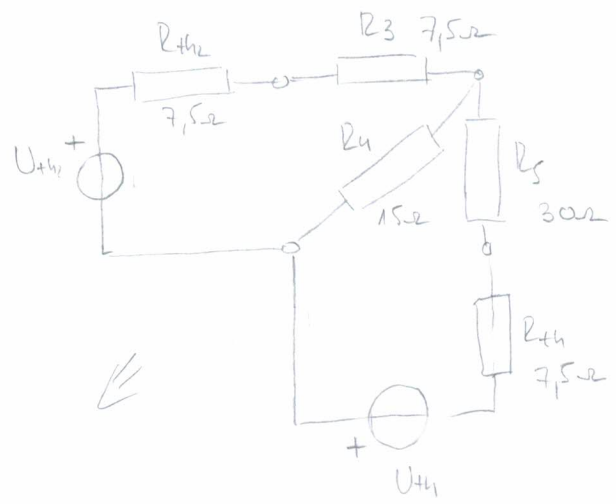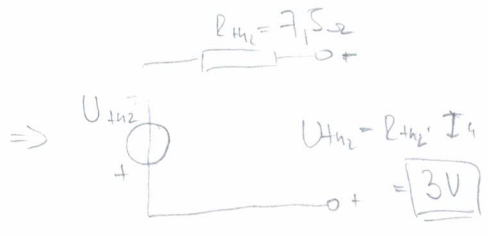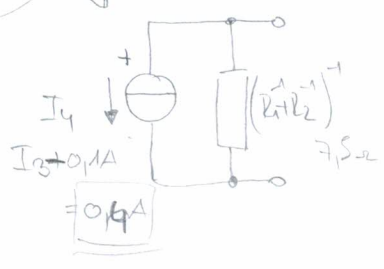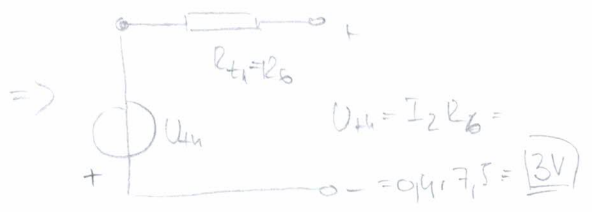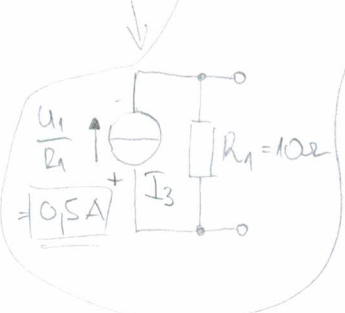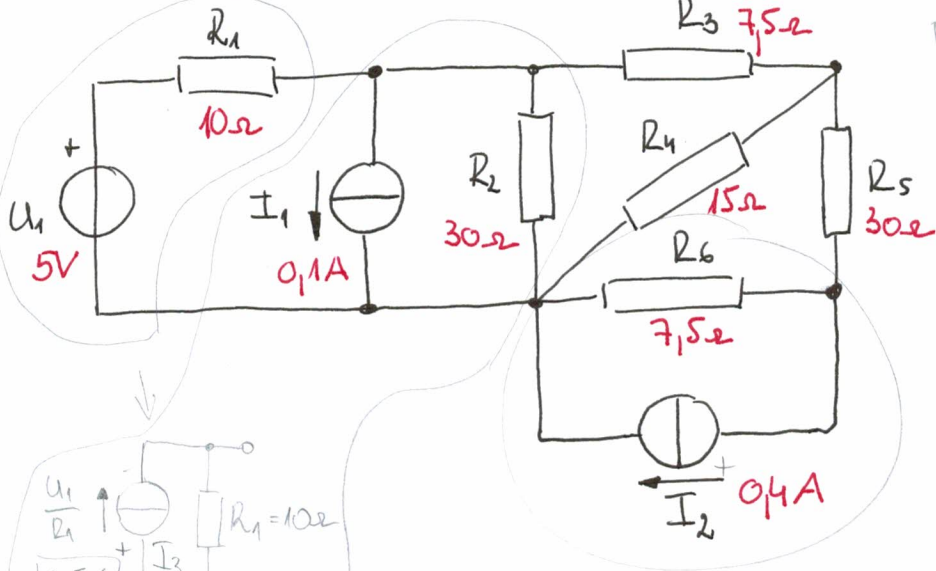

$$1.) -U_{th2} + I_1 R_{th1} + I_3 R_4 = 0 \Rightarrow I_1 = \frac{U_{th2} - I_3 R_4}{R_{th1}} = 0.15A$$

$$2.) -U_{th1} + I_2 (R_5 + R_{th1}) - I_3 R_4 = 0 \Rightarrow I_2 = \frac{U_{th1} + I_3 R_4}{R_5 + R_{th1}} = 0.1A$$


$$A.) I_2 - I_1 + I_3 = 0$$

$$U_{R5} = R_5 \cdot I_2 = 30\Omega \cdot 0.1A = 3V$$

$$P_{R5} = U_{R5} \cdot I_2 = 3V \cdot 0.1A = 0.3W$$


$$\frac{+U_{th1} + I_3 R_4}{R_5 + R_{th1}} + \frac{-U_{th2} + I_3 R_4}{R_{th1}} - I_3 = 0$$
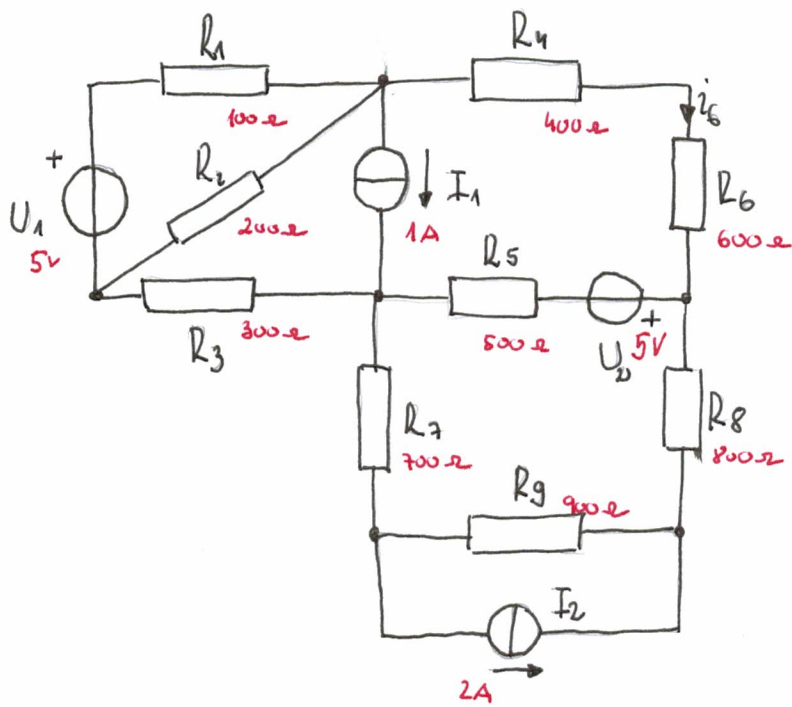
$$I_3 \left(\frac{R_4}{R_5 + R_{th1}} + \frac{R_4}{R_{th1}} + 1 \right) = \frac{+U_{th2}}{R_{th1}} - \frac{U_{th1}}{R_5 + R_{th1}}$$



$i_6 = ?$
 $U_{R6} = ?$
 $P_{R6} = ?$


U_2^I

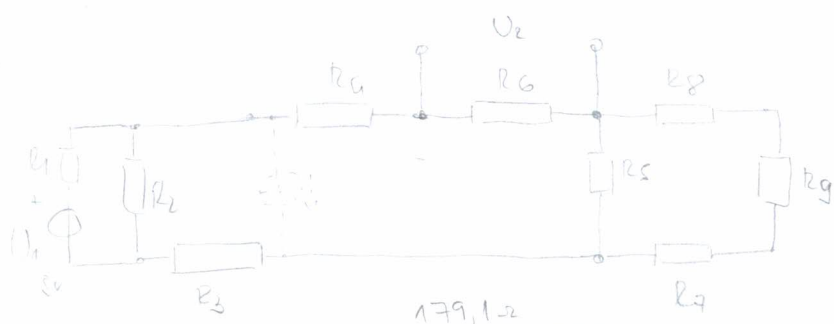


$$U_2^I = \frac{5V \cdot R_2 \parallel (R_4 + R_6 + R_3 + R_5 \parallel (R_8 + R_7 + R_9)) \cdot R_6}{R_1 + (R_2 \parallel (R_4 + R_6 + R_3 + R_5 \parallel (R_8 + R_7 + R_9))) \cdot (R_4 + R_6 + R_3 + R_5 \parallel (R_8 + R_7 + R_9))} = \boxed{1,123V}$$

Handwritten calculations for the denominator:
 $R_8 + R_7 + R_9 = 2400$
 $R_5 \parallel 2400 = 1137,9$
 $R_4 + R_6 + R_3 + 1137,9 = 1713,79$
 $R_2 \parallel 1713,79 = 179,1$
 $R_1 + 179,1 = 279,1$

U_2^{II}

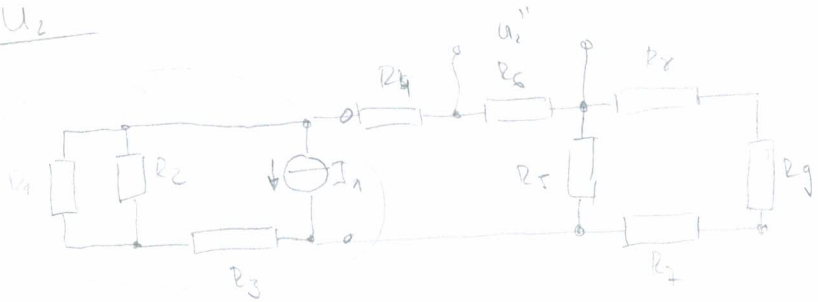


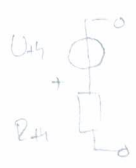$U_{R4} = R_4 \cdot I_1 = 366,67V$
 $R_{eq} = R_3 + R_2 \parallel R_4 = 366,67\Omega$




$$U_2^{II} = \frac{-U_{R4} \cdot R_6}{R_{eq} + R_4 + R_6 + R_5 \parallel (R_7 + R_8 + R_9)} = \boxed{-123,56V}$$

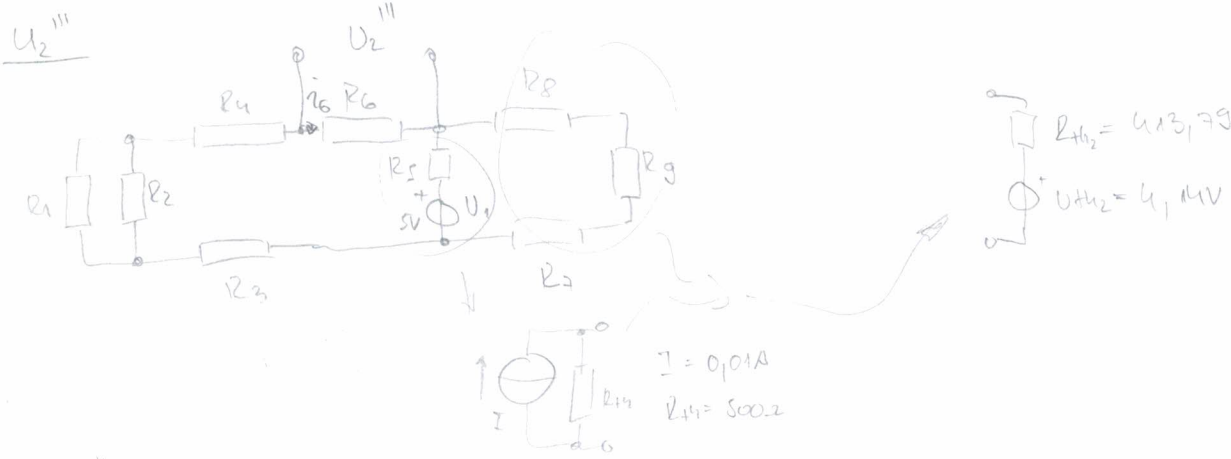Handwritten calculations for the denominator:
 $R_7 + R_8 + R_9 = 2400$
 $R_5 \parallel 2400 = 1137,9$
 $R_{eq} + R_4 + R_6 + 1137,9 = 1780,46\Omega$



$$U_2^{III} = \frac{-U_{Th2} \cdot R_5}{R_{Th2} + R_6 + R_5 + R_3 + R_1 \parallel R_2} = \boxed{-1,39 \text{ V}}$$

1780,959

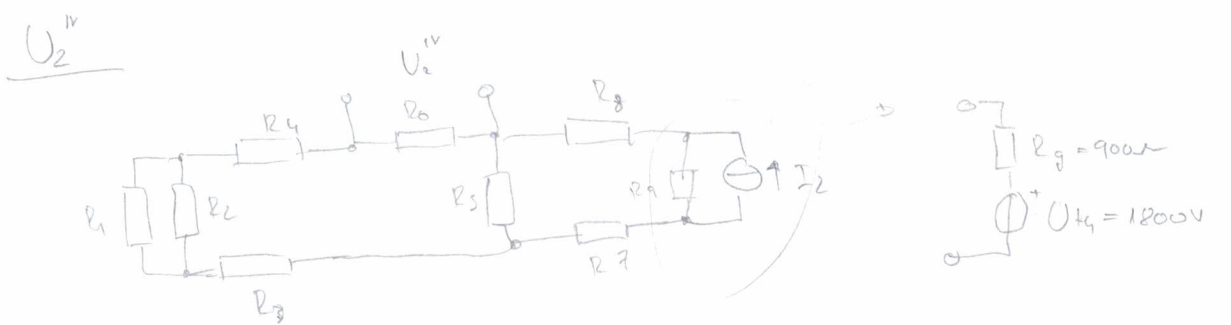

$$U_2^{IV} = \frac{U_{Th} \cdot R_5 \parallel (R_1 \parallel R_2 + R_3 + R_4 + R_6) \cdot R_6}{((R_1 \parallel R_2 + R_3 + R_4 + R_6) \parallel R_5 + R_8 + R_7 + R_9) \cdot (R_6 + R_4 + R_3 + R_1 \parallel R_2)} = \boxed{-104,58 \text{ V}}$$

366,07 2400 1366,67

1366,67 366,07

2766,072

$$U_{R6} = U_2^I + U_2^{II} + U_2^{III} + U_2^{IV} =$$

$$= 1,123 \text{ V} - 123,56 \text{ V} + 1,39 \text{ V} - 104,58 \text{ V} =$$

$$= \boxed{-228,407 \text{ V}}$$

$$P_{R6} = i_{k6} \cdot U_{R6} = \boxed{86,95 \text{ W}}$$

$$i_{k6} = \frac{U_{R6}}{R_6} = \boxed{-0,381 \text{ A}}$$