

$$U_g(t) = 10V \cdot \sin(\omega t)$$

$$f = 1 \text{ kHz}$$

$$U_2, H(j\omega), |H(j\omega)|$$

$$H(j\omega) = \frac{U_2(j\omega)}{U_1(j\omega)} = \frac{I(j\omega) \cdot j\omega C_2}{I(j\omega) \cdot (R_1 + \frac{1}{j\omega C_2})} = \frac{1}{1 + j\omega R_1 C_2}$$

$$= \frac{1 - j\omega R_1 C_2}{1 + (\omega R_1 C_2)^2}$$

$$|H(j\omega)| = \sqrt{\left(\frac{1}{1 + (\omega R_1 C_2)^2}\right)^2 + \left(\frac{-j\omega R_1 C_2}{1 + (\omega R_1 C_2)^2}\right)^2}$$

$$= \sqrt{\frac{1 + (\omega R_1 C_2)^2}{(1 + (\omega R_1 C_2)^2)^2}} = \frac{1}{\sqrt{1 + (\omega R_1 C_2)^2}}$$

$$\text{ang } \varphi = \frac{\text{Im}\{H(j\omega)\}}{\text{Re}\{H(j\omega)\}} = \frac{\frac{-j\omega R_1 C_2}{1 + (\omega R_1 C_2)^2}}{\frac{1}{1 + (\omega R_1 C_2)^2}} = -j\omega R_1 C_2$$


$$\Rightarrow -\text{ang } \varphi(\omega R_1 C_2) = \boxed{-\text{ang } \varphi(2\pi f R_1 C_2)}$$

$$\omega = 2\pi f$$

$$\omega_1 = \frac{1}{R_1 C_2} = \boxed{1 \cdot 10^4 \left[\frac{\text{rad}}{\text{s}}\right]}$$

$$f_1 = \frac{\omega_1}{2\pi} = \frac{1 \cdot 10^4}{2\pi} = \boxed{1591,55 \text{ Hz}}$$

für ω_1

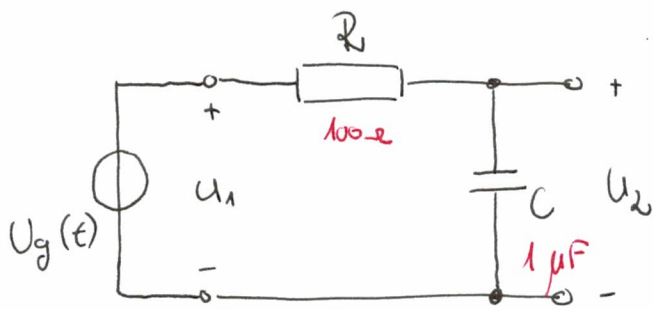

$$U_g(t) = 10V \cdot \sin(\omega t)$$

$$f = 1 \text{ kHz}$$

U_2

$H(j\omega)$

$|H(j\omega)|$

$$H(j\omega) = \frac{U_2(j\omega)}{U_1(j\omega)}$$

$$\frac{U_2(j\omega)}{U_1(j\omega)} = \frac{I(j\omega) \cdot \frac{1}{j\omega C}}{I(j\omega) \cdot (R + \frac{1}{j\omega C})} = \frac{\frac{1}{j\omega C}}{j\omega RC + 1} = \frac{1}{j\omega RC + 1} = \boxed{\frac{1 - j\omega RC}{1 + (\omega RC)^2}}$$

$$|H(j\omega)| = \sqrt{\text{Im}^2(H(j\omega)) + \text{Re}^2(H(j\omega))}$$


$$= \sqrt{\left(\frac{1}{1 + (\omega RC)^2}\right)^2 + \left(\frac{-j\omega RC}{1 + (\omega RC)^2}\right)^2} = \sqrt{\frac{1 + (\omega RC)^2}{(1 + (\omega RC)^2)^2}} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$= \boxed{\frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_1}\right)^2}}}$$

$$\frac{1}{RC} = \omega_1$$

$$\varphi = \arctan \frac{\text{Im}\{H(j\omega)\}}{\text{Re}\{H(j\omega)\}} = \arctan \frac{\frac{-j\omega RC}{1 + (\omega RC)^2}}{\frac{1}{1 + (\omega RC)^2}} = \arctan(-j\omega RC) = \boxed{-\arctan(\omega RC)}$$
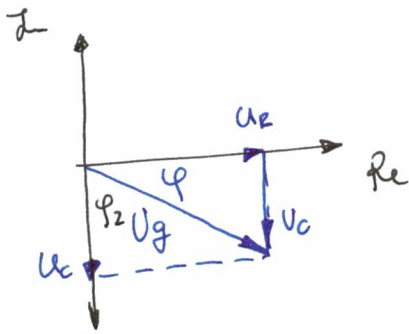
$$\omega = 2\pi f = 2\pi \cdot 1000 \text{ Hz} = \underline{\underline{6283,185 \frac{\text{rad}}{\text{s}}}}$$




$$U_L = U_C = \sin \varphi_2 \cdot U_g$$

$$\varphi = -\arctan(\omega RC) = \underline{\underline{-32,14^\circ}}$$

$$\varphi_2 = 90^\circ - \varphi = \underline{\underline{57,86^\circ}}$$

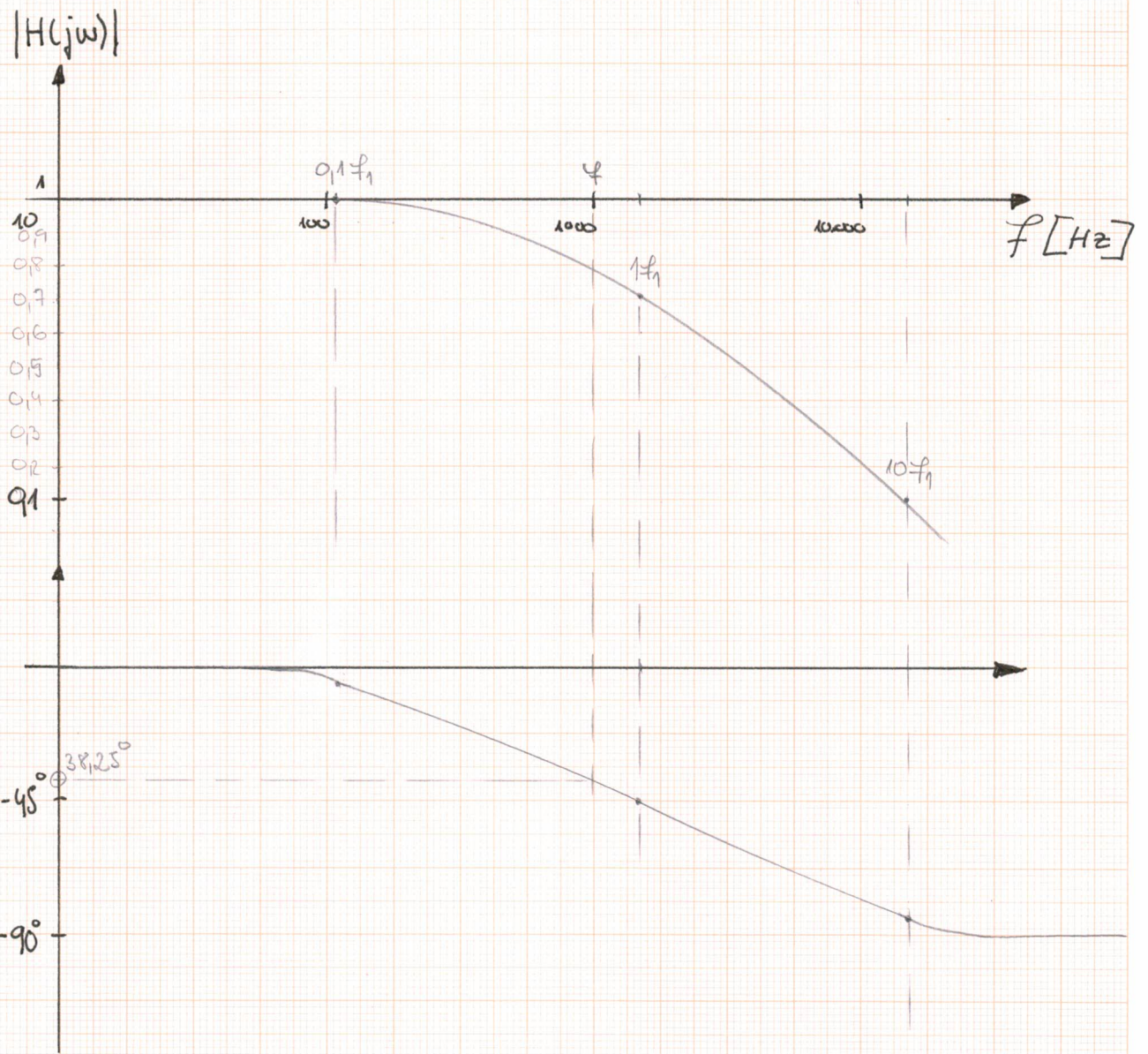
$$U_C = \underbrace{\sin \varphi}_{0,532} \cdot U_g = \underline{\underline{5,32 \text{ V} \cdot \sin(\omega t)}}$$



$\frac{f}{f_1} = \frac{\omega}{\omega_1}$	$ H(j\omega) $	$-\arctan\left(\frac{\omega}{\omega_1}\right)$
$f = 0,1 f_1$	0,1	$-5,71^\circ$
$f = f_1$	1	-45°
$f = 10 f_1$	10	$-84,35^\circ$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_1}\right)^2}}$$
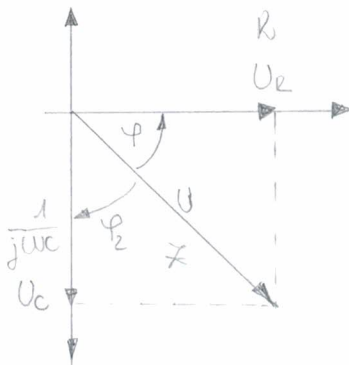
$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi \cdot 1000 \text{ Hz} \cdot 1 \cdot 10^{-6} \text{ F}} = \boxed{159,16 \Omega}$$



$$U_2 = U_C$$


$$\varphi = \arctan\left(\frac{\frac{1}{j\omega C}}{R_1}\right) = \arctan\left(\frac{159,16 \Omega}{100 \Omega}\right) = 57,86^\circ$$

$$\varphi_2 = 90 - \varphi = \boxed{32,14^\circ}$$

$$U_2 = U_C = \underbrace{\sin \varphi_2}_{0,53} \cdot U_g$$

$$U_g(t) = 10 \text{ V} \cdot \sin(\omega t)$$
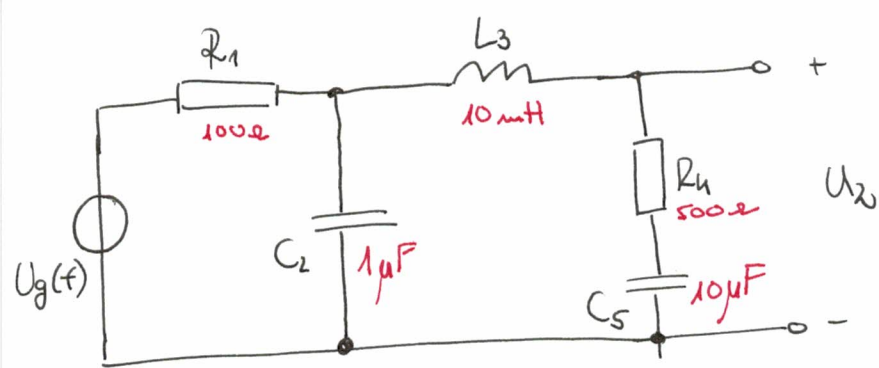
$$\boxed{U_2(t) = 5,32 \cdot \sin(\omega t) \text{ V}}$$



$$U_g(t) = 10V \cdot \sin(2\pi \cdot 1 \text{ kHz} \cdot t)$$

$$H(j\omega) = \frac{U_2(j\omega)}{U_g(j\omega)}$$

$H(j\omega)$, $|H(j\omega)|$, φ

$$U_2(j\omega) = \frac{U_g(j\omega) \cdot \frac{1}{j\omega C_2} \parallel (j\omega L_3 + R_4 + \frac{1}{j\omega C_5}) \cdot (R_4 + \frac{1}{j\omega C_5})}{(R_1 + \frac{1}{j\omega C_2} \parallel (j\omega L_3 + R_4 + \frac{1}{j\omega C_5})) \cdot (j\omega L_3 + R_4 + \frac{1}{j\omega C_5})}$$

$\frac{1}{j\omega C_2} = -j159,16 \Omega$
 $\frac{1}{j\omega C_5} = -j15,92 \Omega$
 $500 + j46,92 \Omega$
 $500 - j15,92 \Omega$
 $500 + j46,92 \Omega$
 $500 + j46,92 \Omega$
 $48,23 - j148,33 \Omega$
 $148,23 - j148,33$


$$\frac{U_2(j\omega)}{U_g(j\omega)} = \frac{(48,23 - j148,33) \cdot (500 - j15,92)}{(148,23 - j148,33) \cdot (500 + j46,92)} = \frac{21753,59 - j74932,82}{81074,64 - j67210,64} =$$


$$= \boxed{(0,61 - j0,42)}$$

$$U_2(j\omega) = H(j\omega) \cdot U_g(j\omega)$$

$$= (0,61 - j0,42) \cdot 10V$$
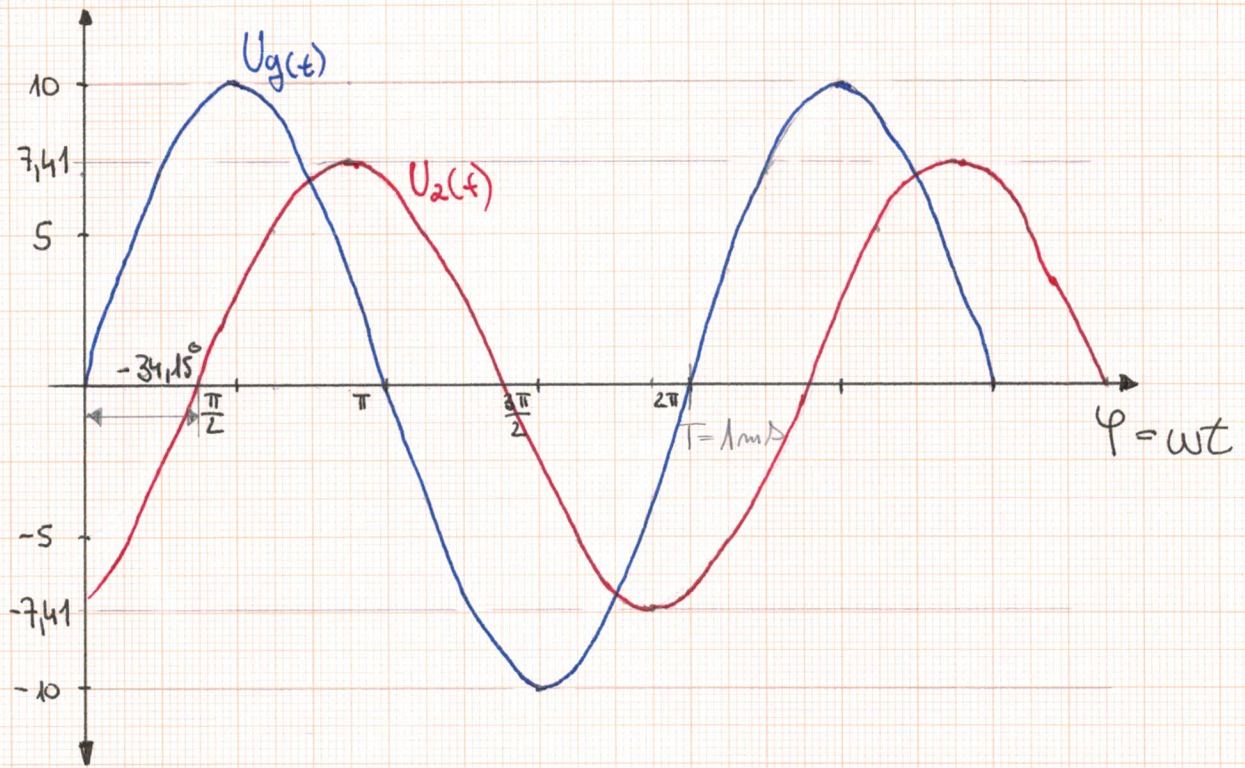
$$= 6,1 - j4,2 = \boxed{7,41 \cdot e^{-j34,15^\circ}}$$



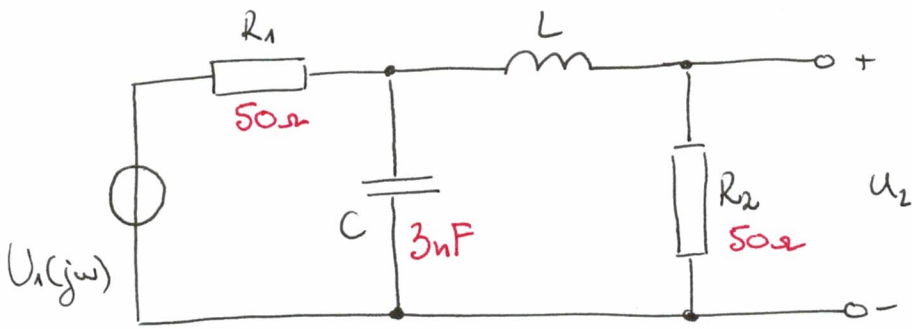

S tuljivo L kompenzira
 fazni pomeš v
 rezju.

$$U_1(t) = 10V \cdot \sin(2\pi \cdot 1MHz \cdot t)$$

$$H(j\omega) = \frac{U_2(j\omega)}{U_1(j\omega)}$$

$$U_2(j\omega) = \frac{U_1(j\omega) \cdot \frac{1}{j\omega C} \parallel (j\omega L + R_2) \cdot R_2}{\left(R_1 + \frac{1}{j\omega C} \parallel (j\omega L + R_2) \right) \cdot (j\omega L + R_2)}$$

$$\frac{U_2(j\omega)}{U_1(j\omega)} = \frac{j\omega C \cdot (j\omega L + R_2) \cdot R_2}{R_1 + \frac{1}{j\omega C} \cdot (j\omega L + R_2)^2} = \frac{R_2 \cdot j\omega C \cdot (j\omega L + R_2)}{R_1 \left(\frac{1}{j\omega C} + j\omega L + R_2 \right) + \frac{1}{j\omega C} \cdot (j\omega L + R_2)^2}$$

$$= \frac{R_2 \cdot \frac{1}{j\omega C} \cdot (j\omega L + R_2)}{(j\omega L + R_2) \cdot \left(R_1 \left(\frac{1}{j\omega C \cdot (j\omega L + R_2)} + 1 \right) + \frac{1}{j\omega C} \cdot (j\omega L + R_2) \right)}$$

$$= \frac{R_2 \cdot \frac{1}{j\omega C}}{\frac{1}{j\omega C} \cdot \left(\left(\frac{R_1}{j\omega L + R_2} + j\omega C \right) + (j\omega L + R_2) \right)} = \frac{R_2}{1} \cdot \frac{R_1 - \omega^2 LC + j\omega C R_2 + (j\omega L + R_2)^2}{j\omega L + R_2}$$

$$= \frac{j\omega L R_2 + R_2^2}{R_1 - \omega^2 LC + j\omega C R_2 - \omega^2 L^2 + 2j\omega L R_2 + R_2^2} = \frac{j\omega L R_2 + R_2}{(R_1 - \omega^2 LC - \omega^2 L^2 + R_2^2) + j(\omega C R_2 + 2\omega L R_2)}$$

$$= \frac{(j\omega L R_2 + R_2) \cdot (-j(\omega C R_2 + 2\omega L R_2))}{(R_1 - \omega^2 LC - \omega^2 L^2 + R_2^2)^2 + (\omega C R_2 + 2\omega L R_2)^2}$$

$$\text{Im}\{H(j\omega)\} = 0$$

$$\frac{\underbrace{-0,943}_{- \omega C R_2} \cdot \underbrace{-200 \omega L}_{- 2\omega L R_2}}{(R_1 - \omega^2 LC - \omega^2 L^2 + R_2^2)^2 + (\omega C R_2 + 2\omega L R_2)^2} = 0 \quad / \cdot (\text{inmemorable})$$

$$-0,943 - 200 \omega L = 0$$

$$L = \frac{0,943}{-200 \omega} = \frac{0,943}{-1256,64 \cdot 1 \cdot 10^6} = -750 \cdot 10^{-12}$$

$$= -75 \text{ pH}$$