

① $U_g - i_1 R_g - U_1 = \emptyset$

$U_1 = i_1 \cdot Z_{in1}$

$i_1 = \frac{U_1}{Z_{in1}}$

$U_g - \frac{U_1 R_g}{Z_{in1}} - U_1 = \emptyset$

$-U_1 \left(\frac{R_g}{Z_{in1}} + 1 \right) = -U_g$

$U_1 = \frac{U_g Z_{in1}}{R_g + Z_{in1}}$

② $A_{u1} U_1 - Z_{in2} i_2 - U_2 = \emptyset$

$i_2 = \frac{U_2}{Z_{in2}}$

$\frac{A_{u1} U_g Z_{in1}}{R_g + Z_{in1}} - \frac{U_2 Z_{in2}}{Z_{in2}} - U_2 = \emptyset$

$U_2 \left(\frac{Z_{in2} + Z_{in2}}{Z_{in2}} \right) = \frac{A_{u1} U_g Z_{in1}}{R_g + Z_{in1}}$

$U_2 = \frac{A_{u1} U_g Z_{in1}}{R_g + Z_{in1}} \cdot \frac{Z_{in2}}{Z_{in2} + Z_{in2}}$

③ $A_{u2} U_2 - i_3 Z_{in2} - U_3 = \emptyset$

$U_3 = i_3 \cdot R_b \Rightarrow i_3 = \frac{U_3}{R_b}$

$A_{u2} U_2 - \frac{U_3 Z_{in2}}{R_b} - U_3 = \emptyset$


$U_3 = \frac{R_b A_{u2} U_2}{Z_{in2} + R_b}$

$U_3 = \frac{R_b A_{u2}}{Z_{in2} + R_b} \cdot \frac{A_{u1} U_g Z_{in1}}{R_g + Z_{in1}} \cdot \frac{Z_{in2}}{Z_{in2} + Z_{in2}} \quad /: U_g$

$A_{uv} = \frac{U_3}{U_g}$

$\frac{U_3}{U_g} = A_{u1} \cdot A_{u2} \cdot \frac{R_b}{R_b + Z_{in2}} \cdot \frac{Z_{in1}}{Z_{in1} + R_g} \cdot \frac{Z_{in2}}{Z_{in2} + Z_{in2}}$

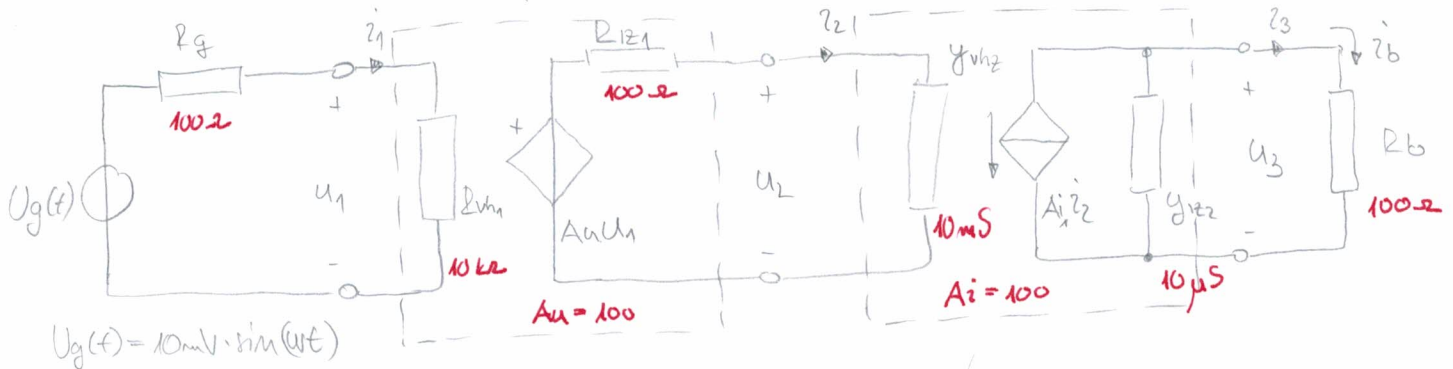$= 20 \cdot 10 \cdot \frac{100 \Omega}{100 \Omega + 50 \Omega} \cdot \frac{100 k\Omega}{100 k\Omega + 50 \Omega} \cdot \frac{100 k\Omega}{100 k\Omega + 50 \Omega} = \boxed{133,2}$



$$U_g(t) = 10 \text{ mV} \cdot \sin(\omega t)$$

$$A_p = A_i \cdot A_u \quad f = 10 \text{ kHz}$$

$$A_{iV} = \frac{i_3}{i_1}$$

$$A_{uV} = \frac{U_3}{U_g} = \frac{U_3}{U_2} \cdot \frac{U_2}{U_1} \cdot \frac{U_1}{U_g}$$

$$U_g = i_1 R_g + i_1 R_{L1}$$

$$U_1 = i_1 R_{L1}$$

$$U_1 = \frac{U_g R_{L1}}{R_g + R_{L1}}$$

$$A_u U_1 - i_2 R_{L1} - i_2 Z_{vh2} = 0$$

$$U_2 = i_2 \cdot Z_{vh2}$$

$$U_2 = \frac{A_u U_1 Z_{vh2}}{R_{L1} + Z_{vh2}}$$

$$[Y] = \begin{bmatrix} 10 \text{ mS} & \emptyset \\ 100 & 10 \mu\text{S} \end{bmatrix} \rightarrow [Z] = \begin{bmatrix} 100 \Omega & \emptyset \\ 100 \text{ k}\Omega & -1 \cdot 10^3 \Omega \end{bmatrix}$$

$$\Delta Y = 0,11 \mu\text{S}^2$$

$$A_i i_2 \cdot Z_{vh2} - i_3 R_L = 0$$

$$U_3 = i_3 R_L$$

$$U_3 = \frac{A_i i_2 \cdot Z_{vh2} R_L}{R_L}$$

$$U_3 = -A_i i_2 \cdot \frac{1}{y_{vh2}} \parallel R_L$$

$$-9881$$

$$U_3 = A_u \cdot U_g$$


$$= -9881 \cdot 10 \text{ mV} \cdot \sin \omega t$$


$$= -98,81 \sin \omega t \text{ V}$$

$$i_b = \frac{U_3}{R_L} = -0,9887 \text{ A} \sin \omega t$$

$$P_{RO} = U_3 \cdot i_b = 97,63 \text{ W} \sin^2 \omega t$$
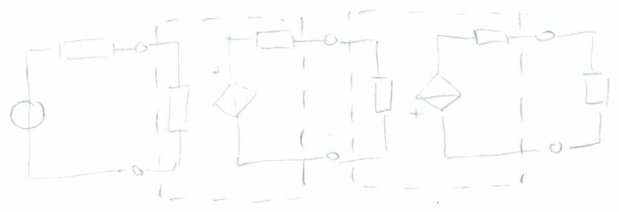
$$P_{RL} = U_{eff} \cdot I_{eff} = \frac{U_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = \frac{U_m I_m}{2}$$



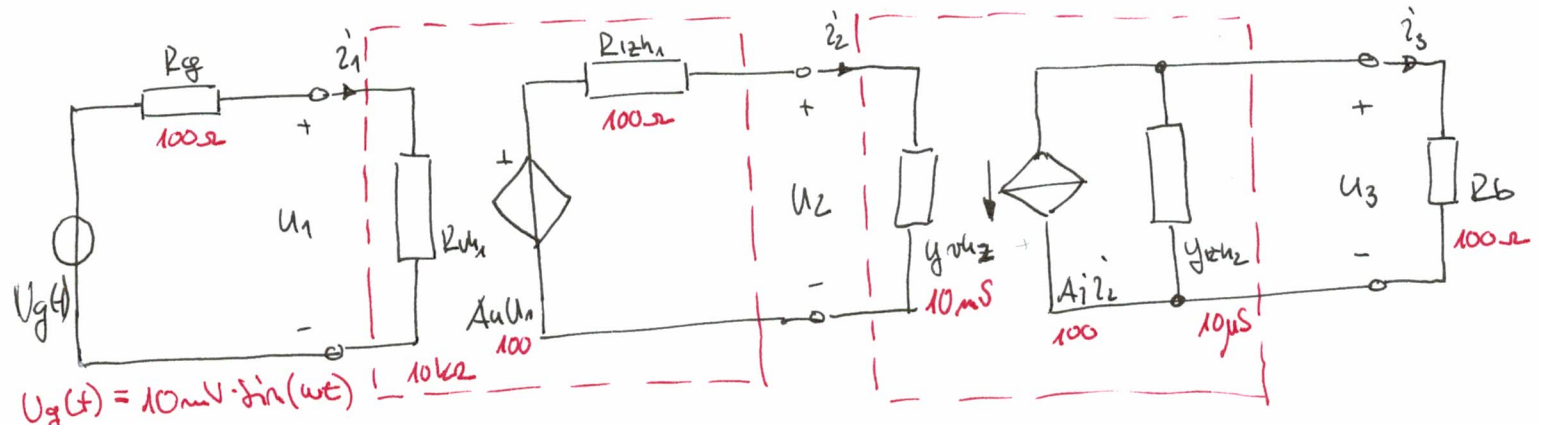

$U_g(t) = 10 \text{ mV} \cdot \sin(\omega t)$
 $f = 10 \text{ kHz}$

① $U_g - i_1 R_g - U_1 = 0$
 $U_1 = i_1 R_{uhn}$

② $A_u U_1 - i_2 R_{1zh1} - U_2 = 0$
 $U_2 = i_2 \cdot \frac{1}{y_{ohz}}$

③ $U_3 = -A_i i_2 \cdot \frac{1}{\frac{1}{y_{ohz}} \parallel R_b}$

$U_g - \frac{R_g U_1}{R_{uhn}} - U_1 = 0$

$i_2 = \frac{A_u U_1}{R_{1zh1} + \frac{1}{y_{ohz}}}$

$U_3 = -A_i A_u \cdot \frac{y_{ohz}}{R_{1zh1} y_{ohz} + 1} \cdot \frac{U_g R_{uhn}}{R_g + R_{uhn}}$

$U_1 \left(\frac{R_g + R_{uhn}}{R_{uhn}} \right) = U_g$

$i_2 = \frac{A_u U_1 y_{ohz}}{R_{1zh1} y_{ohz} + 1}$

$\frac{1}{\frac{1}{y_{ohz}} \parallel R_b} = \frac{1}{\frac{1}{y_{ohz}} + \frac{1}{R_b}}$

$U_1 = \frac{U_g R_{uhn}}{R_g + R_{uhn}}$

$i_2 = \frac{A_u y_{ohz}}{R_{1zh1} y_{ohz} + 1} \cdot \frac{U_g R_{uhn}}{R_g + R_{uhn}}$

$\frac{U_{Rb}}{y_{ohz}} = \frac{U_{Rb}}{\frac{1}{1 + R_b y_{ohz}}}$

$A_{uv} = \frac{U_3}{U_g(t)}$

$\frac{U_3}{U_g} = -A_i A_u \cdot \frac{y_{ohz}}{R_{1zh1} y_{ohz} + 1} \cdot \frac{R_{uhn}}{R_g + R_{uhn}} \cdot \frac{R_b}{R_b y_{ohz} + 1}$

$= -100 \cdot 100 \cdot \frac{10 \text{ mS}}{100 \Omega \cdot 10 \text{ mS} + 1} \cdot \frac{10 \text{ k}\Omega}{100 \Omega + 10 \text{ k}\Omega} \cdot \frac{100 \Omega}{100 \Omega \cdot 10 \mu\text{S} + 1} = -4945,55$

$U_3 = A_u \cdot U_g$
 $= [-49,46 \cdot \sin(\omega t)] \text{ [V]}$

$i_b = \frac{U_3}{R_b} = [-0,495 \cdot \sin(\omega t)] \text{ [A]}$

$P_{Rb} = U_3 \cdot i_b = [24,46 \sin^2(\omega t)] \text{ [W]}$

