

$$i_1 = i_{1a} = i_{1b}$$

$$U_2 = U_{2a} = U_{2b} \quad \text{Skupne neličine}$$

$$U_1 = U_{1a} + U_{1b}$$

$$i_2 = i_{2a} + i_{2b}$$

enačice

$$U_1 = h_{11}i_1 + h_{12}U_2$$

$$i_2 = h_{21}i_1 + h_{22}U_2$$

$$[H_A] = \begin{bmatrix} 4,5k\Omega & 2 \cdot 10^{-4} \\ 330 & 30\mu S \end{bmatrix}$$


$$[H_B] =$$

$$h_{11b} = \frac{U_{1b}}{i_{1b}} \Big|_{U_{2b}=\varnothing} = \frac{i_{2b} \cdot (R_1 + R_2 \parallel R_3)}{i_{1b}} = \boxed{199\Omega}$$

$$h_{12b} = \frac{U_{1b}}{U_{2b}} \Big|_{i_{1b}=\varnothing} = \frac{U_{2b} \cdot R_3}{R_2 + R_3} \cdot \frac{1}{U_{2b}} = \boxed{9,9 \cdot 10^{-3}}$$

$$h_{21b} = \frac{i_{2b}}{i_{1b}} \Big|_{U_{2b}=\varnothing} = \frac{-i_{1b} \cdot R_2 \parallel R_3}{R_2} = \boxed{-9,9 \cdot 10^{-3}}$$

$$h_{22b} = \frac{i_{2b}}{U_{2b}} \Big|_{i_{1b}=\varnothing} = \frac{i_{1b}}{i_{1b} \cdot (R_2 + R_3)} = 99 \cdot 10^{-6} S = \boxed{99\mu S}$$

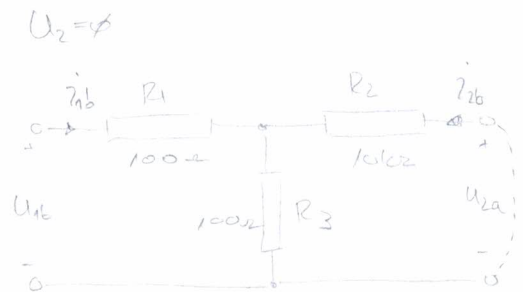

Brez P. V.

S P.V.

$$Z_{in} = \frac{h_{11} + \Delta H_a Z_b}{1 + h_{22} Z_b} = \frac{4,5 \text{ k}\Omega + 0,069 \cdot 10 \text{ k}\Omega}{1 + 30 \mu\text{S} \cdot 10 \text{ k}\Omega} = 3,992 \text{ k}\Omega = -9,935 \text{ k}\Omega$$

$$Z_{12} = \frac{h_{11} + Z_g}{\Delta H_a + h_{22} Z_g} = \frac{4,5 \text{ k}\Omega + 1 \text{ k}\Omega}{0,069 + 30 \mu\text{S} \cdot 1 \text{ k}\Omega} = 55,56 \text{ k}\Omega = -2,154 \text{ k}\Omega$$

$$A_u = \frac{-h_{21} Z_b}{h_{11} + \Delta H_a Z_b} = \frac{-330 \cdot 10 \text{ k}\Omega}{4,5 \text{ k}\Omega + 0,069 \cdot 10 \text{ k}\Omega} = -635,84 = 145$$

$$A_i = \frac{h_{21}}{1 + h_{22} Z_b} = \frac{330}{1 + 30 \mu\text{S} \cdot 10 \text{ k}\Omega} = 253,85 = 144$$

$$A_g = \frac{h_{21}}{h_{11} + \Delta H_a Z_b} = \frac{330}{4,5 \text{ k}\Omega + 0,069 \cdot 10 \text{ k}\Omega} = 63,58 \text{ mS} = -14,5 \text{ mS}$$

$$A_v = \frac{-h_{21} Z_b}{1 + h_{22} Z_b} = \frac{-330 \cdot 10 \text{ k}\Omega}{1 + 330 \cdot 10 \text{ k}\Omega} = -2,54 \text{ M}\Omega = -1,44 \text{ M}\Omega$$


$$A_p = A_u \cdot A_i =$$

$$[H_a] = \begin{bmatrix} 4,5 \text{ k}\Omega & 2 \cdot 10^{-4} \\ 330 & 30 \mu\text{S} \end{bmatrix}$$

$$[H] = [H_a] + [H_b] = \begin{bmatrix} 4,619 \text{ k}\Omega & 10,1 \cdot 10^{-3} \\ 329,99 & 129 \mu\text{S} \end{bmatrix}$$

$$\Delta H_a = 0,069$$

$$\Delta H = -2,737$$

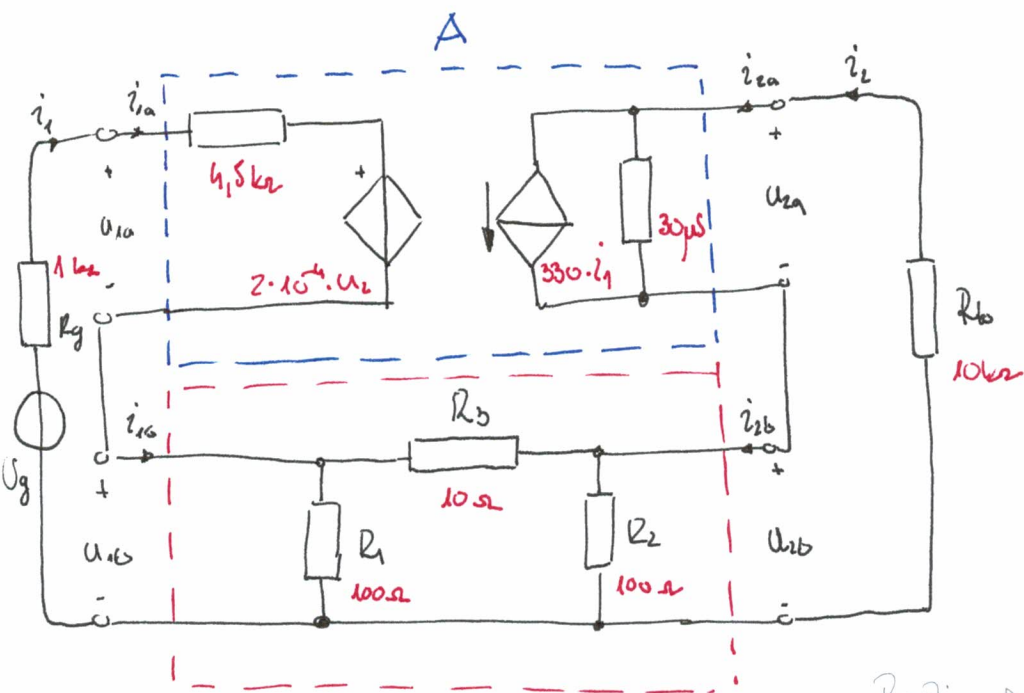

B

$$[H_a] = \begin{bmatrix} 4,5k\Omega & 2 \cdot 10^{-4} \\ 330 & 30\mu S \end{bmatrix} \Rightarrow [Z_a] = \begin{bmatrix} 2,3k\Omega & 6,67\Omega \\ -11M\Omega & 333k\Omega \end{bmatrix}$$


$$\Delta Z_a = 1,5 \cdot 10^8$$

Restri $\rightarrow Z$ parameter

$$[Z_b] =$$

$$U_1 = Z_{11}i_1 + Z_{12}i_2$$

$$U_2 = Z_{21}i_1 + Z_{22}i_2$$

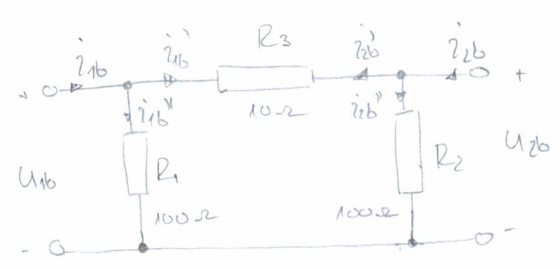

$$Z_{11b} = \left. \frac{U_{1b}}{i_{1b}} \right|_{i_{2b} = \varnothing}$$

$$= \frac{i_{1b} (R_1 \parallel (R_3 + R_2))}{i_{1b}} = 52,38\Omega$$

$$i_{2b}' = \frac{U_{2b}}{R_1 + R_3} \quad i_{2b}'' = \frac{U_{2b}}{R_2}$$

$$U_{1b} = +i_{2b}' \cdot R_1 = \frac{+U_{2b} R_1}{R_1 + R_3}$$

$$i_2 = i_{2b}' + i_{2b}'' = \frac{U_{2b} (R_2 + R_1 + R_3)}{R_2 (R_1 + R_3)}$$

$$Z_{21b} = \left. \frac{U_{1b}}{i_{2b}} \right|_{i_{1b} = \varnothing}$$

$$= \frac{\frac{+U_{2b} R_1}{R_1 + R_3}}{\frac{U_{2b} (R_1 + R_2 + R_3)}{R_2 (R_1 + R_3)}} = \frac{+R_1 R_2}{R_1 + R_2 + R_3} = +47,61\Omega$$

$$i_{1b}' = \frac{U_{1b}}{R_3 + R_2} \quad i_{1b}'' = \frac{U_{1b}}{R_1}$$

$$i_{1b} = \frac{U_{1b} (R_1 + R_2 + R_3)}{R_1 (R_2 + R_3)}$$

$$Z_{22b} = \left. \frac{U_{2b}}{i_{2b}} \right|_{i_{1b} = \varnothing} = \frac{+U_{2b} R_2}{\frac{U_{2b} (R_1 + R_2 + R_3)}{R_1 (R_2 + R_3)}} = \frac{+R_1 R_2}{R_1 + R_2 + R_3} = -47,61\Omega$$

$$U_{2b} = +i_{1b}' \cdot R_2 = + \frac{U_{1b} R_2}{R_2 + R_3}$$

$$Z_{12b} = \left. \frac{U_{2b}}{i_{1b}} \right|_{i_{2b} = \varnothing} = \frac{i_{2b}' (R_1 + R_3) \parallel R_2}{i_{1b}'} = 52,38\Omega$$

$$[Z_b] = \begin{bmatrix} 52,38\Omega & +47,61\Omega \\ +47,61\Omega & 52,38\Omega \end{bmatrix}$$

$$[Z] = [Z_a] + [Z_b] = \begin{bmatrix} 2,352 \text{ k}\Omega & 5428 \Omega \\ -10,99 \text{ M}\Omega & 33,353 \text{ k}\Omega \end{bmatrix}$$

Brez P.V.

S P.V.

$$Z_{uh} = \frac{Z_M Z_0 + \Delta Z}{Z_{22} + Z_0} = \frac{2,3 \text{ k}\Omega \cdot 10 \text{ k}\Omega + 1,5 \cdot 10^8}{33,3 \text{ k}\Omega + 10 \text{ k}\Omega} = 3995 \text{ k}\Omega = 16,12 \text{ k}\Omega$$

$$Z_{12h} = \frac{Z_{22} Z_g + \Delta Z}{Z_M + Z_g} = \frac{33,3 \text{ k}\Omega \cdot 1 \text{ k}\Omega + 1,5 \cdot 10^8}{2,3 \text{ k}\Omega + 1 \text{ k}\Omega} = 55,53 \text{ k}\Omega = 211,5 \text{ k}\Omega$$


$$A_u = \frac{Z_{21} Z_b}{Z_{11} Z_b + \Delta Z} = \frac{-11 \text{ M}\Omega \cdot 10 \text{ k}\Omega}{2,3 \text{ k}\Omega \cdot 10 \text{ k}\Omega + 1,5 \cdot 10^8} = -636 = -157$$

$$A_i = \frac{-Z_{21}}{Z_{22} + Z_b} = \frac{+11 \text{ M}\Omega}{33,3 \text{ k}\Omega + 10 \text{ k}\Omega} = 254 = 254$$

$$A_g = \frac{-Z_{21}}{Z_M Z_b + \Delta Z} = \frac{11 \text{ M}\Omega}{2,3 \text{ k}\Omega \cdot 10 \text{ k}\Omega + 1,5 \cdot 10^8} = 63,6 \text{ m} = 15,74 \text{ m}$$

$$A_v = \frac{Z_{21} Z_b}{Z_{22} + Z_0} = \frac{-11 \text{ M}\Omega \cdot 10 \text{ k}\Omega}{33,3 \text{ k}\Omega + 10 \text{ k}\Omega} = -2,54 \text{ M} = -2,54 \text{ M}$$
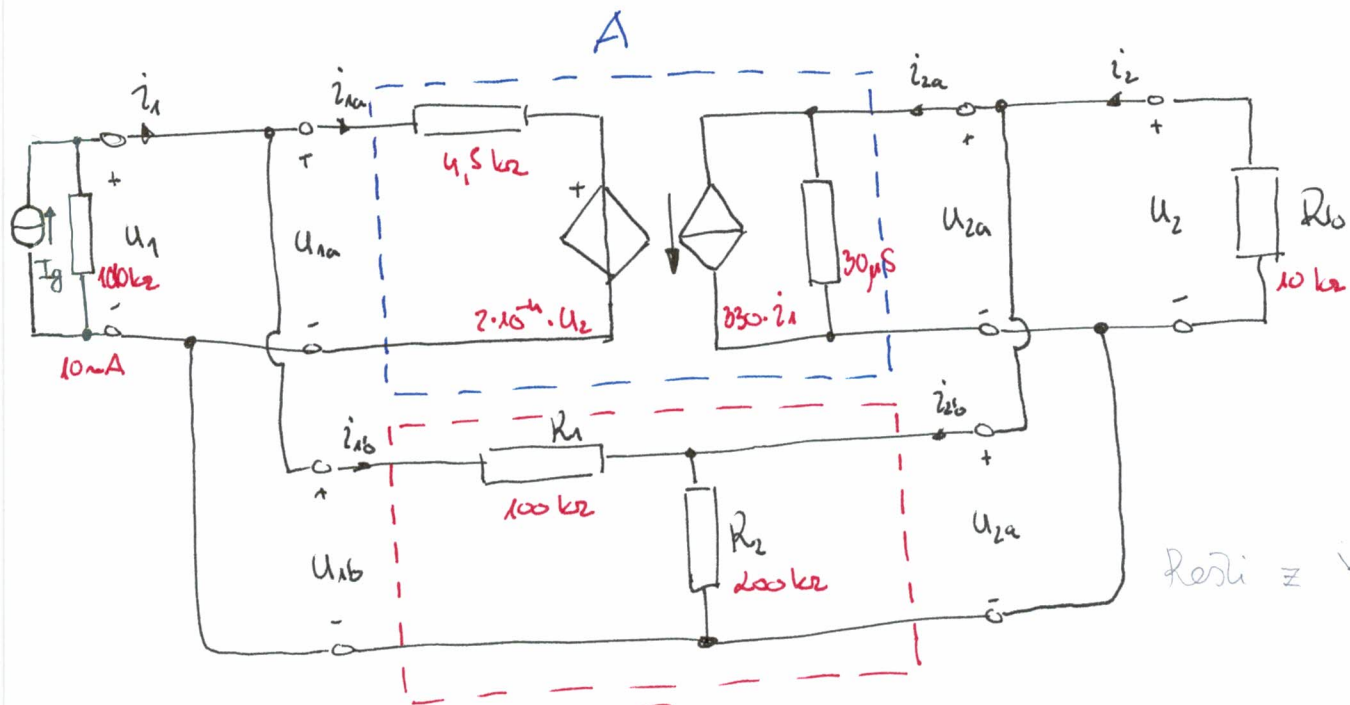
$$A_p = A_u \cdot A_i = -1,62 \cdot 10^5 = -39,93 \cdot 10^5$$



Resti = Y parameterii

$$[h_a] = \begin{bmatrix} 4,5 \text{ k}\Omega & 2 \cdot 10^{-4} \\ 330 & 30 \mu\text{S} \end{bmatrix} \Rightarrow [Y_a] = \begin{bmatrix} 222 \mu\text{S} & -444 \mu\text{S} \\ 73,3 \text{ mS} & 15,3 \mu\text{S} \end{bmatrix}$$


$$\Delta Y_a = 32,5 \mu\text{S}^2$$

$$U_{1a} = U_{1b} = U_1 \quad U_{2a} = U_{2b} = U_2$$

$$i_1 = i_{1a} + i_{1b} \quad i_2 = i_{2a} + i_{2b}$$

$$i_1 = y_{11} U_1 + y_{12} U_2$$

$$i_2 = y_{21} U_1 + y_{22} U_2$$

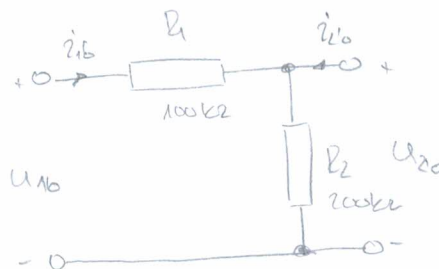

$$y_{11} = \left. \frac{i_{1b}}{U_{1b}} \right|_{U_2 = \emptyset} = \frac{i_{1b}}{i_{1b} \cdot R_1} = \frac{1}{100 \text{ k}\Omega} = 10 \mu\text{S}$$

$$y_{12} = \left. \frac{i_{1b}}{U_{2b}} \right|_{U_1 = \emptyset} = \frac{i_{1b}}{-i_{1b} \cdot R_1} = -10 \mu\text{S}$$

$$y_{21} = \left. \frac{i_{2b}}{U_{1b}} \right|_{U_2 = \emptyset} = \frac{-i_{1b}}{i_{1b} \cdot R_1} = -10 \mu\text{S}$$

$$y_{22} = \left. \frac{i_{2b}}{U_{2b}} \right|_{U_{1b} = \emptyset} = \frac{U_{2b}}{\frac{R_1 \parallel R_2}{U_{2b}}} = \frac{1}{R_1 \parallel R_2} = 15 \mu\text{S}$$

$$[Y_b] = \begin{bmatrix} 10 \mu\text{S} & -10 \mu\text{S} \\ -10 \mu\text{S} & 15 \mu\text{S} \end{bmatrix}$$

$$[Y] = [Y_a] + [Y_b] = \begin{bmatrix} 232 \mu\text{S} & -454 \mu\text{S} \\ 73,29 \text{ mS} & 30,3 \mu\text{S} \end{bmatrix}$$

$$\Delta Y = 32,5 \mu\text{S}^2$$

Brez P.V.

S P.V.

$$Z_{in} = \frac{1 + y_{22} Z_b}{y_m + \Delta y Z_b} = \frac{1 + 30,3 \mu S \cdot 10 k\Omega}{232 \mu S + 32,5 \mu S^2 \cdot 10 k\Omega} = 3,54 \Omega = 4 \Omega$$

$$Z_{izl} = \frac{1 + y_m Z_g}{y_{22} + \Delta y Z_g} = \frac{1 + 232 \mu S \cdot 1 k\Omega}{30,3 \mu S + 32,5 \mu S \cdot 1 k\Omega} = 7,13 \Omega = 7,44 \Omega$$


$$A_u = \frac{-y_{21} Z_b}{1 + y_{22} Z_b} = \frac{-73,29 mS \cdot 10 k\Omega}{1 + 30,3 \mu S \cdot 10 k\Omega} = -636 = -563$$

$$A_i = \frac{y_{21}}{y_m + \Delta y Z_b} = \frac{73,29 mS}{232 \mu S + 32,5 \mu S \cdot 10 k\Omega} = 0,23 = 0,23$$

$$A_g = \frac{y_{21}}{1 + y_{22} Z_b} = \frac{73,29 mS}{1 + 30,3 \mu S \cdot 10 k\Omega} = 63,57 m = 56,25 m$$

$$A_v = \frac{-y_{21} Z_b}{y_m + \Delta y Z_b} = \frac{-73,29 mS \cdot 10 k\Omega}{232 \mu S + 32,5 \mu S \cdot 10 k\Omega} = -2,25 k = -2,25 k$$

$$A_p = A_u \cdot A_i = -143 = -127$$

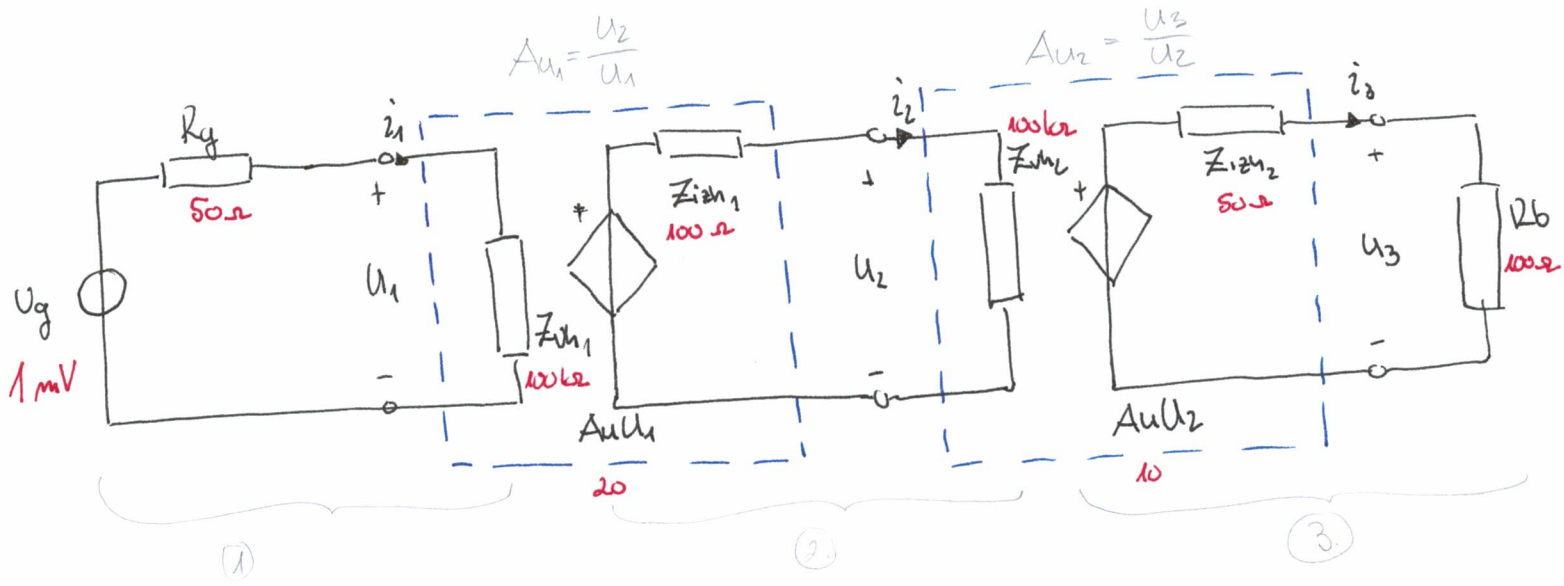

$$U_g - i_1 R_g - i_1 Z_{in1} = 0$$

$$U_1 = i_1 Z_{in1}$$

$$i_1 = \frac{U_g}{R_g + Z_{in1}}$$

$$U_1 = \frac{U_g Z_{in1}}{R_g + Z_{in1}}$$

$$A_{u1} U_1 - i_2 Z_{in2} - i_2 Z_{in2} = 0$$

$$U_2 = i_2 Z_{in2}$$

$$U_2 = \frac{A_{u1} Z_{in2}}{Z_{in2} + Z_{in2}}$$

$$A_{u2} U_2 - i_3 Z_{in2} - i_3 R_b = 0$$

$$U_3 = i_3 R_b$$

$$U_3 = \frac{A_{u2} R_b}{Z_{in2} + R_b}$$


$$A_{uv} = \frac{U_3}{U_g}$$

$$U_3 = \frac{U_g Z_{in1}}{R_g + Z_{in1}} \cdot \frac{A_{u1} Z_{in2}}{Z_{in2} + Z_{in2}} \cdot \frac{A_{u2} R_b}{Z_{in2} + R_b}$$

$$\Rightarrow \frac{U_3}{U_g} = \frac{Z_{in1}}{R_g + Z_{in1}} \cdot \frac{A_{u1} Z_{in2}}{Z_{in2} + Z_{in2}} \cdot \frac{A_{u2} R_b}{Z_{in2} + R_b}$$

$$= \frac{100 \text{ k}\Omega}{50 \Omega + 100 \text{ k}\Omega} \cdot \frac{20 \cdot 100 \text{ k}\Omega}{50 + 100 \text{ k}\Omega} \cdot \frac{10 \cdot 100 \Omega}{50 + 100 \Omega}$$

$$= \underline{\underline{133,2}}$$

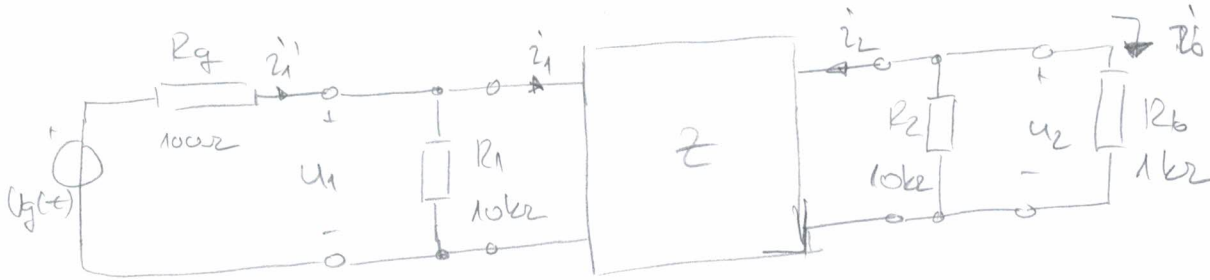

$$A_v = \frac{u_2}{u_1}$$

$$A_i = \frac{i_b}{i_1}$$

$$P_{RB} = ?$$

$$U_g(t) = 10 \text{ mV} \cdot \sin(\omega t)$$

$$f = 1 \text{ kHz}$$

$$[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 2,3 \text{ k}\Omega & \emptyset \\ -11 \text{ M}\Omega & 33,3 \text{ k}\Omega \end{bmatrix}$$


$$U_g - i_1 R_g - u_1 = 0$$

$$u_1 = Z_{11} i_1 + Z_{12} i_2$$

$$u_2 - i_b R_b = 0$$

$$u_2 = Z_{21} i_1 + Z_{22} i_2$$

$$u_2 = -i_2 \cdot (R_2 \parallel R_b)$$

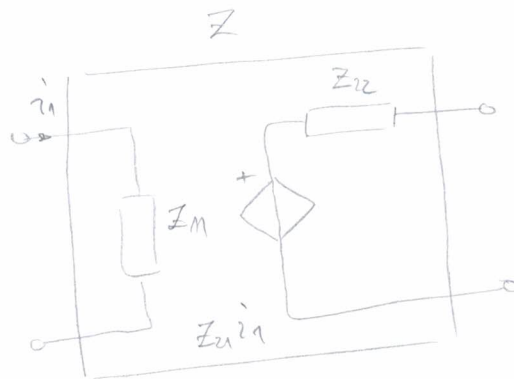

$$i_1 = \frac{u_1}{Z_{11}}$$

$$u_2 = \frac{Z_{21} i_1 \cdot R_2 \parallel R_b}{Z_{22} + R_2 \parallel R_b}$$

$$A_v = \frac{u_2}{u_1} = \frac{Z_{21} R_2 \parallel R_b}{Z_{22} + R_2 \parallel R_b} = -292319$$

$$A_i = \frac{i_b}{i_1} = \frac{u_2}{R_b \cdot i_1} = \frac{A_v}{R_b} = -292319$$

$$P_{RB} = U_{RB} \cdot i_b = i_b^2 \cdot R_b = \boxed{1,46 \text{ mW}} \cdot \sin^2(\omega t) = p_{\text{avg}}$$


$$P = \frac{1}{T} \int_0^T p(t) dt$$

$$u_n = \frac{U_g (R_1 \parallel Z_m)}{R_g + R_1 \parallel Z_m}$$

$$i_b = A_i i_1 = A_i \frac{u_1}{Z_{11}} = \boxed{1,2 \text{ mA}} \cdot \sin(\omega t)$$

$$= \boxed{9,49 \text{ mV}} \sin(\omega t)$$

po metodi superpozicije

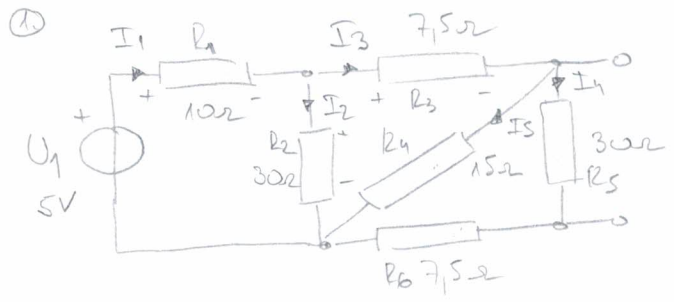


$$I_1 = \frac{U_1}{R_1 + R_2 \parallel (R_3 + R_4 \parallel (R_5 + R_6))} = \frac{5V}{21,33\Omega} = 0,23A$$

$\underbrace{\hspace{10em}}_{37,5}$
 $\underbrace{\hspace{10em}}_{10,71}$
 $\underbrace{\hspace{10em}}_{18,21}$
 $\underbrace{\hspace{10em}}_{11,33}$

$$I_2 = \frac{U_1}{R_2} = \frac{2,66}{30\Omega} = 0,0885A$$

$$I_3 = \frac{U_1}{18,21} = 0,1458A$$

1)

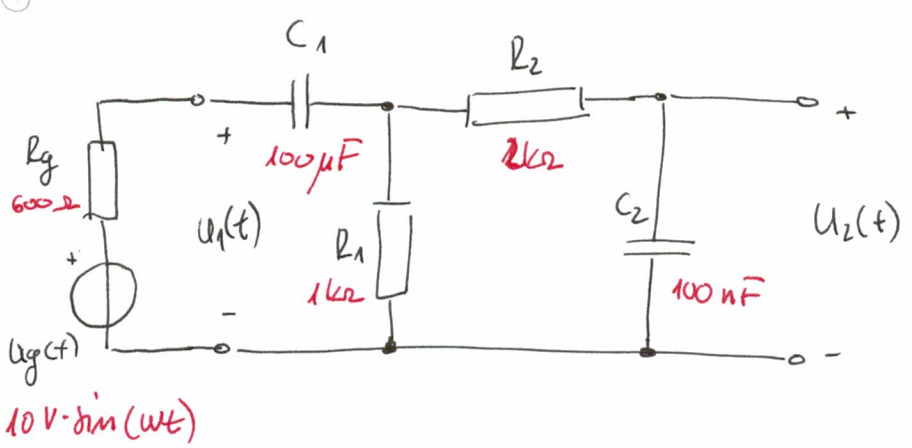

$$H(j\omega) = \frac{U_2(j\omega)}{U_1(j\omega)} = \frac{j\omega R_2 C_2 + 1}{j\omega C_2} \parallel R_1 = \frac{j\omega R_2 C_2 R_1 + R_1}{j\omega R_2 C_2 + 1 + j\omega C_2 R_1}$$

$$U_2(j\omega) = \frac{U_1(j\omega) \cdot R_1 \parallel (R_2 + \frac{1}{j\omega C_2}) \cdot \frac{1}{j\omega C_2}}{\left(\frac{1}{j\omega C_1} + R_1 \parallel (R_2 + \frac{1}{j\omega C_2}) \right) \cdot (R_2 + \frac{1}{j\omega C_2})}$$

$$\Rightarrow \frac{U_2(j\omega)}{U_1(j\omega)} = \frac{\frac{j\omega R_2 C_2 R_1 + R_1}{j\omega C_2 R_2 + 1 + j\omega C_2 R_1} \cdot \frac{1}{j\omega C_2}}{\left(\frac{1}{j\omega C_1} + \frac{j\omega R_2 C_2 R_1 + R_1}{j\omega C_2 R_2 + 1 + j\omega C_2 R_1} \right) \cdot \frac{j\omega R_2 C_2 + 1}{j\omega C_2}}$$

$$= \frac{j\omega R_2 C_2 R_1 + R_1}{j\omega C_2 (j\omega C_2 R_2 + 1 + j\omega C_2 R_1)} \cdot \frac{j\omega C_2}{j\omega C_1 \cdot (j\omega C_2 R_2 + 1 + j\omega C_2 R_1)} = \frac{j\omega R_2 C_2 + 1}{j\omega C_1 \cdot (j\omega C_2 R_2 + 1 + j\omega C_2 R_1)}$$

$$= \frac{R_1 j\omega C_1 (j\omega R_2 C_2 + 1)}{(j\omega C_2 R_2 + 1 + j\omega C_2 R_1 - \omega^2 R_1 R_2 C_2 + j\omega R_1 C_1) \cdot (j\omega R_2 C_2 + 1)}$$

$$= \frac{j\omega C_1 R_1}{j\omega C_1 \left(\frac{C_2 R_2}{C_1} + \frac{1}{j\omega C_1} + \frac{C_2 R_1}{C_1} + j\omega R_1 R_2 C_2 + R_1 \right)} = \frac{R_1}{\left[\frac{C_2 R_2}{C_1} + \frac{C_2 R_1}{C_1} + R_1 \right] + \left[\frac{1}{j\omega C_1} + j\omega R_1 R_2 C_2 \right]}$$

$$= \frac{R_1}{\frac{C_2(R_2 + R_1) + R_1 C_1}{C_1} + \frac{1}{j\omega C_1} + j\omega R_1 R_2 C_2}$$



2.

$$= \frac{R_1}{\left[\frac{C_2(R_1+R_2)+R_1C_1}{C_1} \right]} \cdot \left[1 + \frac{j(\omega R_1 R_2 C_2 - \frac{1}{\omega C_1})}{\frac{C_2(R_1+R_2)+R_1C_1}{C_1}} \right] = \frac{R_1}{\underbrace{\left[\frac{C_2(R_1+R_2)+R_1C_1}{C_1} \right]}_{1003}} \cdot \frac{1}{1 + \frac{jC_1(\omega R_1 R_2 C_2 - \frac{1}{\omega C_1})}{C_2(R_1+R_2)+R_1C_1}} = \frac{1}{\dots}$$

\downarrow
 $\frac{1000}{1003} \approx 1$
 $\dots 9,97$

$$= \frac{jC_1 \left(\frac{\omega^2 R_1 R_2 C_2 - 1}{\omega C_1} \right)}{C_2(R_1+R_2)+R_1C_1} = \frac{jC_1(\omega^2 R_1 R_2 C_2 - 1)}{\omega C_1 (C_2(R_1+R_2)+R_1C_1)} = j \left(\frac{\omega^2 R_1 R_2 C_2}{\omega (C_2(R_1+R_2)+R_1C_1)} - \frac{1}{\omega (C_2(R_1+R_2)+R_1C_1)} \right)$$

$$= \frac{\omega \cdot 2 \cdot 10^{-5}}{0,1003} - \frac{1}{\omega \cdot 0,1003} = \frac{\omega}{5015} - \frac{9,97}{\omega}$$

$$\frac{a \cdot a}{b} = \frac{a}{\frac{a}{b}} \quad \frac{a}{\omega b} = \frac{a}{\omega}$$

$$\frac{1}{1 + j \left(\frac{\omega}{5015} - \frac{9,97}{\omega} \right)}$$

$$C_1 \left(\omega R_1 R_2 C_2 - \frac{1}{\omega C_1} \right) = 0$$

$$\omega R_1 R_2 C_2 - \frac{1}{\omega} = 0$$

$$\omega^2 = R_1 R_2 C_1 C_2$$

$$\omega = \sqrt{R_1 R_2 C_1 C_2}$$

$$\Im \{ H(j\omega) \} = 0$$

$$\frac{\omega}{5015} = \frac{9,97}{\omega}$$

$$\omega^2 = 9,97 \cdot 5015$$

$$\omega_0 = \sqrt{500.00} = 223,61 \left[\frac{\text{rad}}{\text{s}} \right]$$

$$f_0 = \frac{\omega_0}{2\pi} = 35,59 \text{ Hz}$$

3

$$\frac{R_1}{\frac{C_2(R_1+R_2)+R_1C_1}{C_1} + j\left(\omega R_1 R_2 C_2 - \frac{1}{\omega C_1}\right)} = \frac{R_1 \cdot \left[\frac{C_2(R_1+R_2)+R_1C_1}{C_1} - j\left(\omega R_1 R_2 C_2 - \frac{1}{\omega C_1}\right) \right]}{\left(\frac{C_2(R_1+R_2)+R_1C_1}{C_1} \right)^2 + \left(\omega R_1 R_2 C_2 - \frac{1}{\omega C_1} \right)^2}$$

$$P = \text{auctg} \frac{-\omega R_1 R_2 C_2 + \frac{1}{\omega C_1}}{\frac{C_2(R_1+R_2)+R_1C_1}{C_1}} = \text{auctg} \frac{\frac{1}{\omega} - \omega R_1 R_2 C_1 C_2}{C_2(R_1+R_2)+R_1C_1} = \text{auctg} \frac{1 - \omega^2 R_1 R_2 C_1 C_2}{\omega(C_2(R_1+R_2)+R_1C_1)}$$

$$U_2(j\omega) = H(j\omega) \cdot U_1(j\omega)$$

$$I(j\omega) = \frac{U_g(t)}{R_g + \frac{1}{j\omega C_1} + R_1 \parallel \left(R_2 + \frac{1}{j\omega C_2} \right)} = \frac{10 \text{ V} \cdot \sin(\omega t)}{1589,51 + j66,98 \Omega}$$

$\underbrace{600 + j4472} \quad \underbrace{998,51 + j22,26}$
 $\xrightarrow{\hspace{10em}} 1589,51 + j66,98 \Omega$

$$= (6,25 - j0,262) \cdot 10^{-3} \text{ A} \cdot \sin(\omega t)$$

$\frac{998,51 + j22,26}{1589,51 + j66,98}$

$$U_1(j\omega) = I(j\omega) \cdot \left(\frac{1}{j\omega C_1} + R_1 \parallel \left(R_2 + \frac{1}{j\omega C_2} \right) \right) = 6,25 + j0,157 \text{ V} \cdot \sin(\omega t)$$


$\frac{2000 + j4472,36}{1589,51 + j66,98}$

$$U_2 = \frac{R_1 \cdot \left[\frac{C_2(R_1+R_2)+R_1C_1}{C_1} - j\left(\omega R_1 R_2 C_2 - \frac{1}{\omega C_1}\right) \right]}{\left(\frac{C_2(R_1+R_2)+R_1C_1}{C_1} \right)^2 + \left(\omega R_1 R_2 C_2 - \frac{1}{\omega C_1} \right)^2} \cdot (6,25 + j0,157) \cdot \sin(\omega t)$$

$$U_2 = (6,24 + j0,157) \cdot \sin(\omega t) \text{ V}$$

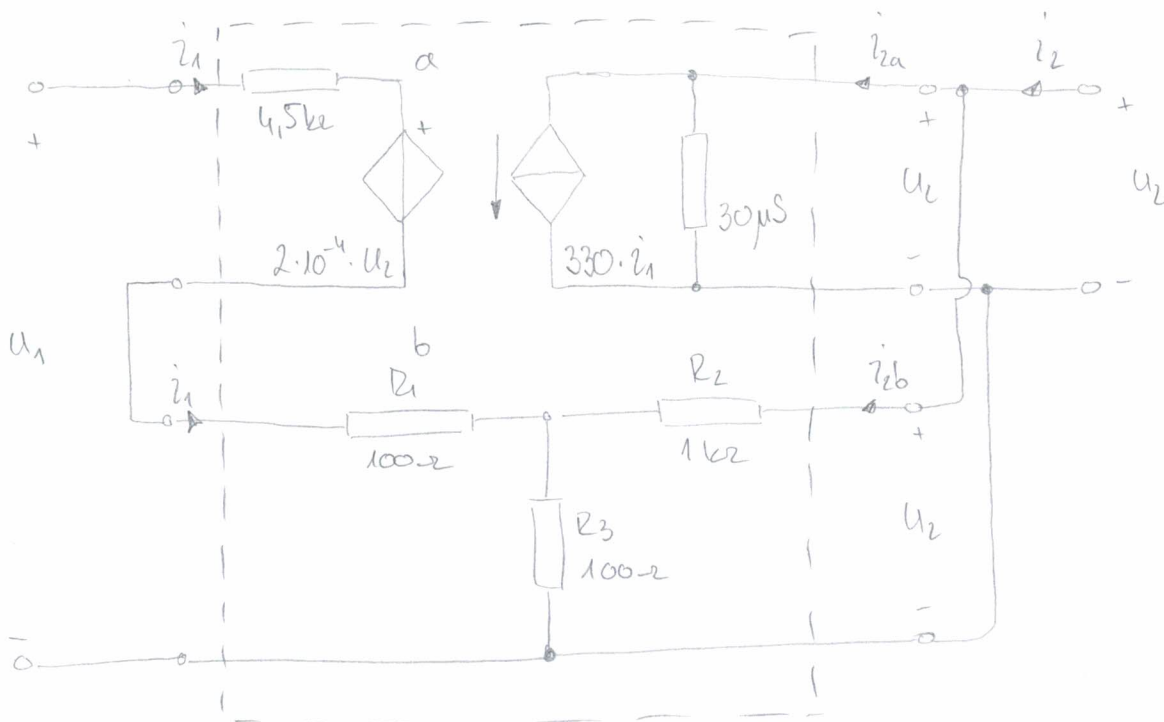$\frac{1006009}{1589,51 + j66,98}$
 $6,24 \text{ V} \cdot e^{+j1,44^\circ}$






$$[H_a] = \begin{bmatrix} 4,5 \text{ k}\Omega & 2 \cdot 10^{-4} \\ 330 & 30 \mu\text{s} \end{bmatrix}$$

$$[H_b] =$$

$$u_1 = h_{11} i_1 + h_{12} u_2$$

$$i_2 = h_{21} i_1 + h_{22} u_2$$

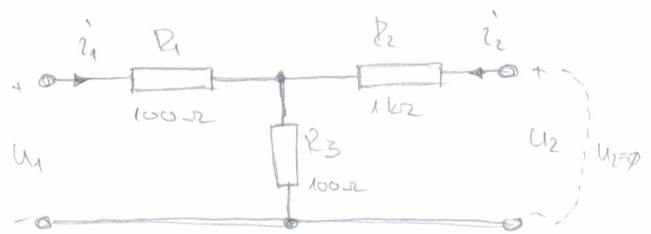


$$h_{11} = \frac{u_1}{i_1} \Big|_{u_2=0} = \frac{i_1 \cdot (R_1 + R_2 \parallel R_3)}{i_1} = \underline{\underline{190,91 \Omega}}$$

$$h_{21} = \frac{i_2}{i_1} \Big|_{u_2=0} = \frac{-i_1 \cdot R_2 \parallel R_3}{i_1} = \frac{R_3}{R_2 + R_3} = \underline{\underline{-90,91 \cdot 10^{-3}}}$$

$$h_{12} = \frac{u_1}{u_2} \Big|_{i_1=0} = \frac{i_2 \cdot R_3}{i_2 \cdot (R_2 + R_3)} = \underline{\underline{90,91 \cdot 10^{-3}}}$$

$$h_{22} = \frac{i_2}{u_2} \Big|_{i_1=0} = \frac{i_2}{i_2 \cdot R_2 + R_3 \parallel R_1} = \underline{\underline{952,381 \mu\text{s}}}$$
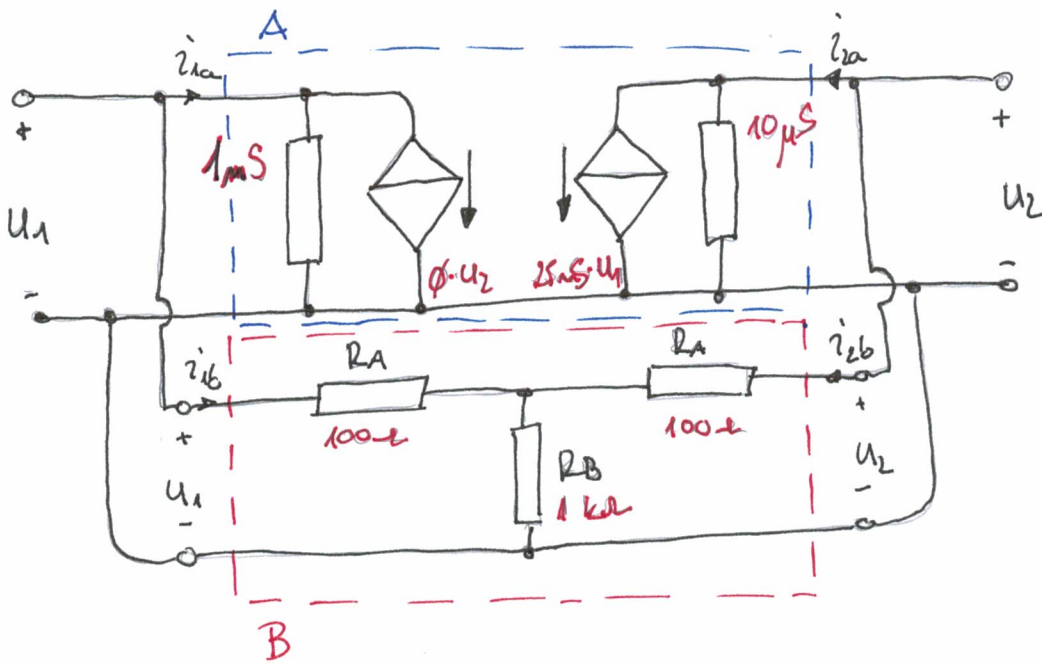
$$[H] = [H_a] + [H_b] = \begin{bmatrix} 4,691 \text{ k}\Omega & 9,11 \cdot 10^{-2} \\ 330,09 & 982,381 \mu\text{s} \end{bmatrix}$$



$$[Y_A] = \begin{bmatrix} 1 \text{ mS} & \phi \\ 25 \text{ mS} & 10 \mu\text{S} \end{bmatrix}$$

$$\begin{aligned} i_1 &= y_{11} U_1 + y_{12} U_2 \\ i_2 &= y_{21} U_1 + y_{22} U_2 \end{aligned}$$

$$[Y_B] =$$

$$y_{11} = \left. \frac{i_1}{U_1} \right|_{U_2 = \phi}$$

$$= \frac{i_1}{i_1 \cdot (R_A + R_A \parallel R_B)} = \boxed{5,238 \text{ mS}}$$

$$y_{12} = \left. \frac{i_1}{U_2} \right|_{U_1 = \phi} = \frac{-i_2 \cdot R_A \parallel R_B}{R_A}$$

$$= \frac{\frac{R_A R_B}{R_A R_B}}{\frac{R_A (R_A + \frac{R_A R_B}{R_A + R_B})}{R_A (R_A + 2R_B)}} = \frac{-R_B}{R_A (R_A + 2R_B)} = \boxed{-4,762 \text{ mS}}$$

$$y_{21} = \left. \frac{i_2}{U_1} \right|_{U_2 = \phi} = y_{12} = \boxed{-4,762 \text{ mS}}$$

$$[Y_B] = \begin{bmatrix} 5,238 \text{ mS} & -4,762 \text{ mS} \\ -4,762 \text{ mS} & 5,238 \text{ mS} \end{bmatrix}$$

$$y_{22} = \left. \frac{i_2}{U_2} \right|_{i_1 = \phi} = \frac{i_2}{i_2 (R_A + R_A \parallel R_B)} = \boxed{5,238 \text{ mS}}$$

$$[Y] = [Y_A] + [Y_B] = \begin{bmatrix} 6,238 \text{ mS} & -4,762 \text{ mS} \\ 20,238 \text{ mS} & 5,238 \text{ mS} \end{bmatrix}$$