

- 1.)  $-U_{th1} + I_1(R_{12} + R_3) + I_3 R_4 = 0$
- 2.)  $U_{th2} - I_2(R_5 + R_6) - I_3 R_4 + U_4 = 0$
- A.)  $I_2 - I_1 - I_3 = 0$

1.) 
$$I_1 = \frac{U_{th1} - I_3 R_4}{R_{12} + R_3} = \frac{20 - I_3 \cdot 300}{300 + 100} = 18,18 \text{ mA}$$

2.) 
$$I_2 = \frac{U_{th2} + U_4 - I_3 R_4}{R_5 + R_6} = \frac{20 + 5 - I_3 \cdot 300}{100 + 200} = 34,25 \text{ mA} = I_{R_6}$$

$$U_{R_6} = I_2 \cdot R_6 = 34,25 \text{ mA} \cdot 200 \Omega = 6,97 \text{ V}$$

$$U_{R_6} = -6,97 \text{ V}$$

Ja jeste u drugo smer

$$I_3 = \left( \frac{U_{th1} - I_3 R_4}{R_{12} + R_3} \right) - \left( \frac{U_{th2} + U_4 - I_3 R_4}{R_5 + R_6} \right) = 0$$


$$I_3 \left( 1 + \frac{R_4}{R_{12} + R_3} + \frac{R_4}{R_5 + R_6} \right) = \frac{U_{th1}}{R_{12} + R_3} + \frac{U_{th2} + U_4}{R_5 + R_6}$$

2,75 0,133



$$I_3 = 48,49 \text{ mA}$$

$$P_{RC} = I_{R_6} \cdot U_{R_6} = 0,253 \text{ W}$$


PO METODI SUPERPOZICIJE

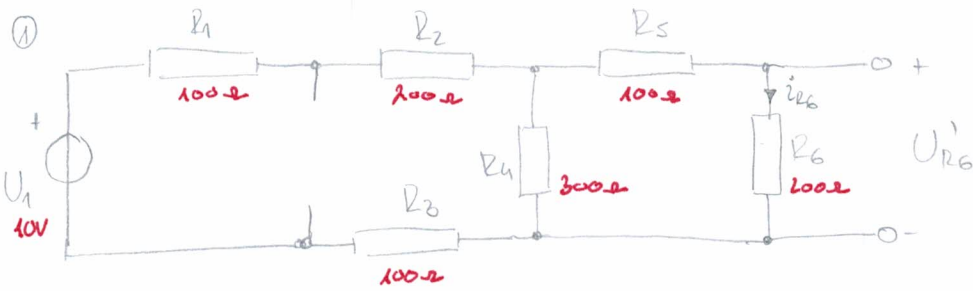
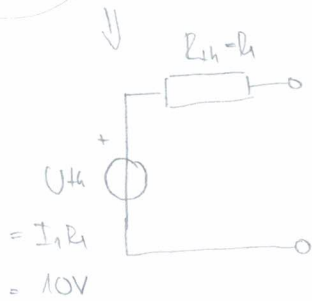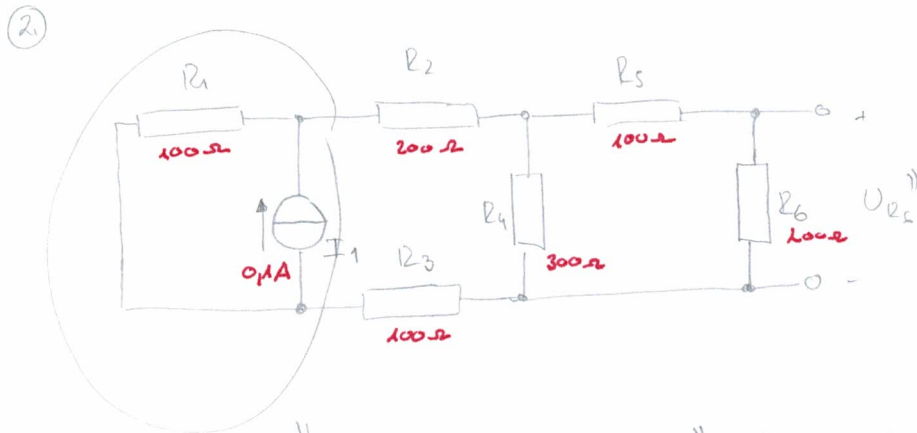
$$U'_{R6} = \frac{U_1 \cdot R_4 \parallel (R_5 + R_6) \cdot R_6}{(R_1 + R_2 + R_3 + R_4 \parallel (R_5 + R_6)) \cdot (R_5 + R_6)} = \frac{10V \cdot 150\Omega \cdot 200\Omega}{550\Omega \cdot 300\Omega} = \boxed{1,82 V}$$



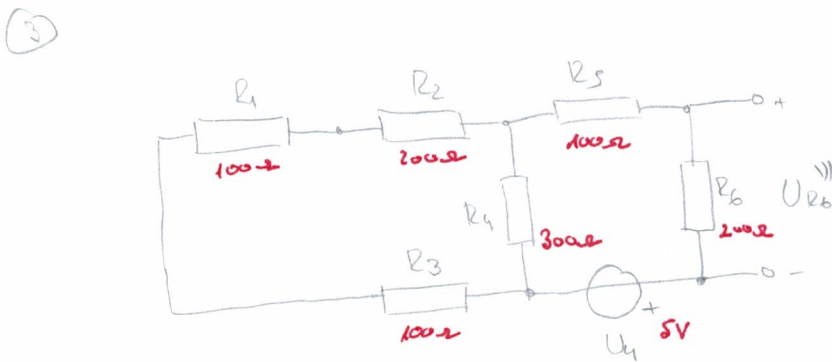
$$U''_{R6} = \frac{U_{th} \cdot R_4 \parallel (R_5 + R_6) \cdot R_6}{R_1 + R_2 + R_3 + R_4 \parallel (R_5 + R_6)} = \boxed{1,82 V}$$



$$U'''_{R6} = \frac{-U_4 \cdot R_6}{(R_1 + R_2 + R_3) \parallel R_4 + R_5 + R_6} = \boxed{-2,12 V}$$

6

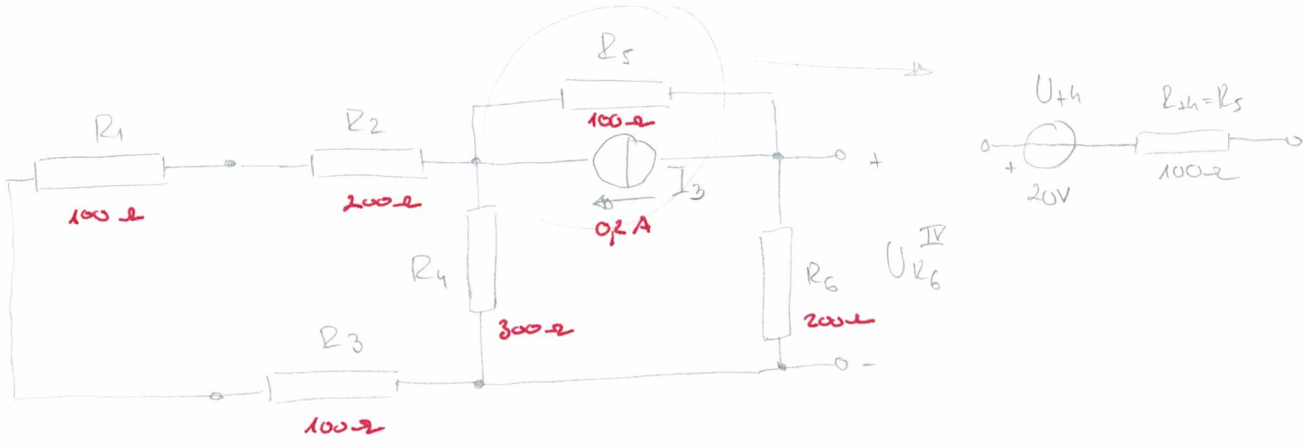

$$U_{R_6}^{IV} = \frac{-U_{th} \cdot R_6}{(R_1 + R_2 + R_3) \parallel R_4 + R_5 + R_6} = \boxed{-8,49 \text{ V}}$$

$$U_{R_6} = U_{R_6}^I + U_{R_6}^{II} + U_{R_6}^{III} + U_{R_6}^{IV}$$








$$= 1,82 \text{ V} + 1,82 \text{ V} - 2,12 \text{ V} - 8,49 \text{ V}$$

$$= \boxed{-6,97 \text{ V}}$$

$$I_{R_6} = \frac{U_{R_6}}{R_6} = \boxed{34,85 \text{ mA}}$$

$$P_{R_6} = I_{R_6} \cdot U_{R_6} = \boxed{0,243 \text{ W}}$$

po Theveninovem teoremu

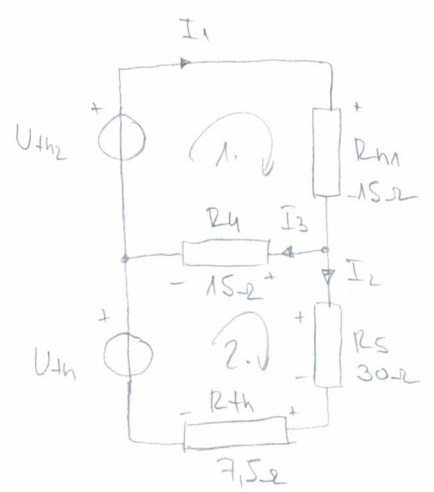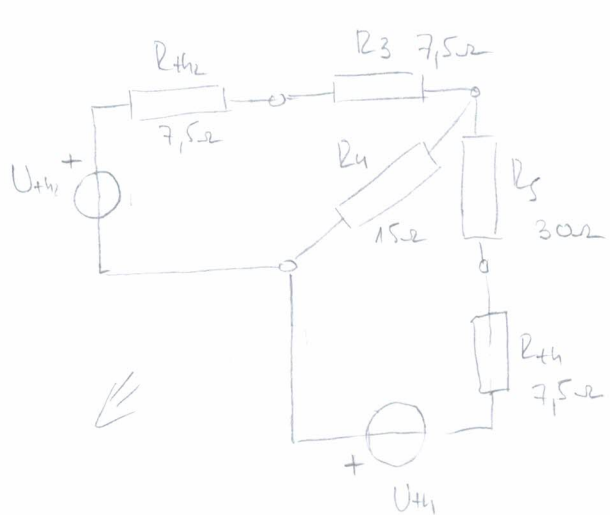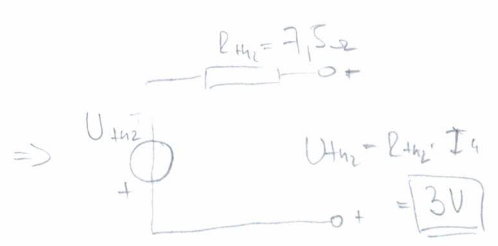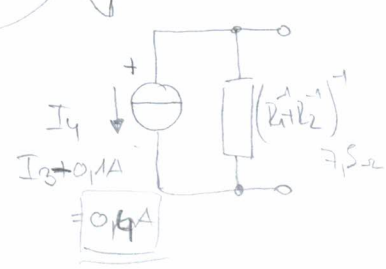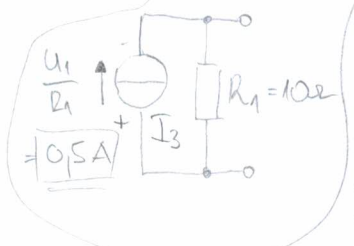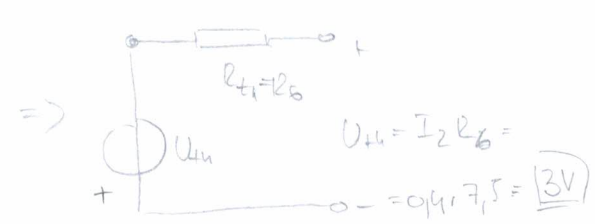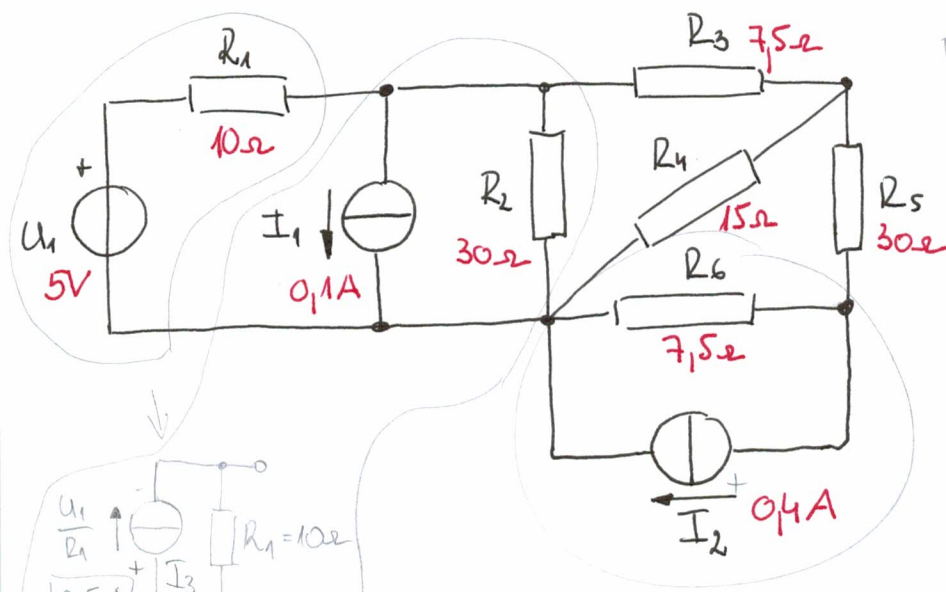

$$1.) -U_{th2} + I_1 R_{th1} + I_3 R_4 = 0 \Rightarrow I_1 = \frac{U_{th2} - I_3 R_4}{R_{th1}} = 0,15 \text{ A}$$

$$2.) -U_{th1} + I_2 (R_5 + R_{th2}) - I_3 R_4 = 0 \Rightarrow I_2 = \frac{U_{th1} + I_3 R_4}{R_5 + R_{th2}} = 0,1 \text{ A}$$

$$A.) I_2 - I_1 + I_3 = 0$$


$$U_{R5} = R_5 \cdot I_2 = 30 \Omega \cdot 0,1 \text{ A} = 3 \text{ V}$$

$$P_{R5} = U_{R5} \cdot I_2 = 3 \text{ V} \cdot 0,1 \text{ A} = 0,3 \text{ W}$$

$$\frac{+U_{th1} + I_3 R_4}{R_5 + R_{th2}} + \frac{-U_{th2} + I_3 R_4}{R_{th1}} - I_3 = 0$$


$$I_3 \left( \frac{R_4}{R_5 + R_{th2}} + \frac{R_4}{R_{th1}} + 1 \right) = \frac{U_{th2}}{R_{th1}} - \frac{U_{th1}}{R_5 + R_{th2}}$$

$$I_3 = 0,05 \text{ A}$$

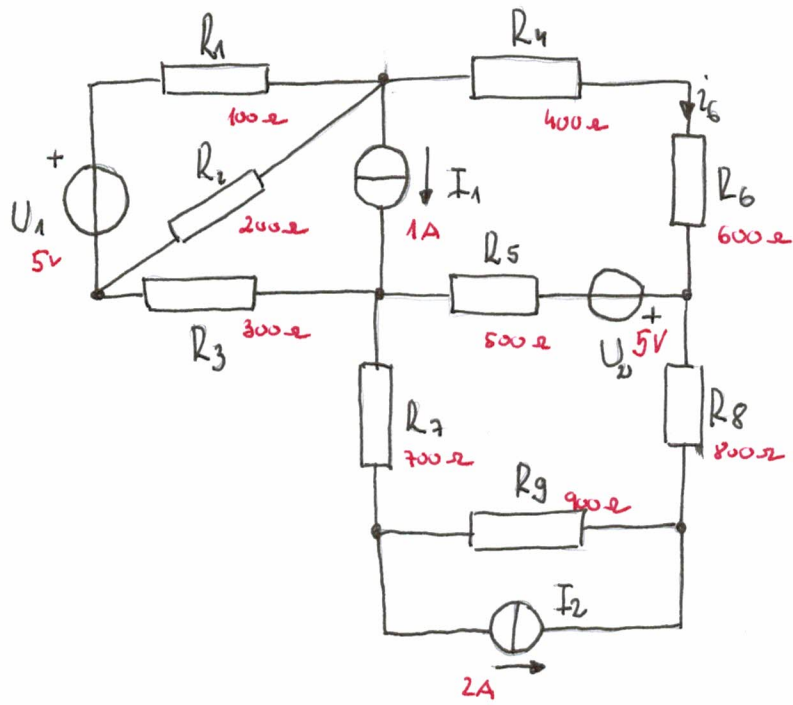

$i_6 = ?$   
 $U_{R6} = ?$   
 $P_{R6} = ?$


$U_2'$

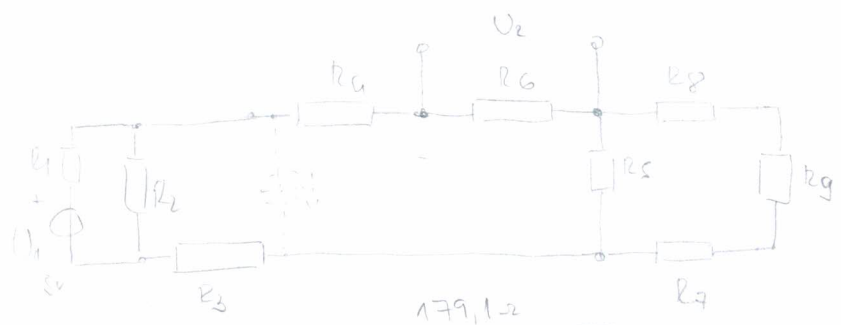

$$U_2' = \frac{5V \cdot R_2 \parallel (R_4 + R_6 + R_3 + R_5 \parallel (R_7 + R_8 + R_9)) \cdot R_6}{R_1 + (R_2 \parallel (R_4 + R_6 + R_3 + R_5 \parallel (R_7 + R_8 + R_9))) \cdot (R_4 + R_6 + R_3 + R_5 \parallel (R_7 + R_8 + R_9))} = \boxed{1,123V}$$

$\underbrace{\hspace{10em}}_{2400}$       $\underbrace{\hspace{10em}}_{1713,79\Omega}$   
 $\underbrace{\hspace{10em}}_{413,79}$       $\underbrace{\hspace{10em}}_{1713,79}$   
 $\underbrace{\hspace{10em}}_{179,1}$       $\underbrace{\hspace{10em}}_{279,1}$

$U_2''$

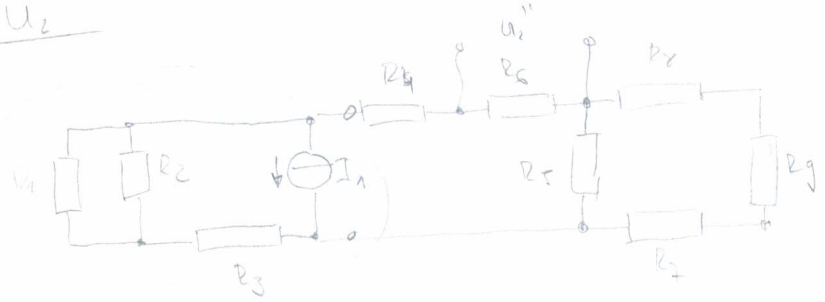


$U_{R4} = R_4 \cdot I_1$   
 $= 366,67V$   
 $R_{eq} = I_1 \cdot R_1 \parallel R_2$   
 $= 366,67\Omega$



$$U_2'' = \frac{-U_{R4} \cdot R_6}{R_4 + R_4 \parallel R_2 + R_5 \parallel (R_7 + R_8 + R_9)} = \boxed{-123,56V}$$

$\underbrace{\hspace{10em}}_{413,79}$       $\underbrace{\hspace{10em}}_{1750,46\Omega}$


$U_2'''$

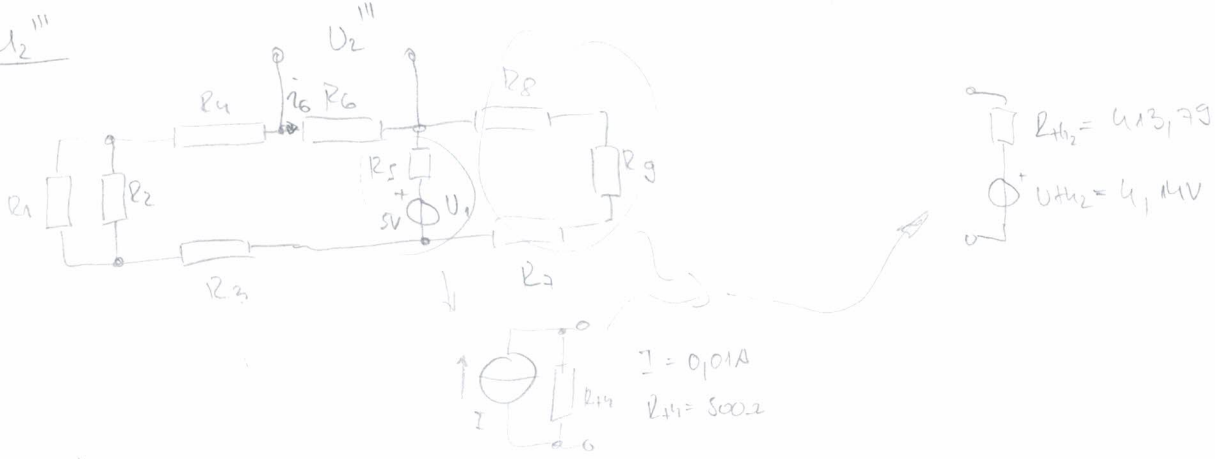

$$U_2''' = \frac{U_{th2} \cdot R_6}{R_{th2} + R_6 + R_4 + R_3 + R_1 \parallel R_2} = \boxed{-1,39 \text{ V}}$$

1780,954

$U_2^{IV}$

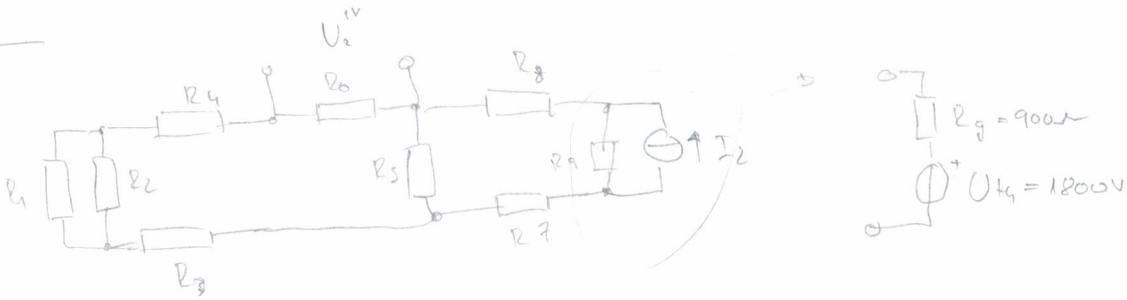

$$U_2^{IV} = \frac{U_{I2} \cdot R_5 \parallel (R_1 \parallel R_2 + R_3 + R_4 + R_6) \cdot R_6}{((R_1 \parallel R_2 + R_3 + R_4 + R_6) \parallel R_5 + R_8 + R_7 + R_9) \cdot (R_6 + R_4 + R_3 + R_1 \parallel R_2)} = \boxed{-104,58 \text{ V}}$$

366,07      2400      1366,67

1366,67      366,07

2766,072

$$U_{R6} = U_2' + U_2'' + U_2''' + U_2^{IV} =$$

$$= 1,123 \text{ V} - 123,56 \text{ V} + 1,39 \text{ V} - 104,58 \text{ V} =$$

$$= \boxed{-228,407 \text{ V}}$$

$$P_{R6} = i_{k6} \cdot U_{R6} = \boxed{86,95 \text{ W}}$$

$$i_{k6} = \frac{U_{R6}}{R_6} = \boxed{-0,381 \text{ A}}$$