

$$U_{R1} = 30 - j20 \text{ V}$$

$$I = ? \quad I = I_1 + I_2$$

$$R_1 = 10 \Omega$$

$$R_2 = 20 \Omega$$

$$R_3 = 30 \Omega$$

$$X_{L1} = 10 \Omega$$

$$X_{L2} = 20 \Omega$$

$$X_{C1} = 20 \Omega$$

$$X_{C2} = 10 \Omega$$

$$I_1 = \frac{U_{R1}}{R_1} = \frac{30 - j20}{10} = \underline{\underline{3 - j2 \text{ A}}}$$

$$U_1 = I_1 \cdot Z_1 = (3 - j2) \cdot (10 - j20) = \underline{\underline{-10 - j80 \text{ V}}}$$

$$I_2 = \frac{U_1}{jX_{L1}} = \frac{-10 - j80}{j10} = \underline{\underline{8 + j \text{ A}}}$$

$$I = I_1 + I_2 = (3 - j2) + (-8 + j) = \underline{\underline{5 - j \text{ A}}}$$

$$Z = ? \quad Z = Z_2 + Z_3 + R_2$$


$$Z_2 = \frac{Z_1 \cdot jX_{L1}}{Z_1 + jX_{L1}} = \frac{(10 - j20) \cdot j10}{(10 - j20) + j10} = \underline{\underline{5 + j15 \Omega}}$$

$$Z_3 = \frac{(30 + j20) \cdot (-j10)}{30 + j20 - j10} = \underline{\underline{3 - j11 \Omega}}$$

$$Z = 5 + j15 + 3 - j11 + 20 = \underline{\underline{28 + j4 \Omega}}$$



2

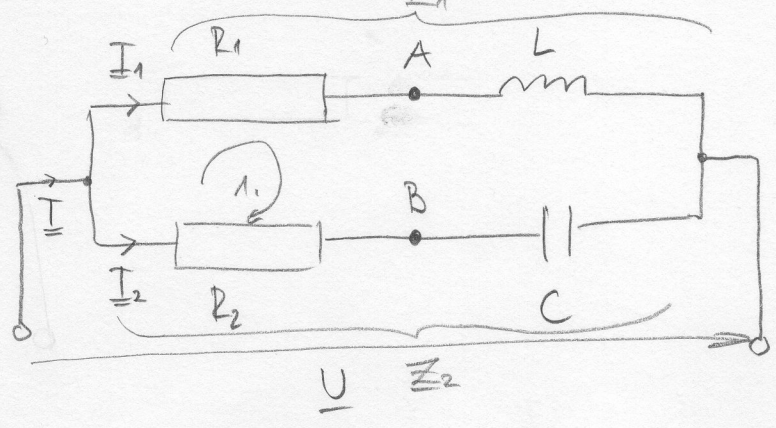

$\underline{U}_{AB} = ?$

$\underline{U} = 130 \text{ V} \quad \underline{Z}_1 = 8 + j6 \Omega \quad \underline{Z}_2 = 12 - j5 \Omega$

1)  $\underline{U}_{R1} + \underline{U}_{AB} - \underline{U}_{R2} = 0$

$\underline{U} = \underline{I}_2 \cdot \underline{Z}_2 = \underline{I}_1 \cdot \underline{Z}_1$

$\Rightarrow \underline{I}_1 = \frac{\underline{U}}{\underline{Z}_1} = \frac{130}{8 + j6} = \underline{104 - j7,8 \text{ A}}$

$\underline{I}_2 = \frac{\underline{U}}{\underline{Z}_2} = \frac{130}{12 - j5} = \underline{9,23 + j3,85 \text{ A}}$

$\underline{U}_{R1} = \underline{I}_1 \cdot R_1 = (104 - j7,8) \cdot 8 = \underline{832 - j62,4 \text{ V}}$


$\underline{U}_{R2} = \underline{I}_2 \cdot R_2 = (9,23 + j3,85) \cdot 12 = \underline{110,8 + j46,2 \text{ V}}$

$\underline{U}_{AB} = \underline{U}_{R2} - \underline{U}_{R1} = (110,8 + j46,2) - (832 - j62,4) = \underline{27,6 + j108,6 \text{ V}}$


$= \underline{112 e^{j75,75^\circ} \text{ V}}$



3

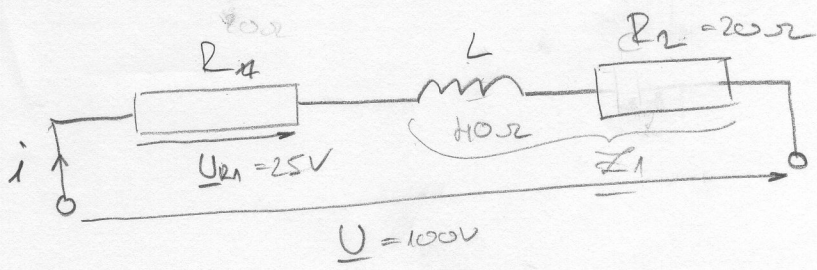

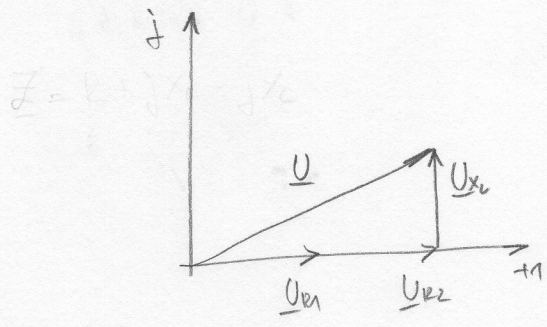$U = 100V$   
 $U_{R1} = 25V$   
 $R_2 = 20\Omega$   
 $X_L = 40\Omega$



$Z = ?$

$$U^2 = (U_{R1} + U_{R2})^2 + U_{X_L}^2$$

$$I_{R2} = I_{X_L}$$

$$\frac{U_{R2}}{R_2} = \frac{U_{X_L}}{X_L} \Rightarrow \frac{U_{R2}}{U_{X_L}} = \frac{R_2}{X_L} = \frac{20}{40} = \frac{1}{2} \Rightarrow U_{X_L} = 2U_{R2}$$

$$U^2 = (U_{R1} + U_{R2})^2 + (2U_{R2})^2$$

$$100^2 = 25^2 + 50U_{R2} + U_{R2}^2 + 4U_{R2}^2$$

$$100^2 = 25^2 + 50U_{R2} + 5U_{R2}^2 \quad /: 5$$

$$2000 = 125 + 10U_{R2} + U_{R2}^2$$

$$U_{R2}^2 + 10U_{R2} - 1875 = 0$$

$$U_{R2} = \frac{-10 \pm \sqrt{10^2 - 4 \cdot (-1875)}}{2}$$

$$U_1 = 38,37V \checkmark = U_{R2}$$


$$U_2 = -48,37V \text{ rne ustawa}$$

$$I = \frac{U_{R2}}{R_2} = \frac{38,37}{20}$$

$$R_1 = \frac{U_{R1}}{I} = \frac{25}{1,9185}$$
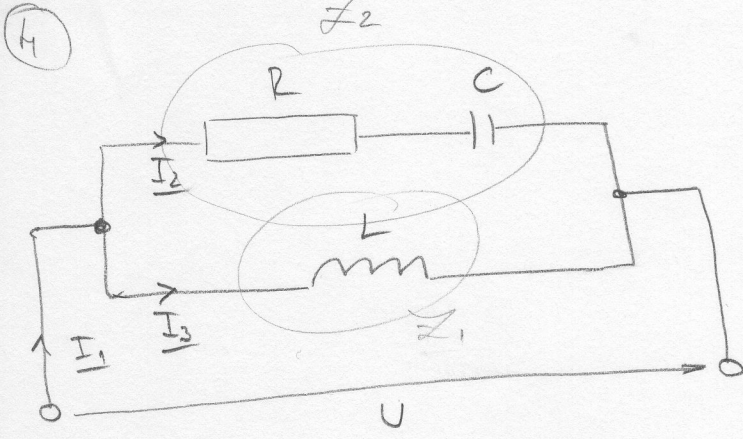
$$Z = R_1 + R_2 + jX_L = \underline{\underline{33,03 + j40\Omega}}$$






$$\underline{I}_1 = \underline{I}_2 + \underline{I}_3$$

$$Z_2 = \frac{U}{I_2} = \frac{100V}{7,21A} = \underline{13,87 \Omega}$$

$$Z_2 = Z_2 e^{j\varphi_2} = \underline{13,87 \cdot e^{-j56,29^\circ}}$$

Iskrenjen tokovi:

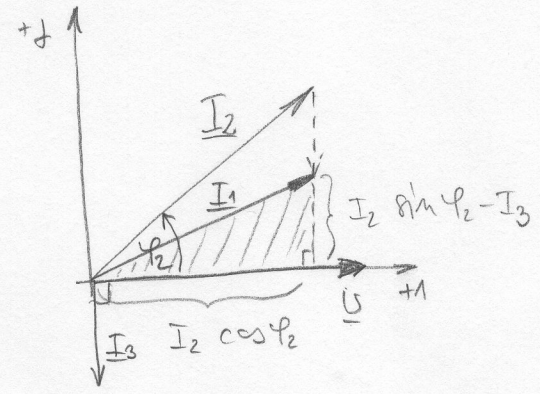- $I_1 = 5A$
- $I_2 = 7,21A$
- $I_3 = 3A$
- $U = 100V$
- $f = 100 Hz$



de.  $13,87 \cdot \cos \varphi_2$   
 Imi  $13,87 \sin \varphi_2$

$$Z_2 = R - jX_C = \underline{77 - j11,54 \Omega}$$

$Z = ?$

$$X_L = \frac{U}{I_3} = \underline{33,33 \Omega}$$

$$I_1^2 = (I_2 \sin \varphi_2 - I_3)^2 + (I_2 \cos \varphi_2)^2$$

$$I_1^2 = I_2^2 \sin^2 \varphi_2 - 2I_2 I_3 \sin \varphi_2 + I_3^2 + I_2^2 \cos^2 \varphi_2$$

$$I_1^2 = I_2^2 (\sin^2 \varphi_2 + \cos^2 \varphi_2) - 2I_2 I_3 \sin \varphi_2 + I_3^2$$

$$I_1^2 = I_2^2 + I_3^2 - 2I_2 I_3 \sin \varphi_2$$

$$\sin \varphi_2 = \frac{I_1^2 - I_2^2 - I_3^2}{2I_2 I_3} \Rightarrow \varphi_2 = \underline{56,29^\circ}$$


$$Z = \frac{(R - jX_C) \cdot jX_L}{R - jX_C + jX_L}$$

$$Z = \frac{(77 - j11,54) \cdot j33,33}{77 - j11,54 + j33,33}$$

$$Z = \underline{16,02 + j11,99 \Omega}$$



5

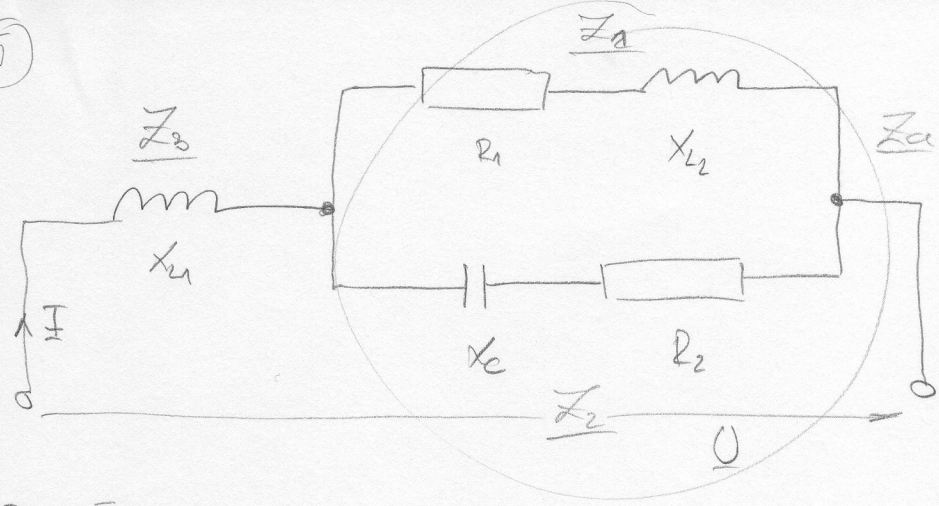

- $R_1 = 5 \Omega$
- $R_2 = 8 \Omega$
- $X_{L1} = 10 \Omega$
- $X_{L2} = 4 \Omega$
- $X_C = 2 \Omega$

$$\underline{U} = \frac{100}{\sqrt{2}} e^{j30^\circ} = 50\sqrt{2} + j50 = 132,29 e^{j22,21^\circ}$$

$$U = 100 \cdot e^{j30^\circ}$$

$\underline{I} = ?$

$\underline{Z}_n = ?$

$$\underline{Z}_a = \frac{(s + ja)(8 + j2)}{(s + ja) + (8 + j2)} = \underline{3,86 + j1,1 \Omega}$$


$$\underline{Z}_n = \underline{Z}_a + \underline{Z}_3 = \underline{3,86 + j11,1 \Omega}$$

$$\underline{I} = \frac{\underline{U}}{\underline{Z}_n} = \frac{50\sqrt{2} + j50}{3,86 + j11,1} = \underline{6,44 - j5,56 A}$$

$$= 8,51 e^{j40,82^\circ}$$



6

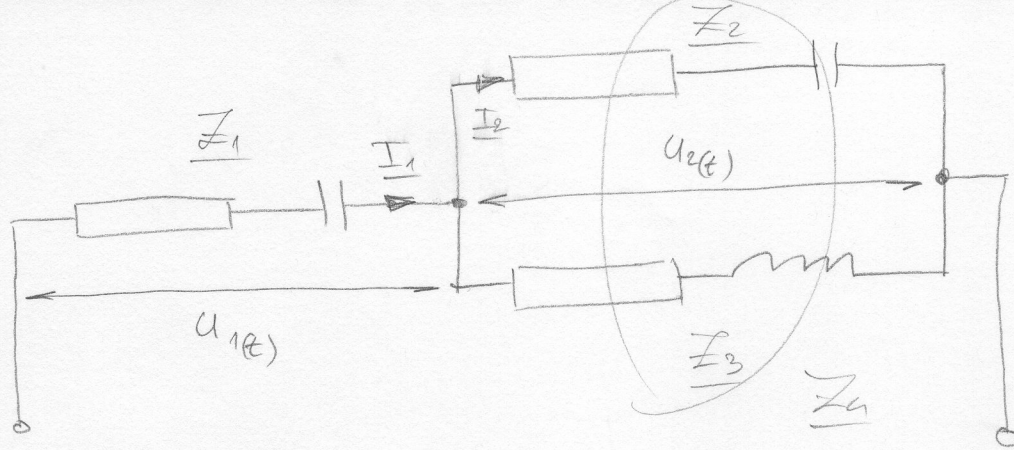

$$u_2(t) = 80 \cos(\omega t + 45^\circ)$$

$$Z_1 = 10 - j20 \Omega$$

$$Z_2 = 20 - j10 \Omega$$

$$Z_3 = 10 + j5 \Omega$$

$$u_1(t) = ?$$

$$\underline{U}_2 = \frac{80}{\sqrt{2}} \cdot e^{j45^\circ} = 40 + j40$$

$$\underline{Z}_a = \frac{Z_2 Z_3}{Z_2 + Z_3} = \frac{(20 - j10)(10 + j5)}{(20 + j10) + (10 + j5)}$$

$$\underline{Z}_a = 8.11 + j1.35 \Omega$$

$$\underline{I}_1 = \frac{\underline{U}_2}{\underline{Z}_a} = \frac{40 + j40}{8.11 + j1.35} = \boxed{5.6 + j4 \text{ A}}$$

$$\underline{U}_1 = \underline{I}_1 \cdot \underline{Z}_1 = (5.6 + j4) \cdot (10 - j20) = 136 - j72$$

$$= \boxed{153.88 e^{-j27.9^\circ}}$$

$$u_1(t) = 153.88 \sqrt{2} \cdot \cos(\omega t - 27.9^\circ)$$

